

# ELEN 50 Class 09 – The Node Voltage Method: Dependent Sources and Supernodes


S. Hudgens

## To Recap the Node Voltage Method from Last Lecture:


- Identify all extraordinary nodes, set one as the reference (ground) node, and assign node voltages ( $v_1$ ,  $v_2$ ,  $v_3$ , etc.) to the  $n_{\text{ex}} - 1$  remaining nodes.
- At each of the  $n_{\text{ex}} - 1$  nodes, write the KCL equation requiring the sum of all currents leaving the node to be zero.
- Solve the  $n_{\text{ex}} - 1$  independent simultaneous equations to determine the unknown node voltages.

let's talk, one more time, about the issue of how to know which way the current is flowing in a circuit.

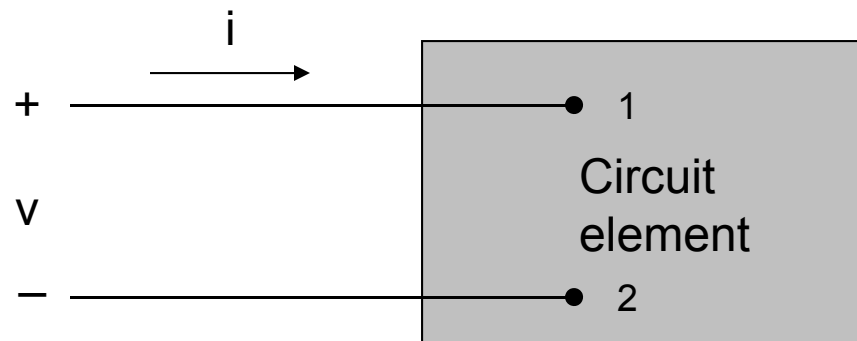- As we know, the “passive sign convention” states: whenever the current in an element is flowing in the direction of the reference voltage drop across an element, we choose to use a positive sign in any expression that relates the voltage to the current.



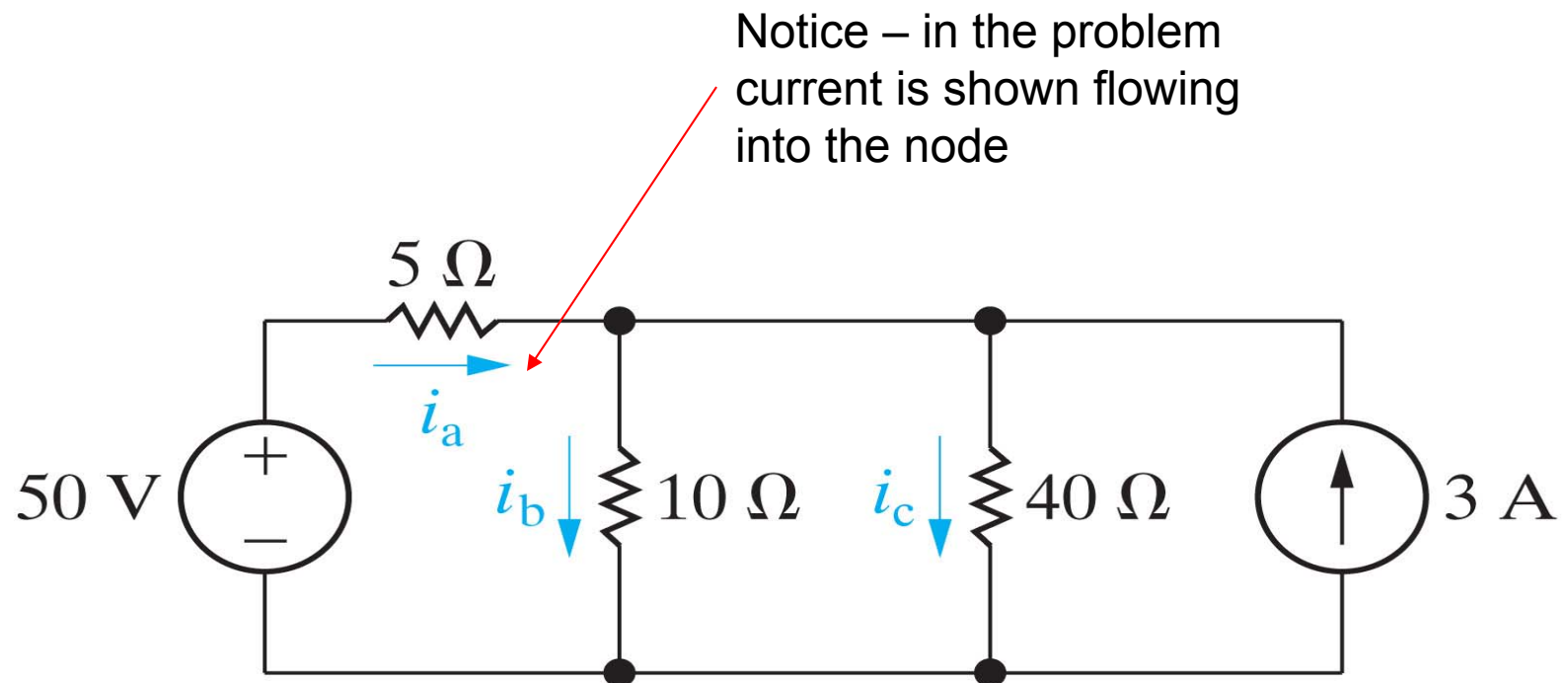
Here's a circuit we analyzed earlier -- we want to determine all of the branch currents using the node voltage method.




- We wrote KCL for currents leaving the single essential node as:

$$(v_1 - 50)/5 + v_1/10 + v_1/40 - 3 = 0$$

$$\rightarrow v_1 = 40V$$

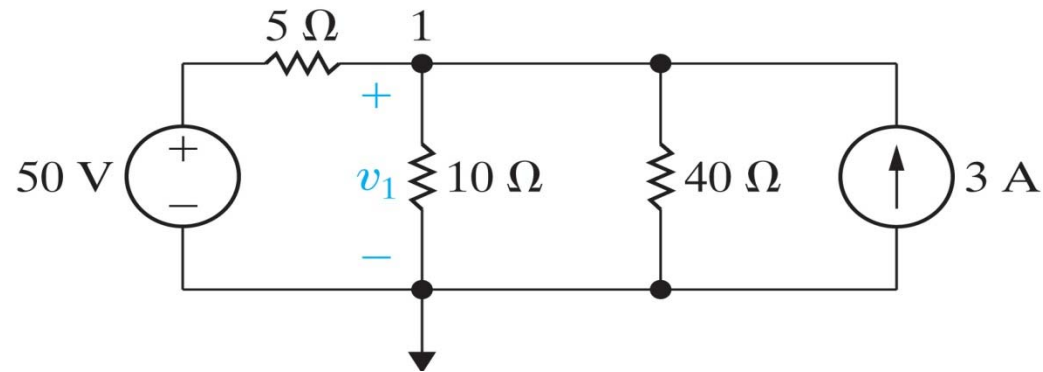

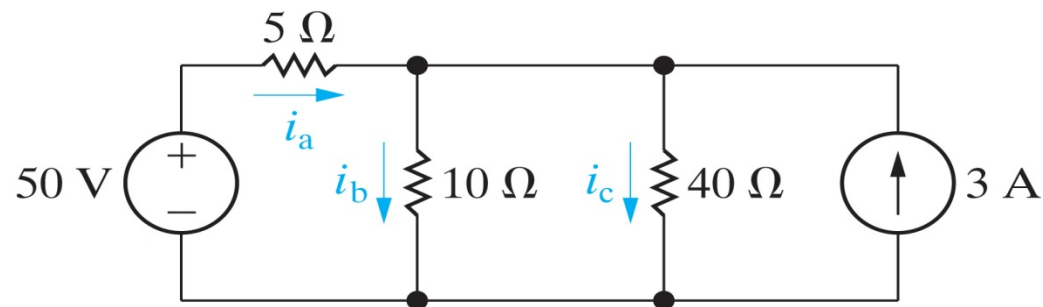So, for the current directions shown below :  $i_a = (50-40)/5 = 2A$ ,  $i_b = 40/10 = 4A$ , and  $i_c = 40/40 = 1A$



- Some might object that if we are supposed to write the KCL for currents leaving the single essential node the equation should have been:

$$-(50 - v_1)/5 + v_1/10 + v_1/40 - 3 = 0$$

We should write the first term as  $-(50 - v_1)/5$  because the current is flowing into the node from this branch according to the passive sign convention.

However...this is just:

$(v_1 - 50)/5 + v_1/10 + v_1/40 - 3 = 0$  which is the equation we saw earlier ...and we get  $v_1 = 40\text{V}$  and  $i_a$  is flowing into the node


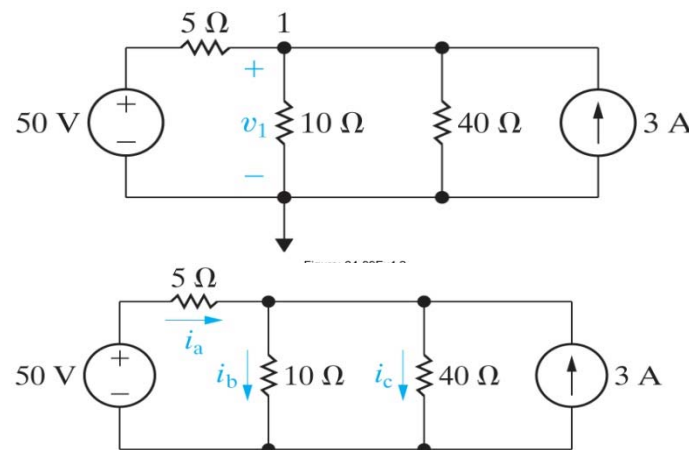


Figure: 04-08  
Copyright © 2008 Pearson Prentice Hall, Inc.

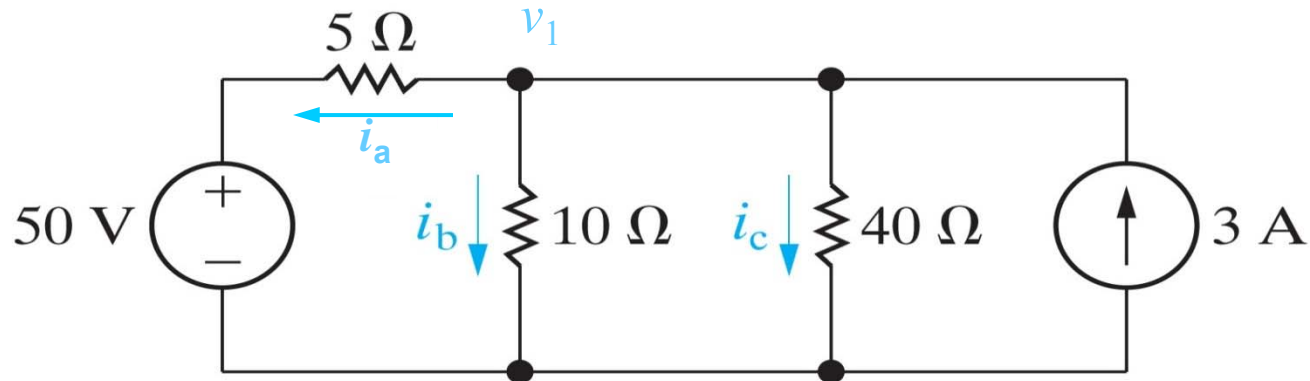

If we had drawn the current going the other direction (as shown above), then the passive sign convention would require that  $v_1$  is higher than 50V (since current “flows downhill”) and the KCL equation for this node would have been:

$$(v_1 - 50)/5 + v_1/10 + v_1/40 - 3 = 0$$


Which is exactly the same equation we used previously – and we get  $v_1 = 40\text{V}$ . Now, using Ohm’s law we calculate  $i_a = (v_1 - 50\text{V})/5\Omega$ . Since  $v_1 = 40\text{V}$ , this gives  $i_a = -2\text{A}$ . The minus sign means the current is actually flowing the other direction....the direction we had shown it flowing initially....so everything is OK.

Here's another one:

For the circuit shown below

$R_1 = 6\ \Omega$ ,  $R_2 = 6\ \Omega$ ,  $R_3 = 9\ \Omega$ ,  $I_{S1} = 2\text{ A}$ ,  
and  $I_{S2} = 0\text{ A}$ .

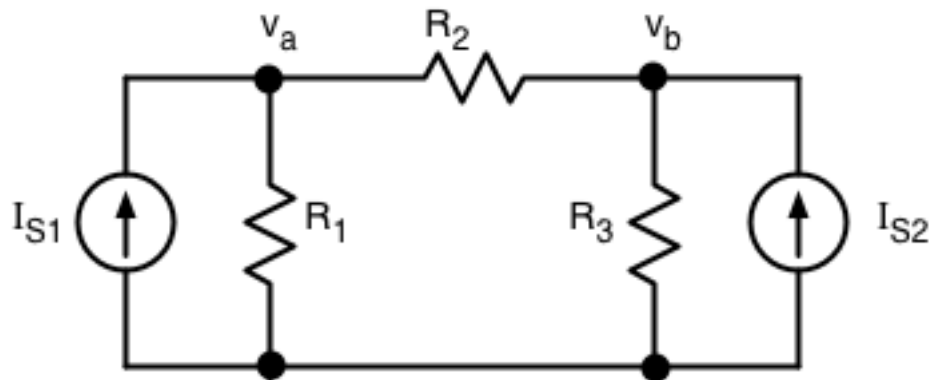
Use the node-voltage technique to find  $v_a$   
and  $v_b$ .



What is the first step? What is the second step?



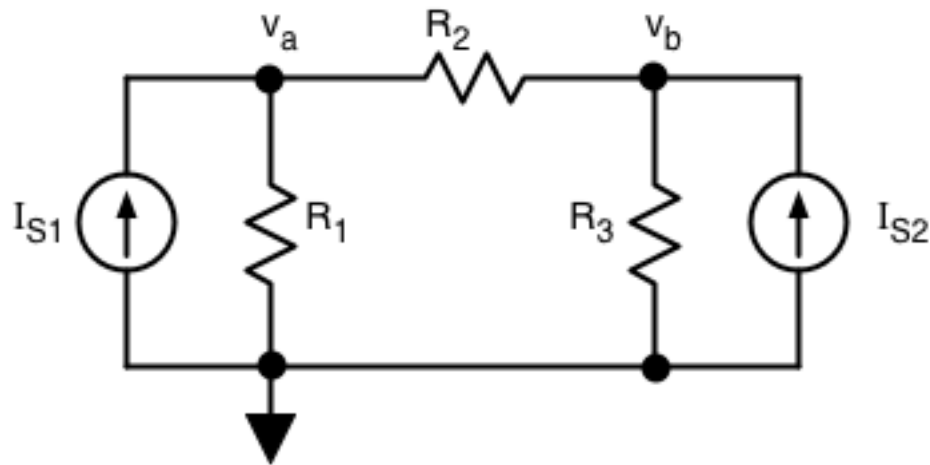Pick a ground reference and label remaining essential nodes




$R_1 = 6 \, \Omega$ ,  $R_2 = 6 \, \Omega$ ,  $R_3 = 9 \, \Omega$ ,  $I_{S1} = 2 \, \text{A}$ , and  $I_{S2} = 0 \, \text{A}$ .

$$-2 + \frac{v_a}{6} + \frac{v_a - v_b}{6} = 0$$

$$\frac{v_b}{9} - \left( \frac{v_a - v_b}{6} \right) + 0 = 0$$

$$v_a = 8.571 \, \text{V}, \text{ and } v_b = 5.143 \, \text{V}$$

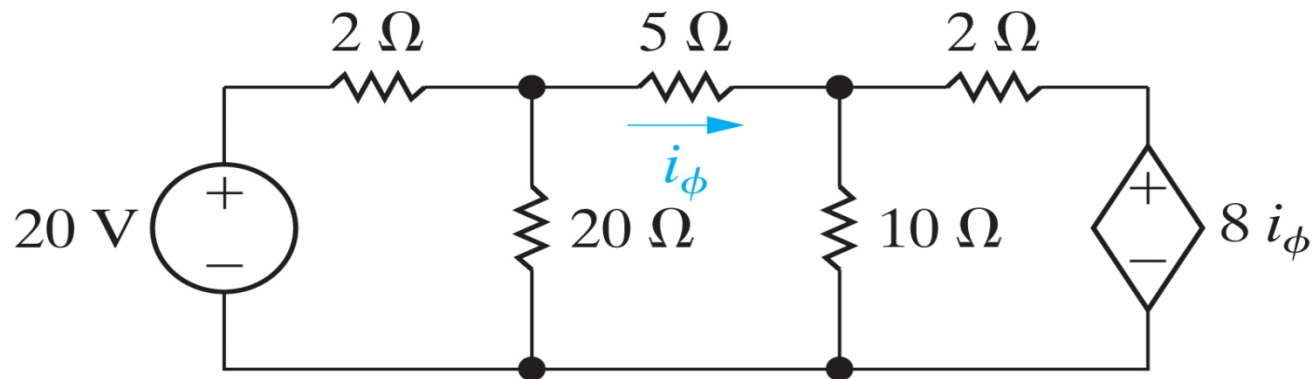- Now, let's talk about something new -- using the node voltage method with dependent sources.
- Consider the following circuit:




- It's similar to some we have analyzed and we want to solve for  $i_\phi$  using the node voltage method -- but notice, the circuit now contains a dependent voltage source.....and it depends on  $i_\phi$ . Will this introduce any complications in using the node voltage method?

- As usual, we identify the essential nodes, select a reference node, and label the appropriate voltages and currents.

- Summing all of the current flowing out of node 1 gives:

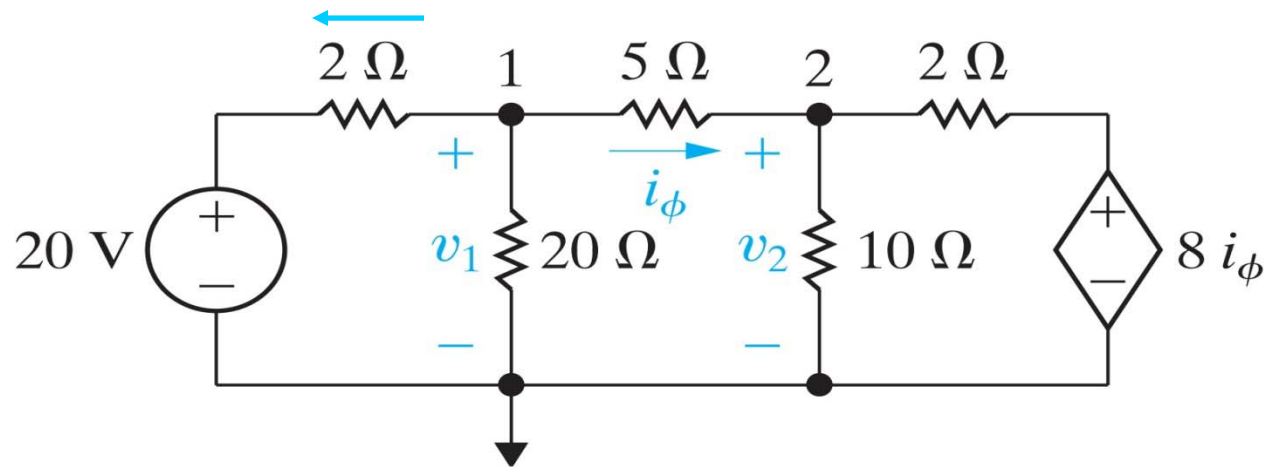$(v_1 - 20)/2 + v_1/20 + (v_1 - v_2)/5 = 0$  (notice here again, if we drew the current through the  $2\Omega$  resistor going in the other direction, then the term for this current would have been  $-(20 - v_1)/2$  ....and the equation would be unchanged.



now we can write the KCL equation for node 2


Node 1:  $(v_1 - 20)/2 + v_1/20 + (v_1 - v_2)/5 = 0$

Node 2:  $-(v_1 - v_2)/5 + v_2/10 + (v_2 - 8i_\phi)/2 = 0$

So it appears we've got two equations in three unknowns ( $v_1$ ,  $v_2$ , and  $i_\phi$ ). However, these aren't independent variables and we can express  $i_\phi$  in terms of  $v_1$  and  $v_2$  using Ohms law:  $i_\phi = (v_1 - v_2)/5$


So the equations become:  $0.75 v_1 - 0.2 v_2 = 10 \rightarrow v_2 = 10 \text{ V}$

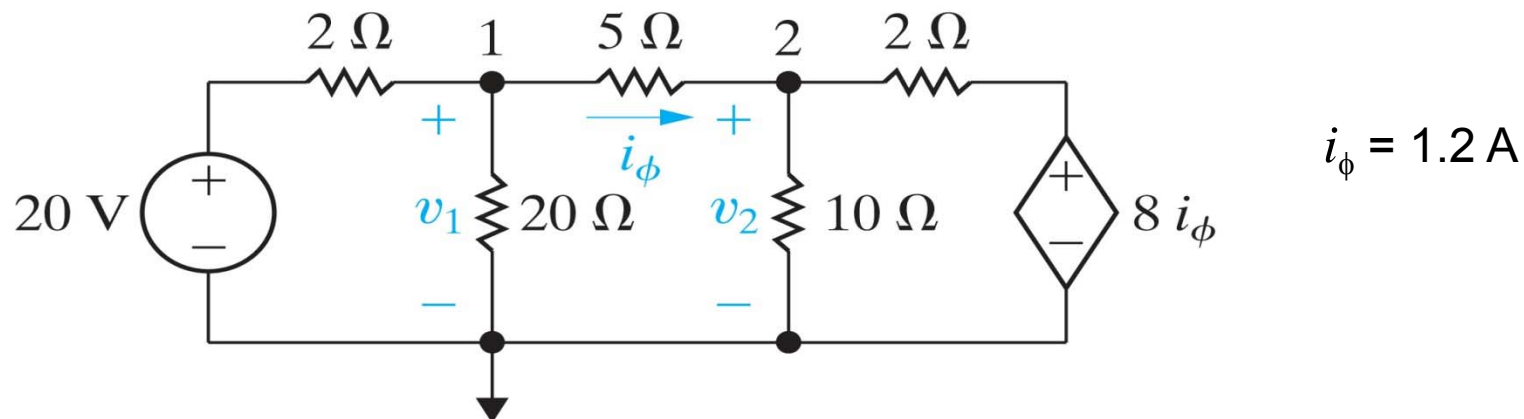$-v_1 + 1.6 v_2 = 0 \rightarrow v_1 = 16 \text{ V}$




If we have a dependent source, it's constraint equation must be used along with the KCL equations. 12

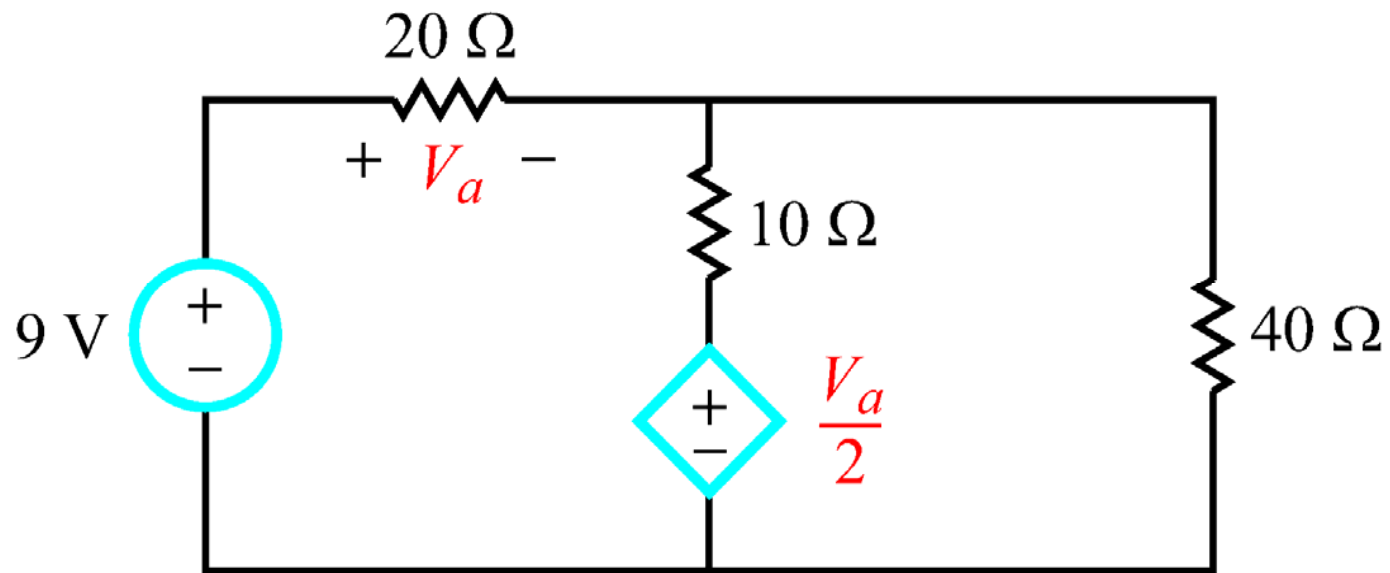Use Node Voltage Analysis to determine  $V_a$



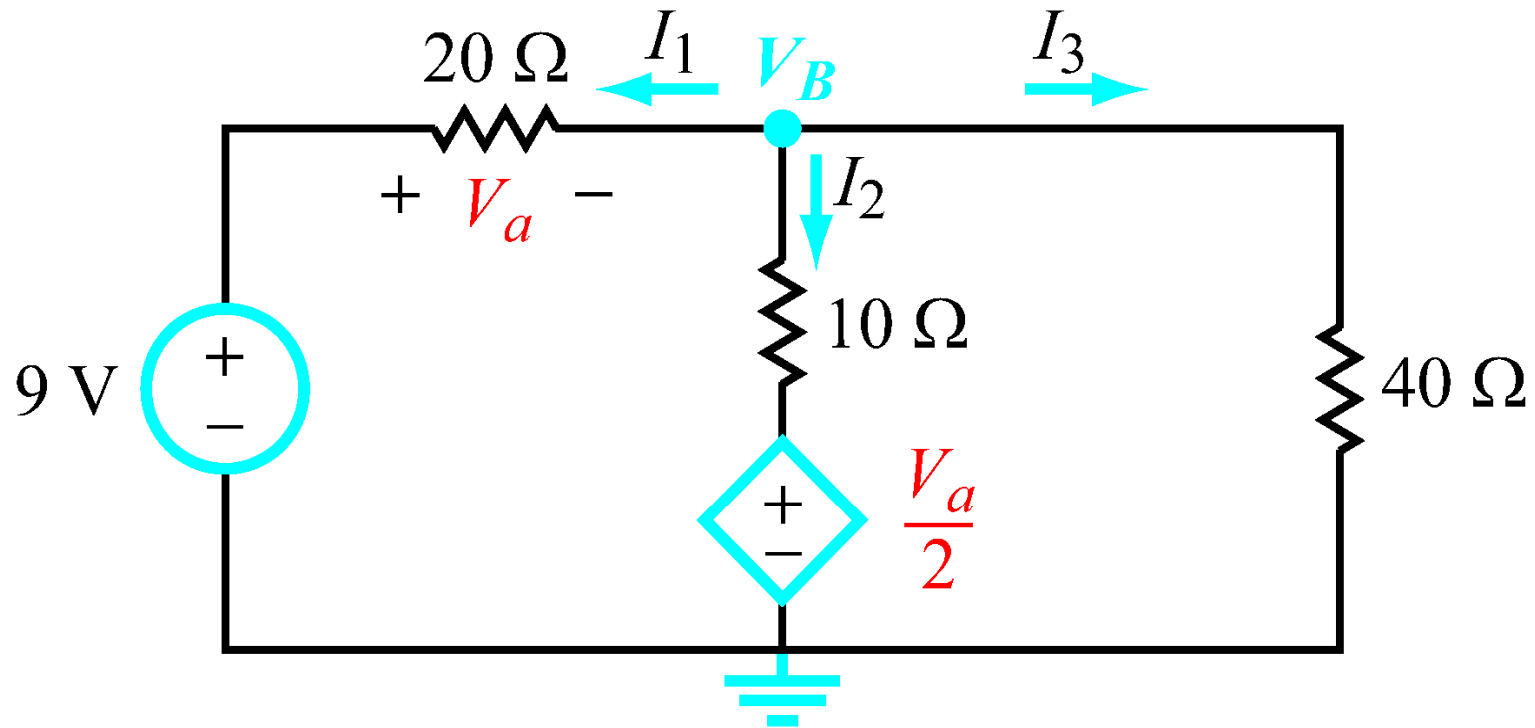What are the steps for node voltage analysis?



Just one equation

$$\frac{V_B - 9}{20} + \frac{V_B - \frac{V_a}{2}}{10} + \frac{V_B}{40} = 0$$


But since  $V_a = 9 - V_B$

$$V_a = 5V$$

why the minus sign
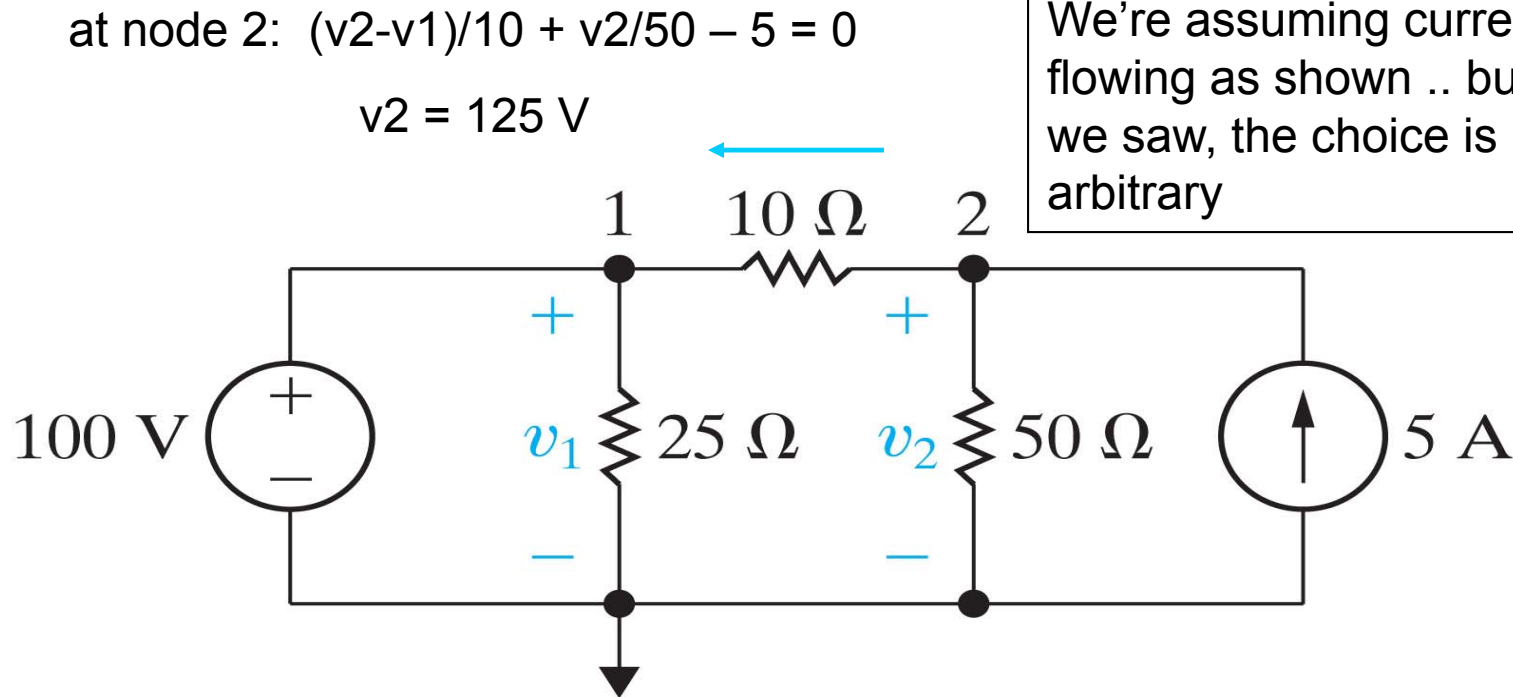
## Special Cases: Quasi-Supernodes and Supernodes


- In this circuit there are three essential nodes ...but two of them (node 1 and the reference node) are connected by a voltage source ...which constrains  $v_1$ ...so, basically, we already know  $v_1$ ! Node 1 is called a **quasi-supernode**!
- Consequently, although we'd expect two equations in two unknowns in the solution, there is really only one unknown voltage .... $v_2$ .


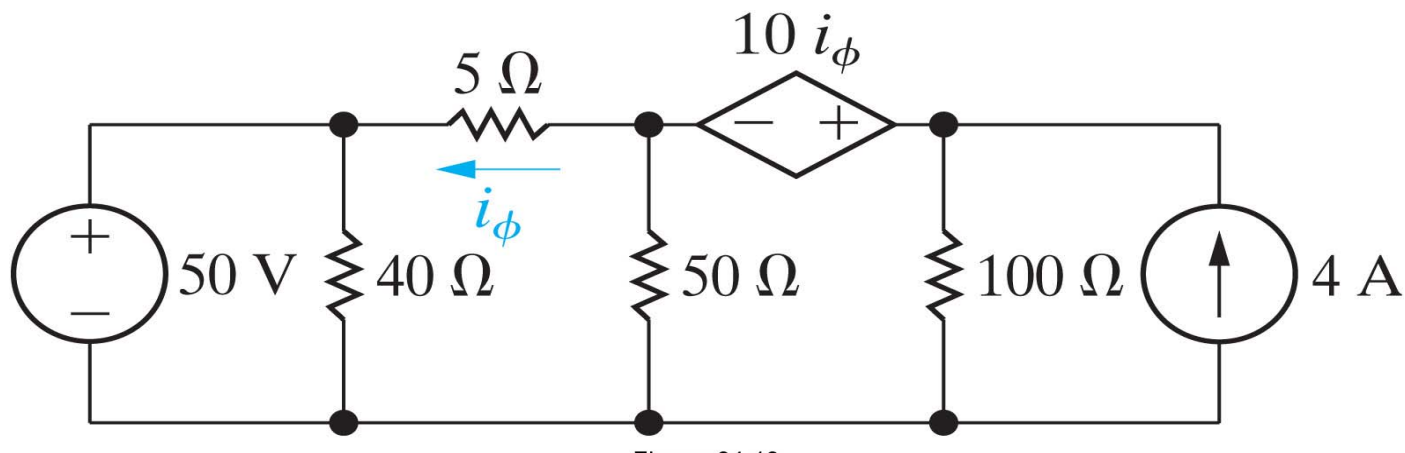
## Special Cases: Quasi-Supernodes and Supernodes

Here's another example of a circuit with voltage sources between essential nodes – in this case, we have four essential nodes, but two of them are connected by voltage sources – one independent and one dependent.

Consequently, we can use two equations rather than the four we would otherwise expect with four essential nodes. One of the nodes is a quasi-supernode if we pick the bottom nodes as ground..as we discussed earlier. We already know the voltage at that node --- it's 50V.





Node 2 and 3 together create a special situation. This configuration is called a “supernode.” The voltages at the two nodes are not independent and we can’t write the normal node voltage equations in terms of voltages and the resistance in the branches.

For node 2 we could label the unknown current through the dependent voltage source as  $i$  ...and then write for node 2:

$$(v_2 - v_1)/5 + v_2/50 + i = 0$$


Then for node 3 we can write:

$$v_3/100 - i - 4 = 0$$

Adding these two equations eliminates  $i$

$$(v_2 - v_1)/5 + v_2/50 + v_3/100 - 4 = 0 \text{ or } (v_2 - 50)/5 + v_2/50 + v_3/100 - 4 = 0$$

since  $v_1 = 50\text{V}$

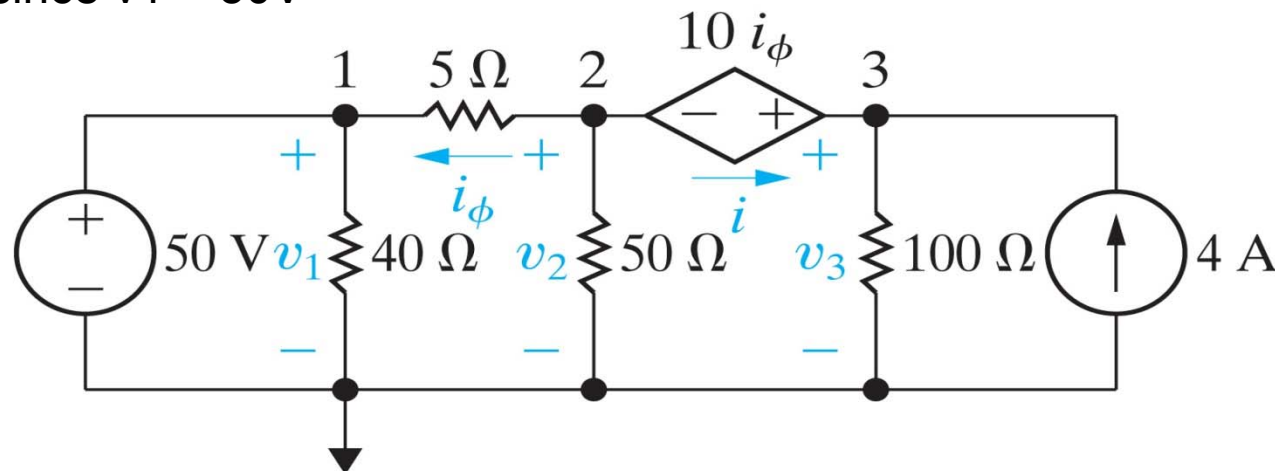


Now we can express  $v_3$  in terms of  $v_2$  because of the dependent voltage source between these two essential nodes:

$$v_3 = v_2 + 10 i_\phi$$

$$\text{and } i_\phi = (v_2 - 50)/5 \text{ so } v_3 = v_2 + 10(v_2 - 50)/5 = 2v_2 - 100$$

$$\text{Substituting for } v_3 \text{ in: } (v_2 - 50)/5 + v_2/50 + v_3/100 - 4 = 0$$
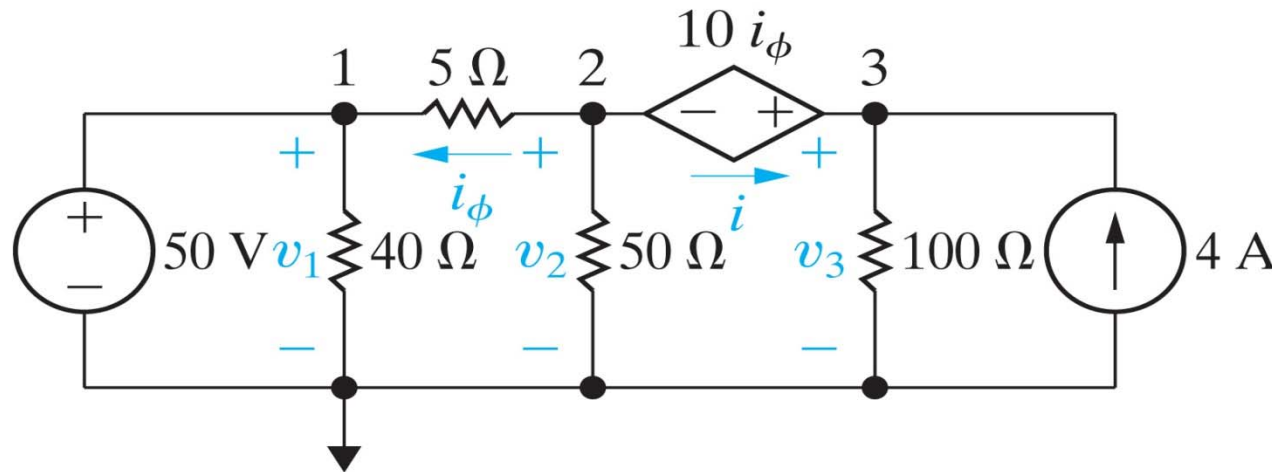
$$\text{Gives } v_2 = 60 \text{ V so } i_\phi = (60 - 50)/5 = 2 \text{ A and } v_3 = 60\text{V} + 20\text{V} = 80\text{V}$$




There's a simpler way to get the equation:

$$(v_2 - 50)/5 + v_2/50 + v_3/100 - 4 = 0$$

We can write it down directly by using the concept of a **supernode**.

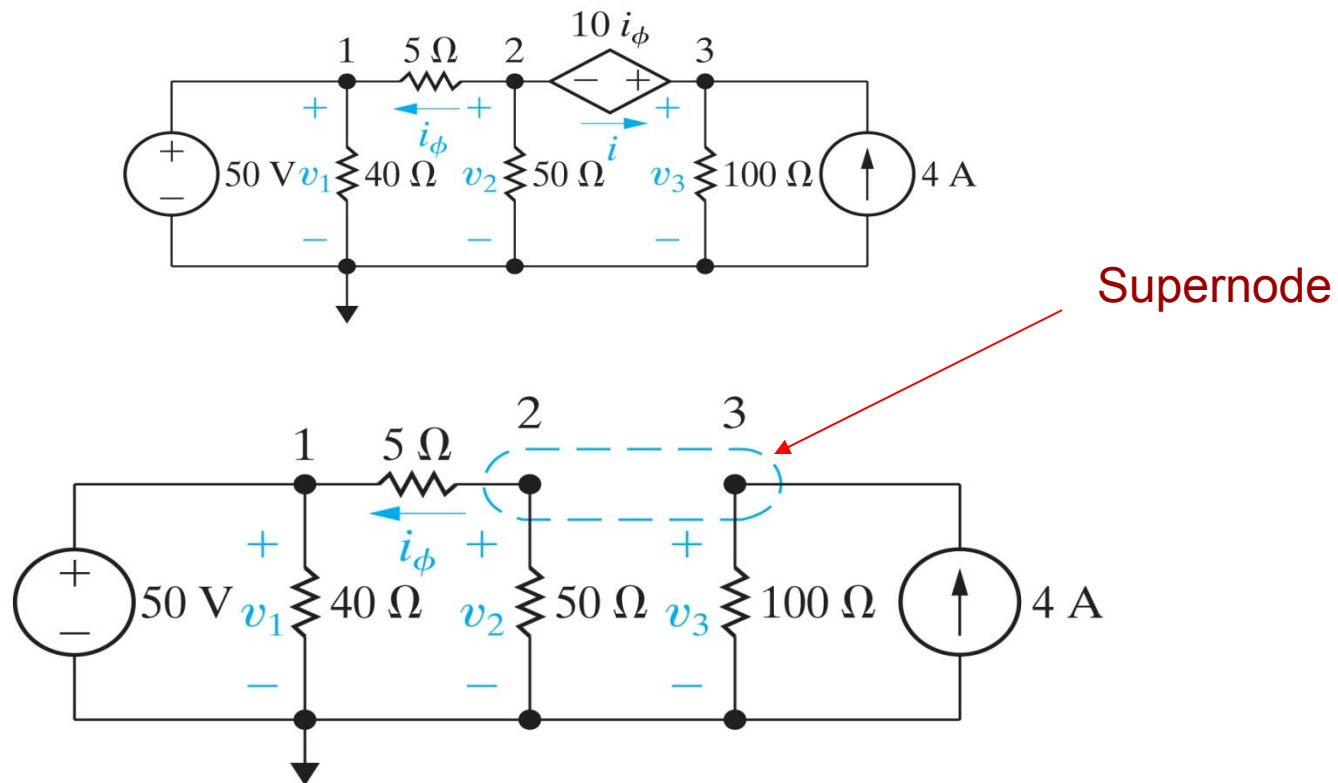
A supernode is two essential nodes connected by a voltage source --- and KCL holds for the composite supernode just like for a regular node ---- so we can write a single KCL equation for it.




Instead of writing equations for the current out of nodes 2 and 3 separately, we can write a single equation for the current out of the supernode as:

$$(v_2 - 50)/5 + v_2/50 + v_3/100 - 4 = 0$$

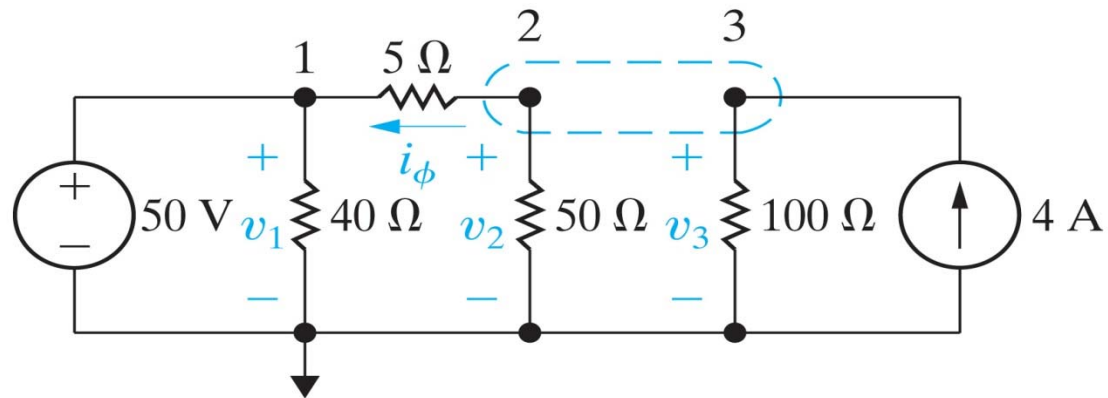Then we proceed as before to solve the circuit




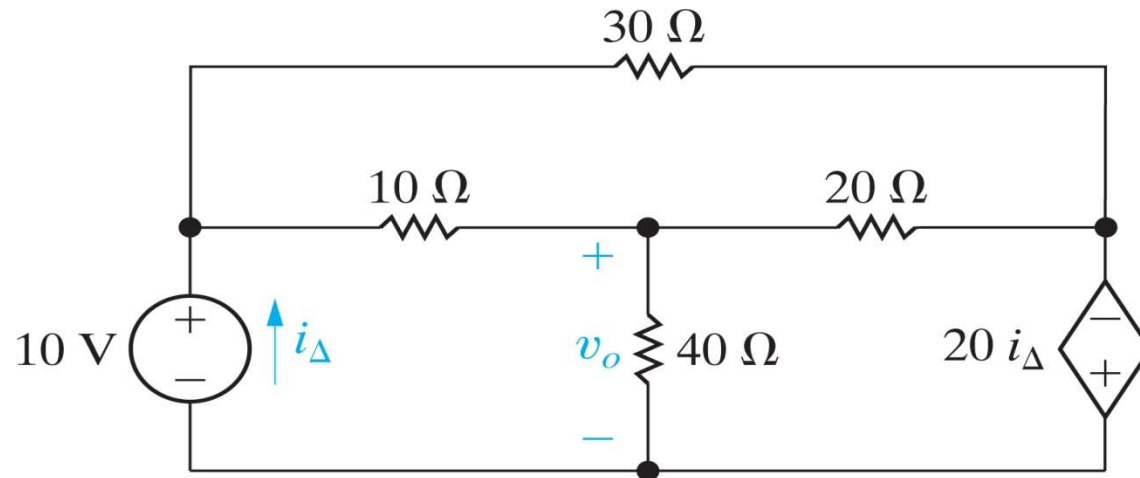Here's another circuit to analyze – find the voltage,  $v_o$  and the current,  $i_\Delta$



How many essential nodes are there? Which one is a good choice for a reference node? Does any pair of essential nodes qualify as a supernode?

How about this node?

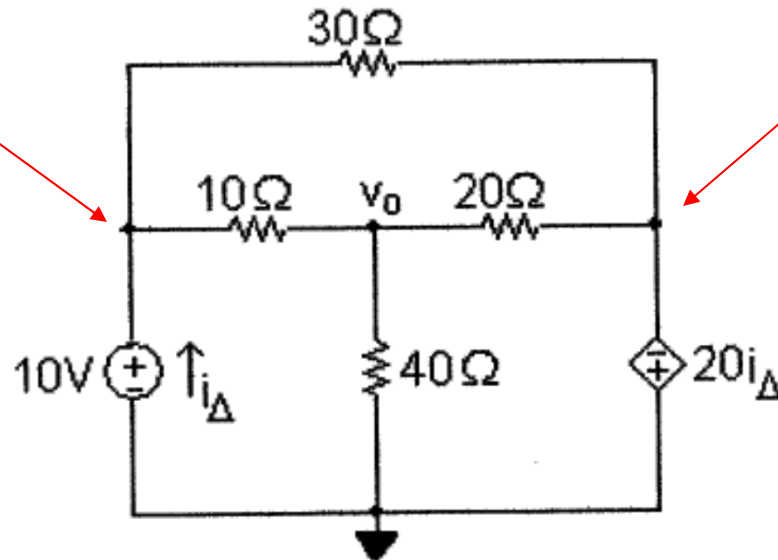

How about this node?

There is only one (useful) essential node (other than the reference node)....and we can write the node voltage equation for it:

$$\frac{v_o}{40} + \frac{v_o - 10}{10} + \frac{v_o + 20i_{\Delta}}{20} = 0$$

Why the plus sign?

We've got two unknowns ...we need another equation involving  $i_{\Delta}$


We can write for the constraint equation on  $i_\Delta$ :

$$i_\Delta = (10 - v_0)/10 + (10 + 20 i_\Delta)/30$$

So we have two equations in  $v_0$  and  $i_\Delta$ :

$$v_o \left( \frac{1}{40} + \frac{1}{10} + \frac{1}{20} \right) + i_\Delta (1) = 1$$

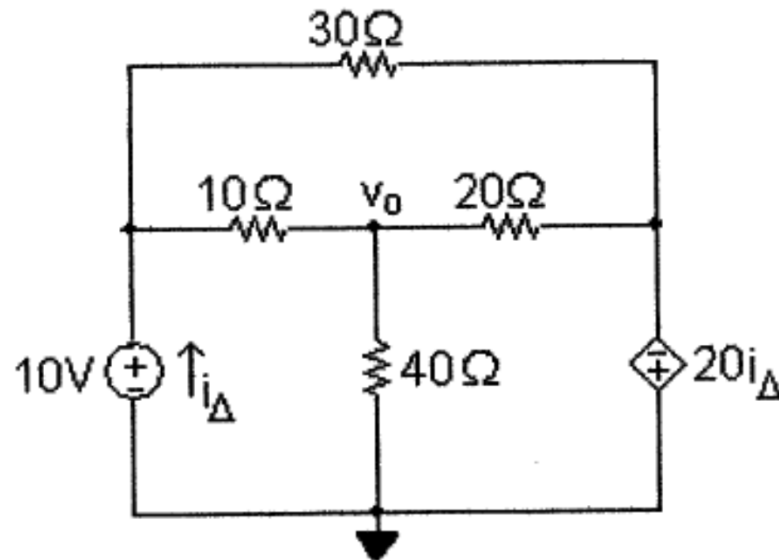
$$v_o \left( \frac{1}{10} \right) + i_\Delta \left( 1 - \frac{20}{30} \right) = 1 + \frac{10}{30}$$



Which we can solve:

$$i_{\Delta} = -3.2\text{A and } v_0 = 24\text{ V}$$

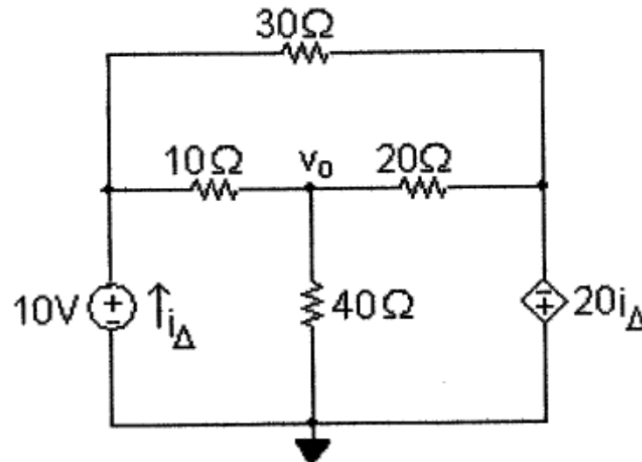Let's check the results - the current ( $i_{\Delta}$ ) through the  $10\Omega$  resistor from the  $10\text{V}$  source is  $(10 - 24)/10 = -1.4\text{A}$  and through the  $30\Omega$  resistor is  $(10 - 3.2 \cdot 20)/30 = -1.8\text{A}$ , so the sum is  $-3.2\text{ A}$





## Attributes of Supernodes

- At a supernode, Kirchoff's current law (KCL) can be applied to the combination of the two nodes as if it were a single node.
- KVL is used to express the voltage difference between the two nodes in terms of the voltage source between them
- If a supernode contains a resistor in parallel with the voltage source – as usual – the resistor can be removed since it will have no impact on other parts of the circuit as we discussed earlier.
- For a quasi-supernode (a supernode where one of the nodes is the reference node) the node voltage of the non reference node is equal to the voltage magnitude of the source.

