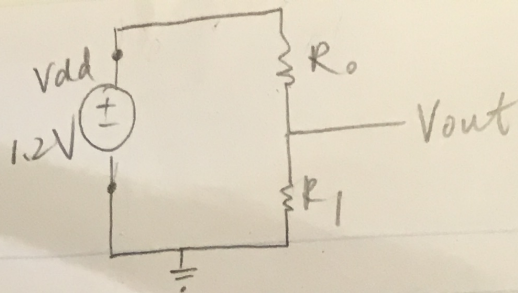


$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$



(1)

i. (a) if  $R_1 \ll R_0$ ,  $R_1 = 10\Omega$ ,  $R_0 = 1k\Omega$



$$V_{out} = V_{in} \cdot \frac{R_1}{R_1 + R_0} = 1.2V \cdot \frac{10\Omega}{10\Omega + 1k\Omega} = 1.2 \cdot \frac{10}{1010} = 0.01188V \approx (0)$$

(b) if  $R_1 \gg R_0$ ,  $R_1 = 10M\Omega$ ,  $R_0 = 1k\Omega$


$$V_{out} = V_{in} \cdot \frac{R_1}{R_1 + R_0} = 1.2V \cdot \frac{10,000,000\Omega}{1,001,000\Omega} = 1.1988V (\approx V_{in})$$

ii (a)

iii (b)

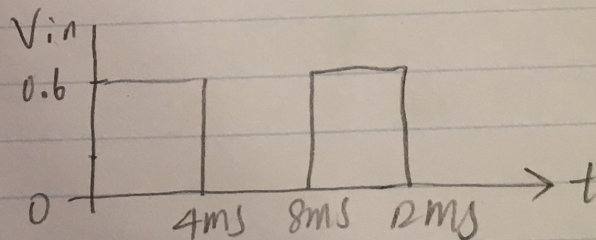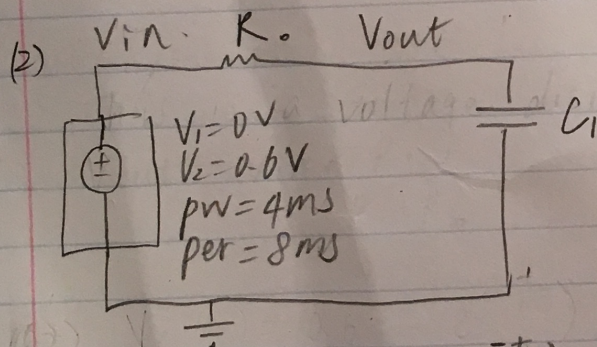

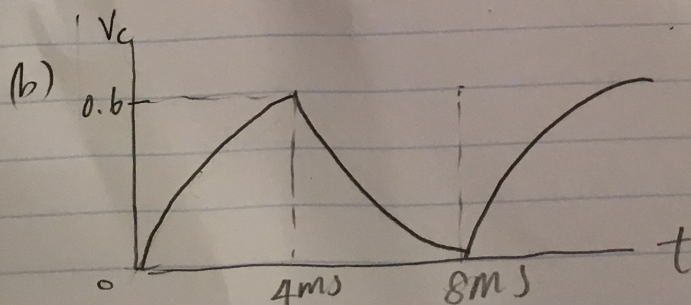(a)  $V_C(t) = 0.6(1 - e^{-\frac{t}{RC}})$



(c) final result for  $V_C(t)$  is  $V_{in} = 0.6V$

(d)  $\tau = RC = 1k\Omega \cdot 1\mu F = 0.001s = 1ms$