


ELEN 50: Mid-term #1 Review

S. Hudgens

now..... a quick review before the mid-term

Topics that will appear in mid-term problems may include:

Sorry – no Wye to
Delta problems on
exam

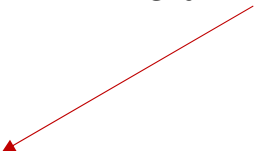


1. Kirchoff's Laws and Ohm's Law
2. Equivalent circuits (series, parallel, and wye to delta)
3. Source transforms
4. Node Voltage Analysis (including supernodes and quasi-supernodes)
5. Thevenin and Norton Equivalent Circuits
6. Max Power Transfer

The exam will be 1 hour long and have 5 problems – about the same difficulty or slightly less difficult than the homework problems.

The exam is open book, open notes, including access to Camino or the Design Center if you need it.


Passive Sign Convention

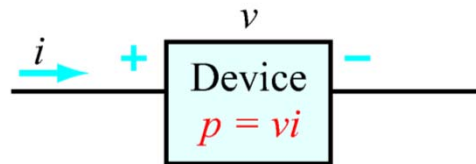

$p > 0$ power delivered to device

$p < 0$ power supplied by device

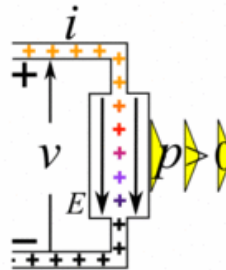
*Note that i direction is defined as entering (+) side of v .



Another way to say it:


If the device is a voltage source, then current comes out of the positive side ...if it's a resistor, then current goes into the positive side.

Review of KCL and KVL

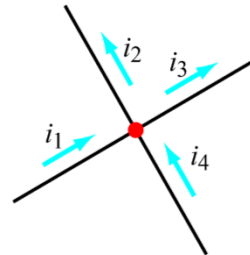

$$i_1 + i_4 = i_2 + i_3$$

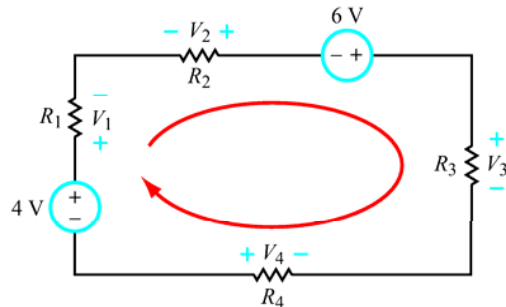
Kirchhoff Current Law (KCL) – the total current entering a node must be equal to the total current leaving a node ...i.e. charge doesn't “build up” at a node. **The sign convention is that current leaving a node is considered positive.**



$$-4 + V_1 - V_2 - 6 + V_3 - V_4 = 0$$


Kirchhoff Voltage Law (KVL) – the algebraic sum of the voltage drops around a closed loop is zero. **The sign convention is that the voltage drop on an element appears with the sign first encountered by the arrow on the loop.**

Equivalent Circuits

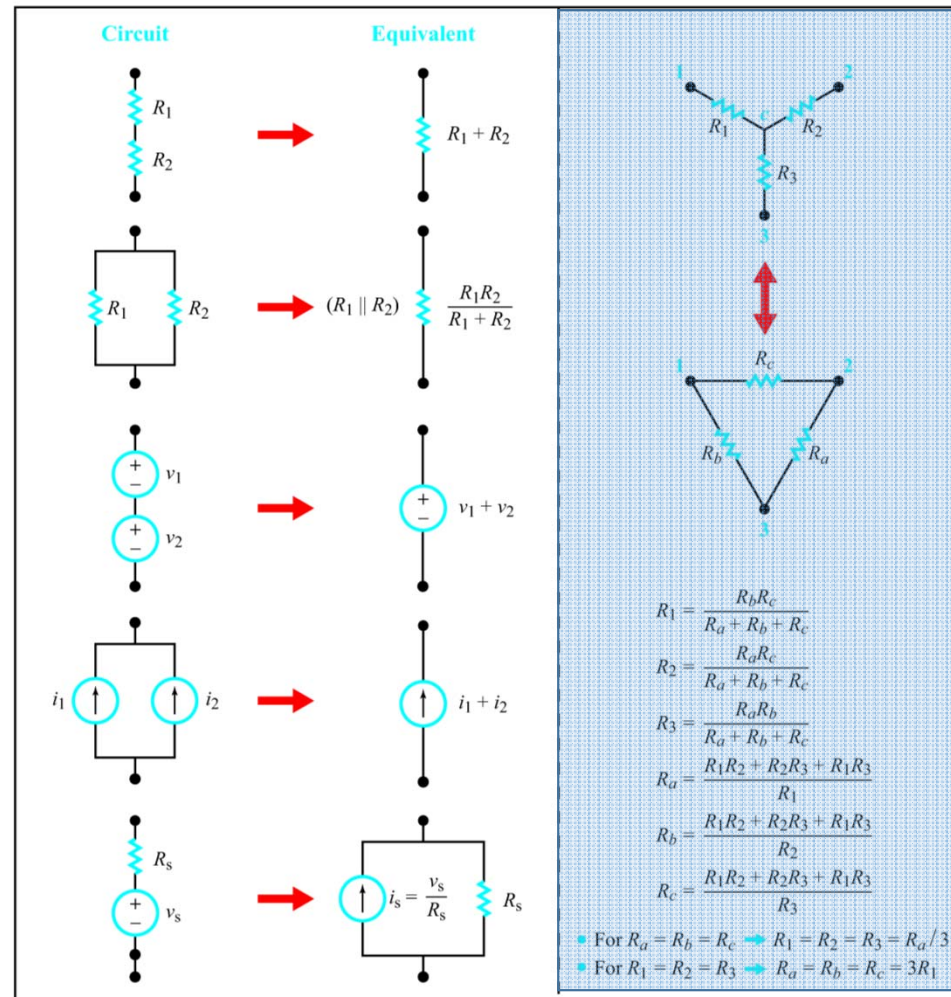


Won't be on exam

The Wheatstone Bridge

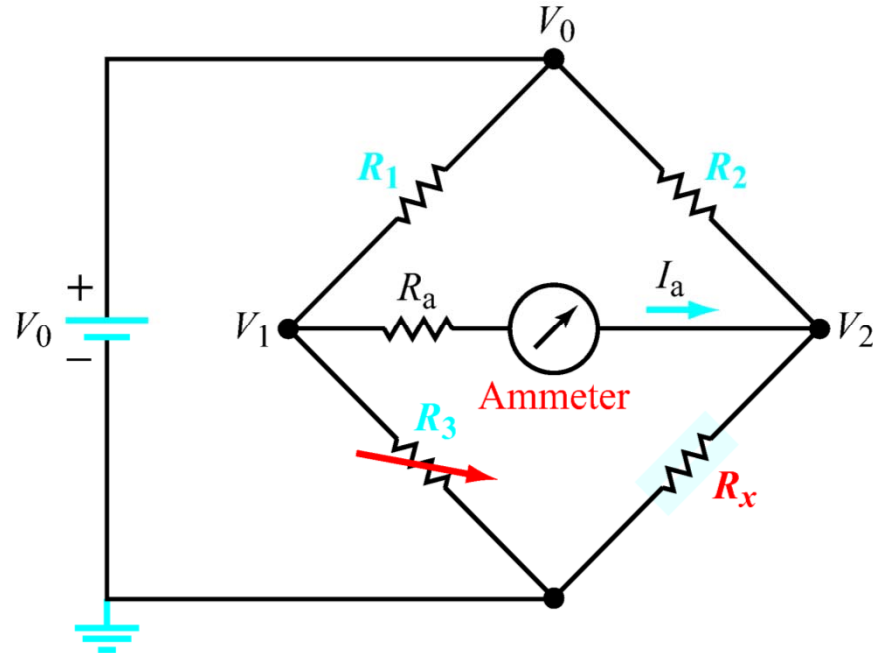

R_1 and R_2 are known, fixed resistors, R_3 is a (known) adjustable resistor, and R_x is the unknown resistor. V_0 is any convenient voltage source. R_3 is adjusted until I_a is zero – the bridge is in balance. You can solve this without using a Wye to Delta transform ...do you see why?

Balanced Bridge

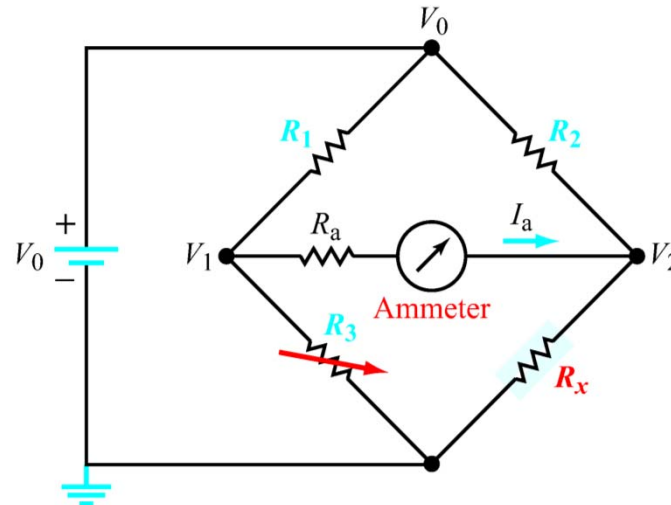

In balance, $V_1 = V_2$, so, since:

$$V_1 = R_3 V_0 / (R_1 + R_3)$$

$$V_2 = R_x V_0 / (R_2 + R_x)$$

Both sides are
voltage dividers!

$$\frac{R_3 V_0}{R_1 + R_3} = \frac{R_x V_0}{R_2 + R_x}$$



Also, since the voltages across R_1 and R_2 are equal at balance:

$$\frac{R_1 V_0}{R_1 + R_3} = \frac{R_2 V_0}{R_2 + R_x}$$


So, dividing these equations:

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}$$

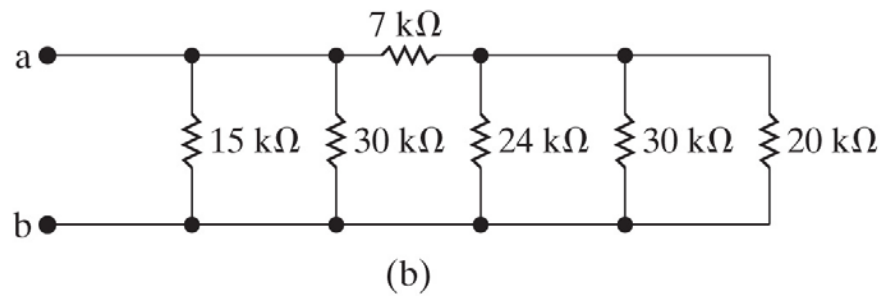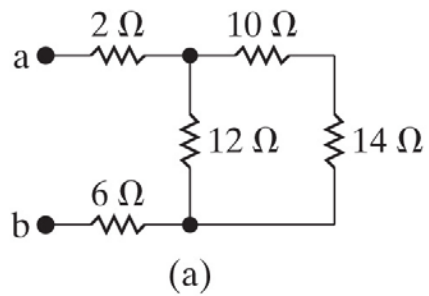Find the equivalent resistance R_{ab} for each of these circuits:



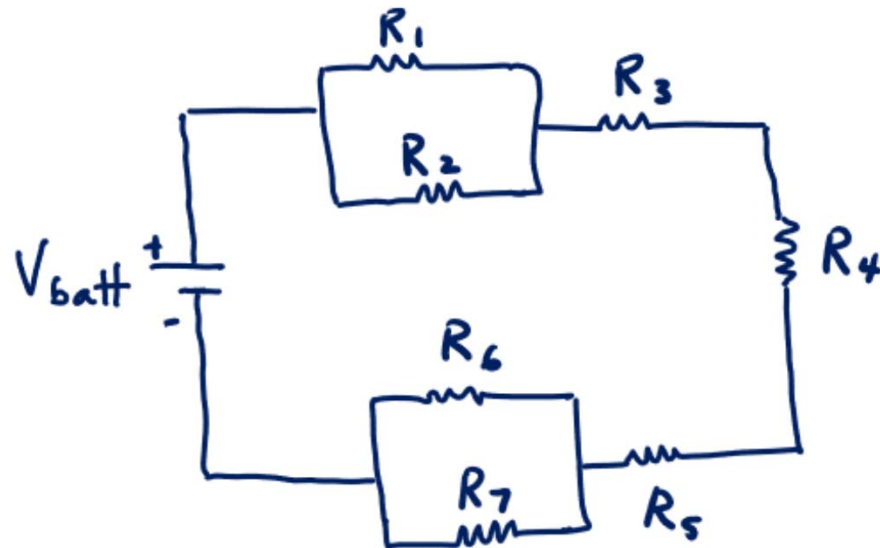
Is it clear which of these circuit elements are in series and which are in parallel?



How would you replace all these resistors with a single, equivalent resistor? Which resistors are in parallel and which are in series?

Another important kind of circuit simplification is a Source Transform

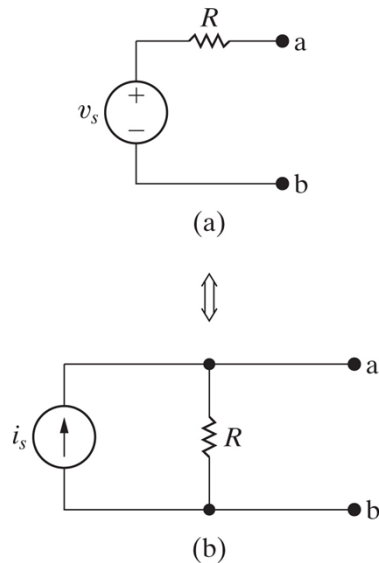A source transform allows a voltage source in series with a resistor to be transformed into a current source in parallel with a resistor. This can be very useful in simplifying a circuit prior to doing a circuit analysis.




these two circuits are equivalent, if:

$$i_s = v_s/R$$

You can show this relationship by attaching a load resistor to a and b and calculating the current flowing

Formal Methods of Circuit Analysis

Not on this
mid-term

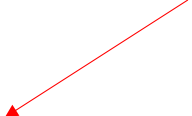

Node Voltage Method


- Identify essential nodes
- Select reference node
- Label voltages at remaining essential nodes (v_1, v_2, \dots, v_n)
- Write equations for KCL at these nodes in terms of node voltages referenced to reference node.
- Solve n equations in n unknowns

Mesh Current Method

- Identify mesh currents
- no reference node needed since we're explicitly calculating currents and not voltages.
- Label mesh currents (i_a, i_b, \dots, i_n)
- Write equations for KVL around the mesh current paths.
- Solve n equations in n unknowns

Circuit Analysis with the Node Voltage Method

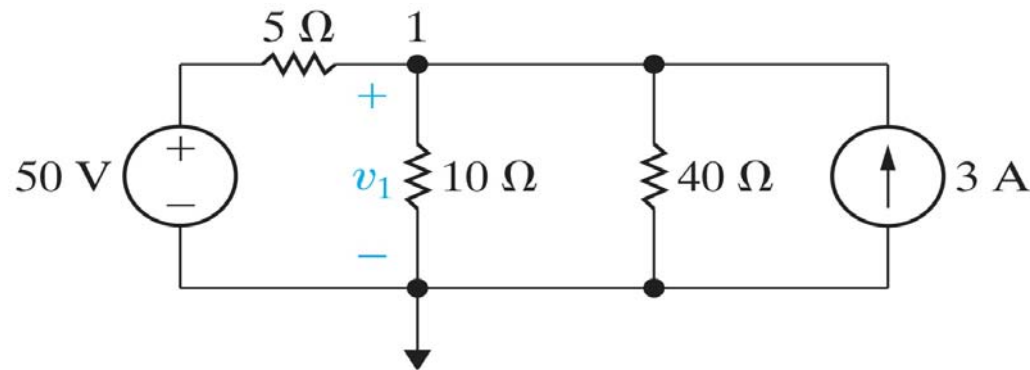
- Choose a reference node and label the other essential nodes
- Well...there is only one other essential node so we can solve this circuit with a single equation! How many terms will the equation have?




- Now we write the KCL for currents leaving the single essential node:
- If we assume that current is leaving the node through all the branches except the one with the current source:

$$(v_1 - 50)/5 + v_1/10 + v_1/40 - 3 = 0$$

$$\rightarrow v_1 = 40\text{V}$$

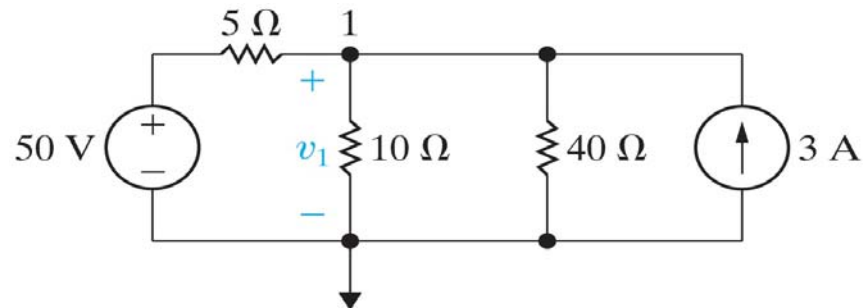

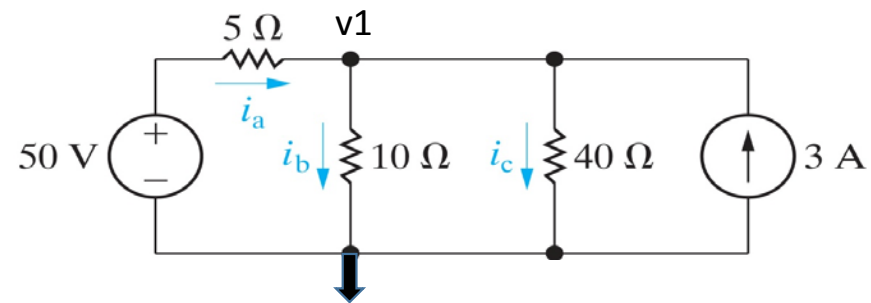If, instead, we had assumed that the branch currents were flowing as shown below:



The KCL equation would be:


$$-(50 - v_1)/5 + v_1/10 + v_1/40 - 3 = 0$$

$$(v_1 - 50)/5 + v_1/10 + v_1/40 - 3 = 0 \quad \text{the same as before!}$$

...and we get the same answer:


$$\rightarrow v_1 = 40\text{V}$$

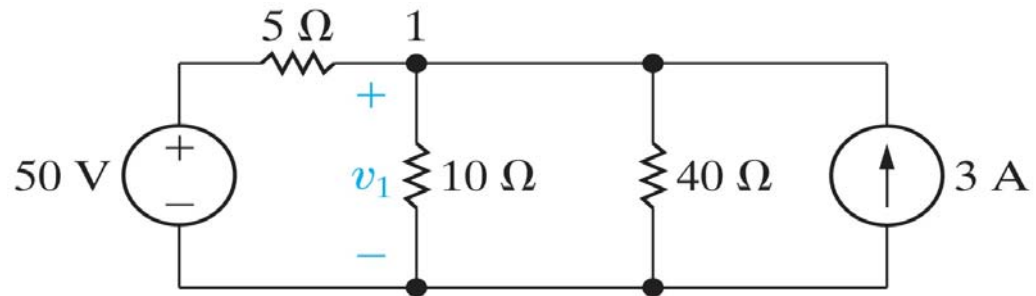What if you wanted to solve for v_1 using source transforms?




Would this be easier than a node voltage solution? Why?

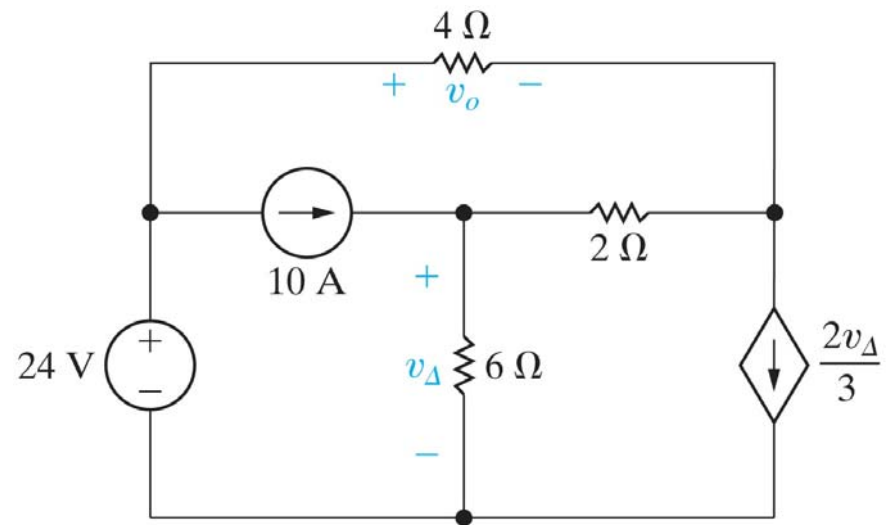
Dependent Sources: -- we want to know v_o using the node voltage method




We label the essential nodes and chose a reference node

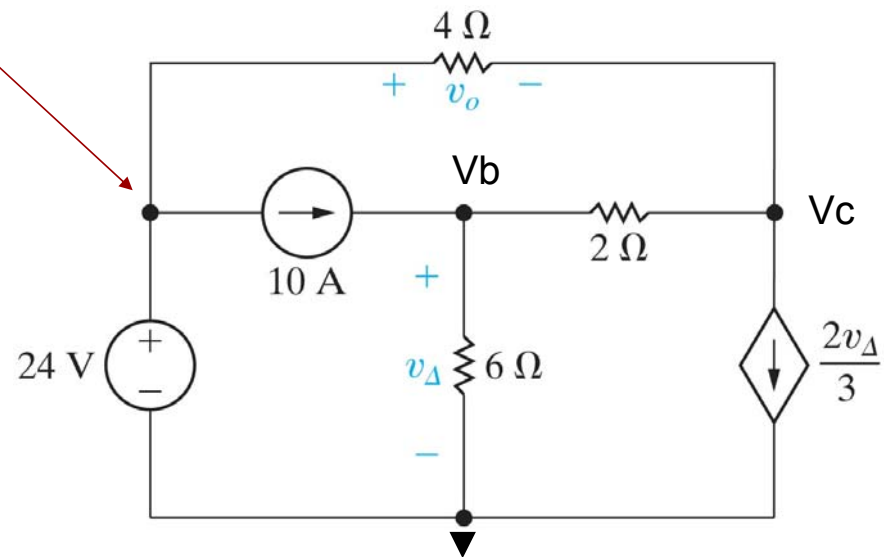We know
the voltage
at this
quasi-
supernode
by
inspection



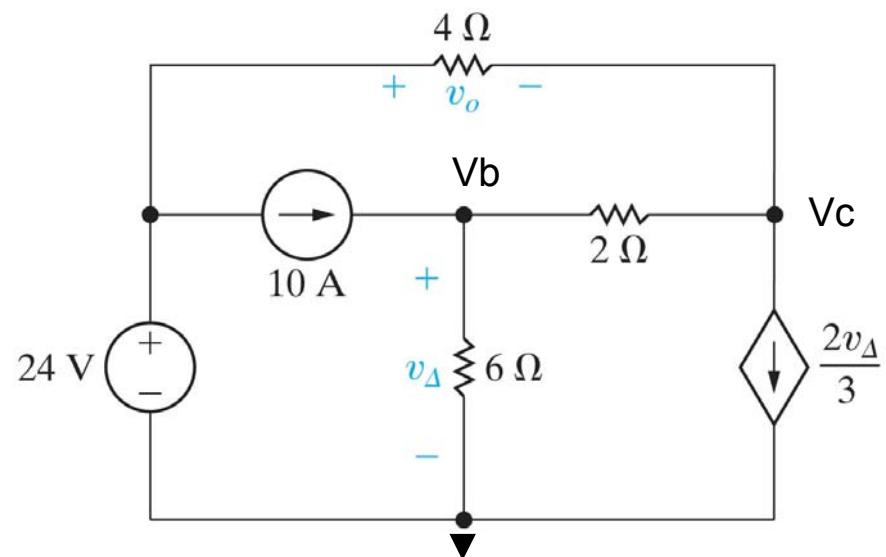

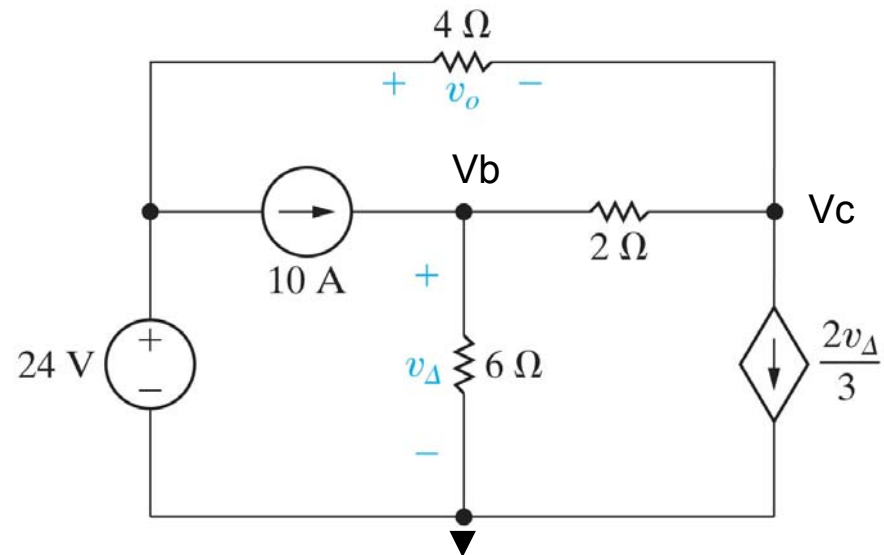
Write the node voltage equations at the two remaining essential nodes -- node b and node c



$$\begin{aligned} -10 + \frac{v_b}{6} + \frac{v_b - v_c}{2} &= 0 && \text{at node b} \\ \frac{2v_\Delta}{3} + \frac{v_c - v_b}{2} + \frac{v_c - 24}{4} &= 0 && \text{at node c} \end{aligned}$$

We need another equation involving v_Δ because we've got two equations in three unknowns – we always need constraint equations when using the node voltage method with dependent sources -- what is the third equation involving v_Δ , v_c and v_b ?

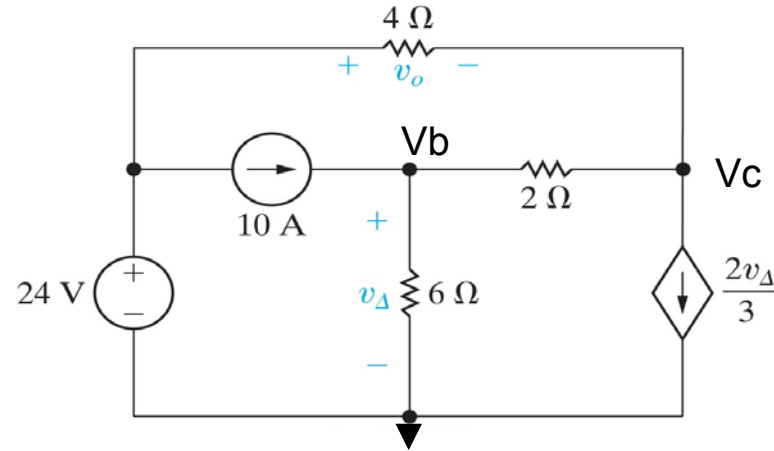Well ...the constraint equation here is trivial: $v_{\Delta} = V_b$



Putting the equations in standard form we could write (including the constraint equation):


$$v_b \left(\frac{1}{6} + \frac{1}{2} \right) + v_c \left(-\frac{1}{2} \right) + v_{\Delta}(0) = 10$$

$$v_b \left(-\frac{1}{2} \right) + v_c \left(\frac{1}{2} + \frac{1}{4} \right) + v_{\Delta} \left(\frac{2}{3} \right) = \frac{24}{4}$$

$$v_b(1) + v_c(0) + v_{\Delta}(-1) = 0$$

and solve a 3 X 3 matrix using MATLAB :

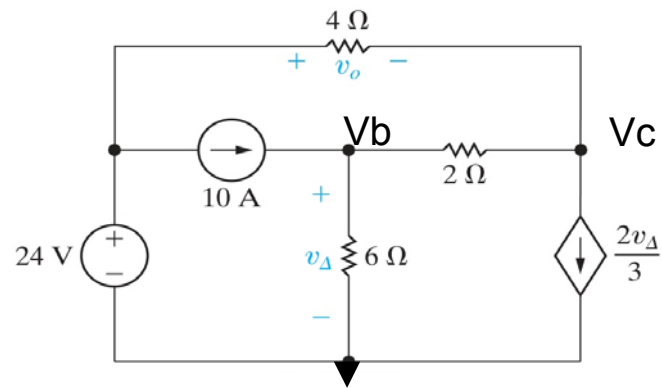orwe can use the constraint equation to eliminate v_{Δ} immediately by substitution (giving us two KCL equations at two nodes)



$$-10 + \frac{V_b}{6} + \frac{V_b - V_c}{2} = 0$$

$$\frac{2V_b}{3} + \frac{V_c - V_b}{2} + \frac{V_c - 24}{4} = 0$$

In standard form:

$$\begin{bmatrix} \left(\frac{1}{6} + \frac{1}{2}\right) & \left(-\frac{1}{2}\right) \\ \left(\frac{2}{3} - \frac{1}{2}\right) & \left(\frac{1}{2} + \frac{1}{4}\right) \end{bmatrix} \begin{bmatrix} v_b \\ v_c \end{bmatrix} = \begin{bmatrix} 10 \\ 6 \end{bmatrix}$$

And we can use MATLAB to solve thisor we can use substitution and just write:

$$4V_b - 3V_c = 60$$


$$2V_b + 9V_c = 72$$

multiplying the second eq. by 2 and subtracting

$$-21V_c = -84 \quad \text{so } V_c = 4, V_b = 18$$


We can solve:

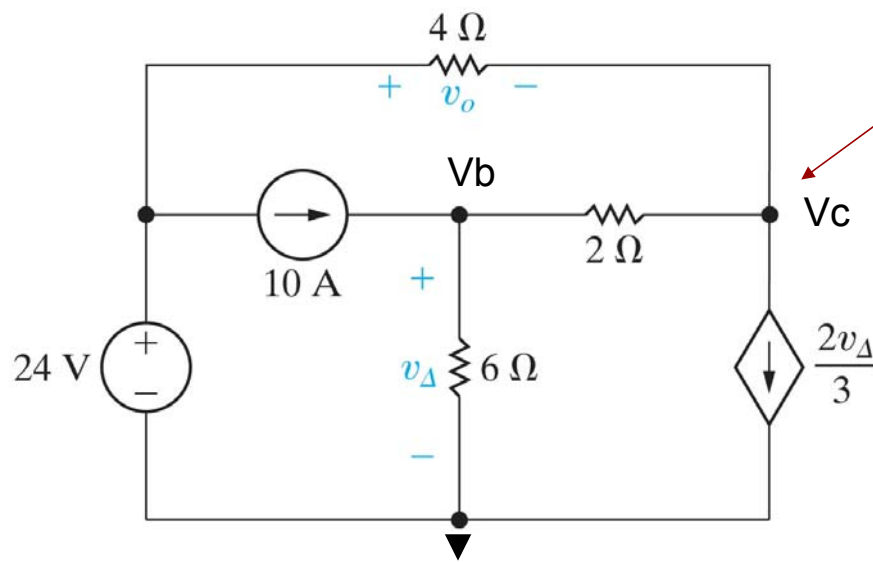$V_b = 18\text{V}$; $V_c = 4\text{V}$; $v_\Delta = 18$, so $v_0 = 24 - V_c = 20\text{V}$ and we're done!



why isn't this a quasi-supernode??

Nodes, Supernodes, and Quasi-Supernodes

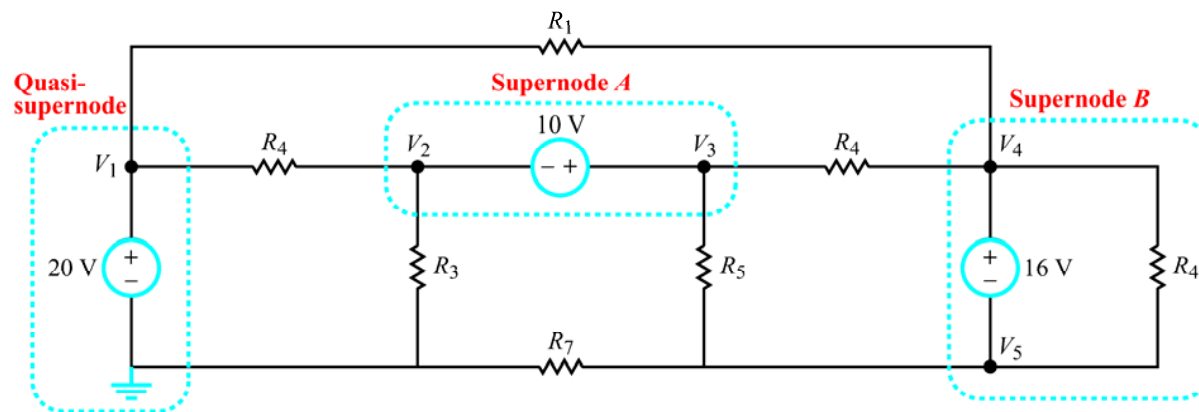

Here's an exercise from another textbook that we saw before ...apply the supernode concept to determine I in the circuit.



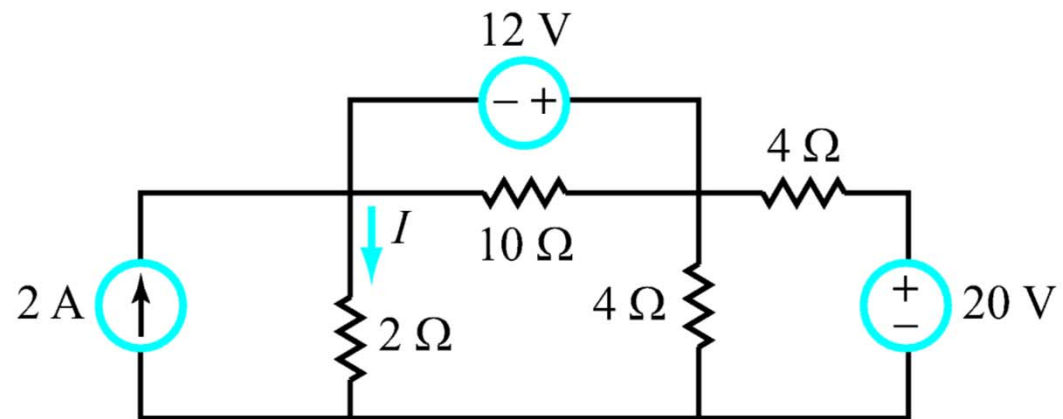


Figure E3.3

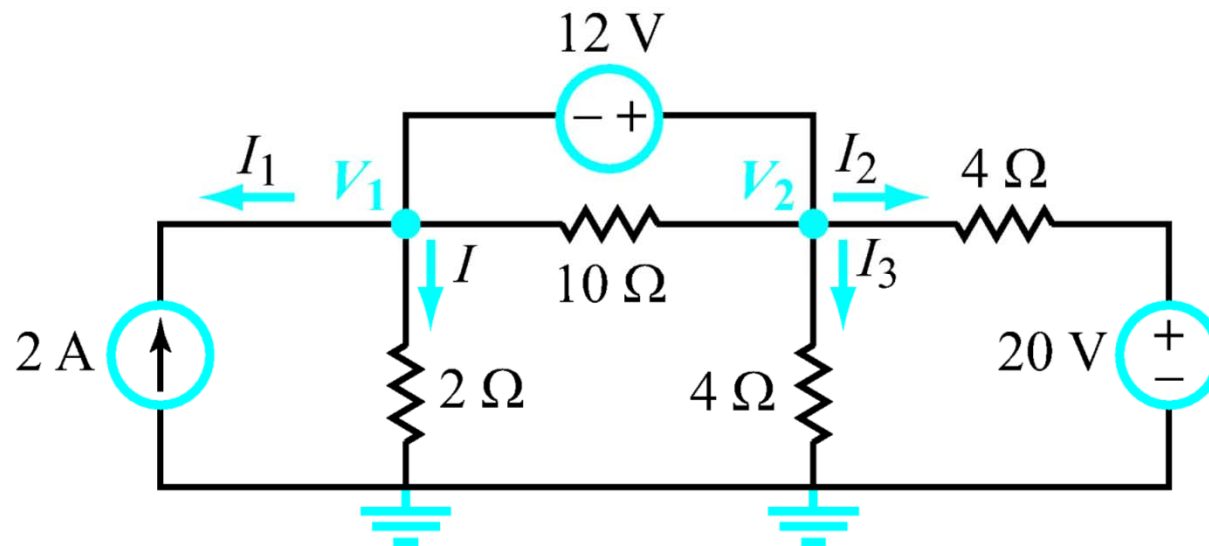Number essential nodes and chose a reference node. Is there a supernode in this circuit?



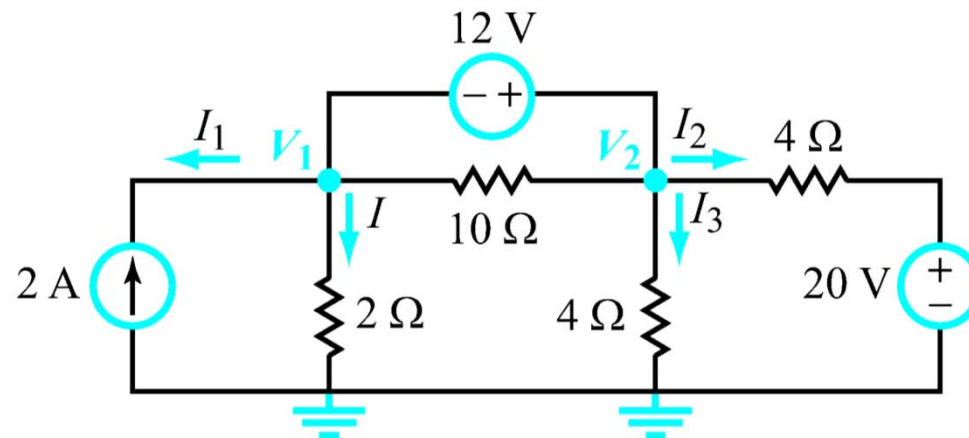


V_1 and V_2 form a supernode so we can write a single KCL equation for it:

$$I_1 + I + I_2 + I_3 = 0$$


$$I_1 = 2, I = V_1/2, I_3 = V_2/4, I_2 = (V_2 - 20)/4 \text{ and KVL gives us } V_2 - V_1 = 12$$

So, solving for V_1 and substituting:

$$I = 0.5\text{A}, V_1 = 1, V_2 = 13$$

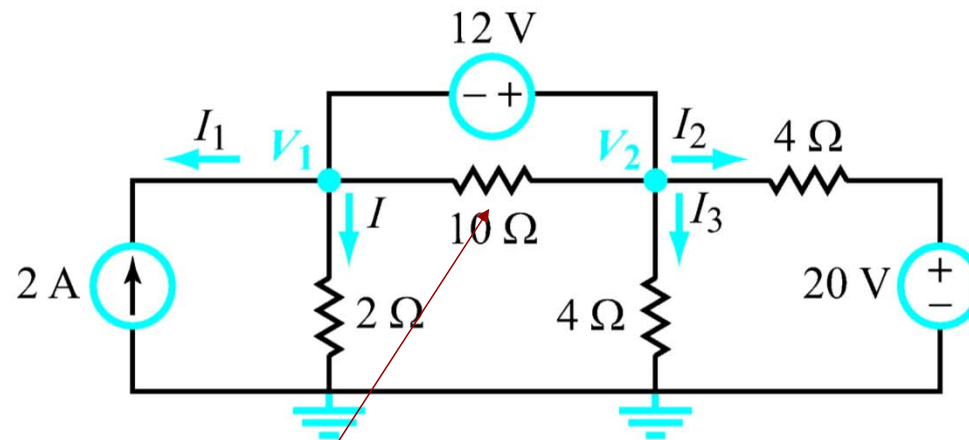


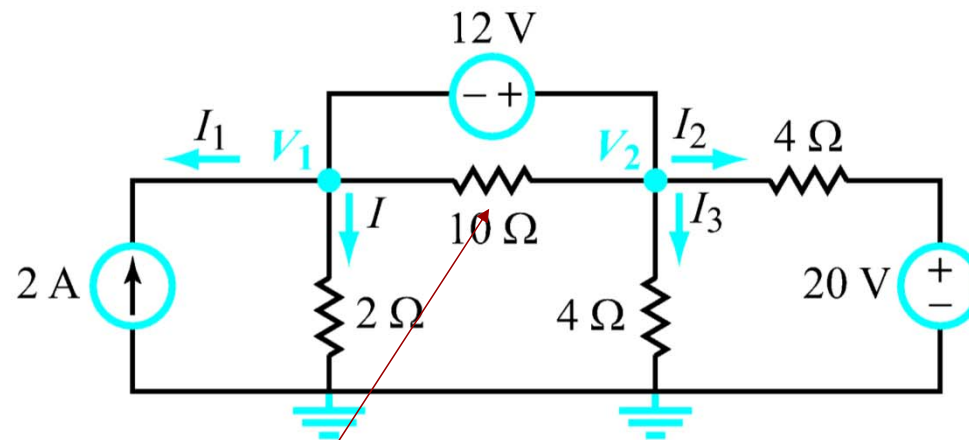How about the current through this resistor – we didn't account for it in any of the calculations? Does the behavior of this circuit depend on the value of this resistor?




This is one of these “superfluous resistors” we’ve talked about before... it’s a resistor in parallel with a voltage source that can be removed from a circuit without affecting anything. Another way to look at it -- if we had included it in the supernode equation it would have added one current term to the v_1 part of the equation and the negative of the same current term to the v_2 part of the equationcancelling each other out.

Here's another node voltage problem

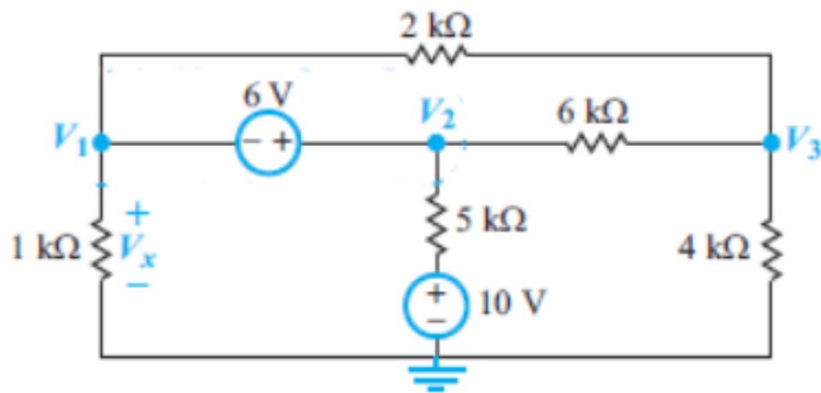

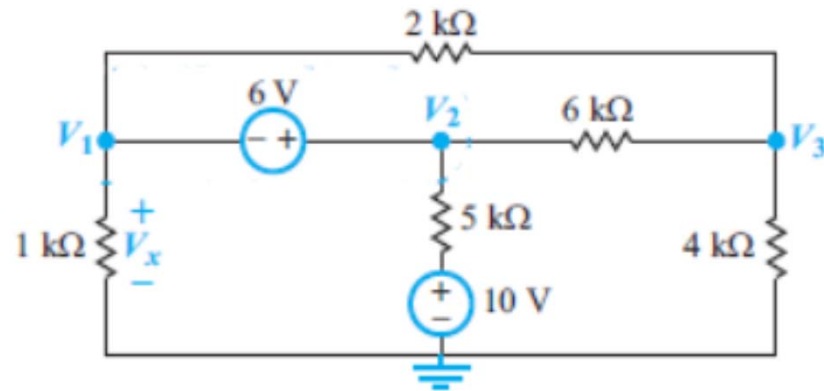What is V_x ...the voltage drop across the 1K resistor?



For V1 and V2 of the supernode:
$$\frac{V_1}{10^3} + \frac{V_1 - V_3}{2 \times 10^3} + \frac{V_2 - 10}{5 \times 10^3} + \frac{V_2 - V_3}{6 \times 10^3} = 0$$

And for V3:
$$\frac{V_3 - V_1}{2 \times 10^3} + \frac{V_3 - V_2}{6 \times 10^3} + \frac{V_3}{4 \times 10^3} = 0.$$

Also ...there is the auxiliary equation: $V_2 - V_1 = 6$

MATLAB gives:

$$V_1 = 0.38\text{V}$$


$$V_2 = 6.38\text{V}$$

$$V_3 = 1.37\text{V}$$

$$\text{So } V_x = V_1 = 0.38\text{V}$$

Thevenin Equivalent Circuit

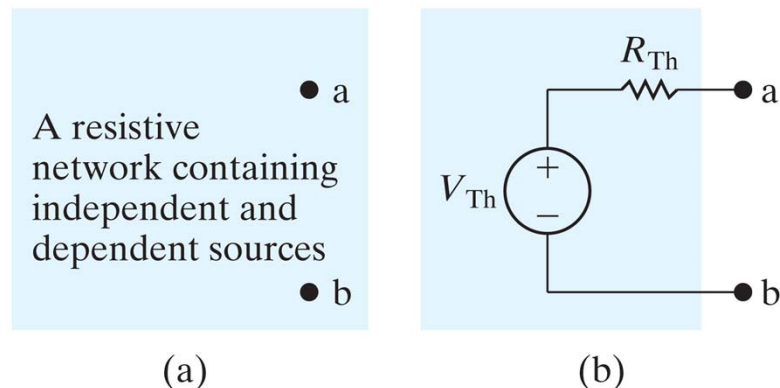Thevenin (and Norton) equivalent circuits are ways of replacing complicated and/or irrelevant parts of a circuit with a simple circuit based on the behavior of the circuit at a particular pair of terminals using source transformations.








The Thevenin equivalent circuit for a resistive network is a voltage source, V_{th} , in series with a resistor, R_{th} . We chose these values by measuring the open circuit voltage for the network ...this is V_{th} ...then we measure the short circuit current out of the network. Since this will be V_{th}/R_{th} , the value of R_{th} is: $R_{th} = V_{th}/i_{sc}$. The Norton equivalent is just the source transform of the Thevenin circuit into a current source in parallel with a resistor.

Thevenin Equivalent Circuit – General Calculation Strategy


- **Obtain v_{th}** by calculating the voltage across the two specified terminals when no load is present (open circuit voltage)
- **Obtain R_{th}** by either:
 - Calculating the current that will flow between the specified terminals in a short circuit. R_{th} is obtained from $R_{th} = v_{th}/I_{sc}$ **OR**
 - If the circuit doesn't contain dependent sources, you can calculate the equivalent resistance between the specified terminals after all independent voltage sources are deactivated (replaced with short circuits) and all independent current sources are deactivated (replaced with open circuits). The equivalent resistance is R_{th} , the Thevenin resistance. **OR**
 - If the circuit contains independent and dependent sources, R_{th} can be determined by deactivating independent sources, and adding an external source (v_{ex} or i_{ex})...then solve the circuit to determine the current i_{ex} or voltage v_{ex} supplied by the external source. $R_{th} = v_{ex}/i_{ex}$

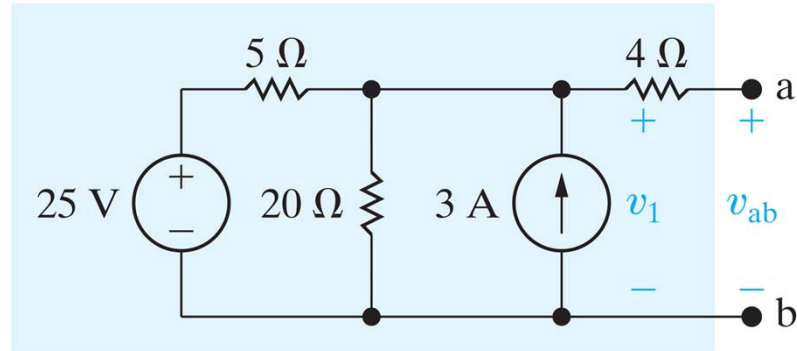Sometimes it will be possible to obtain a Thevenin equivalent circuit simply by doing a series of source transforms. For example – what is the Thevenin equivalent circuit at terminals a and b?



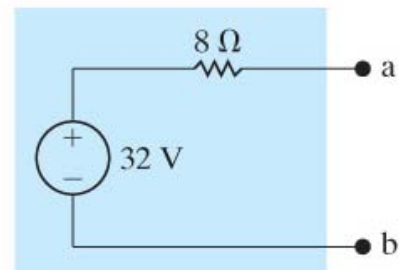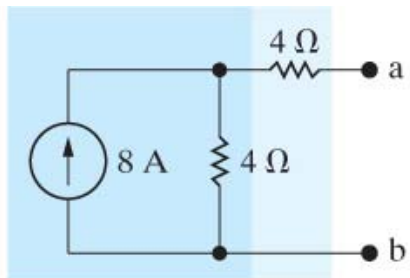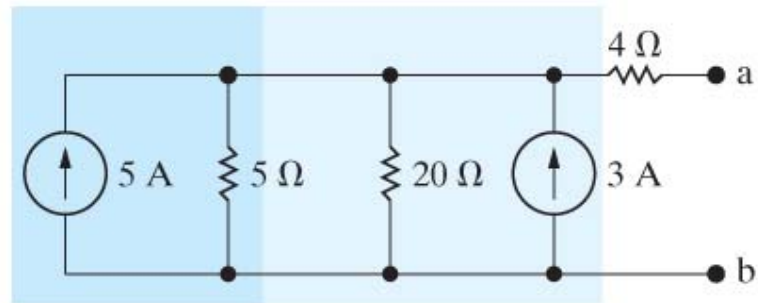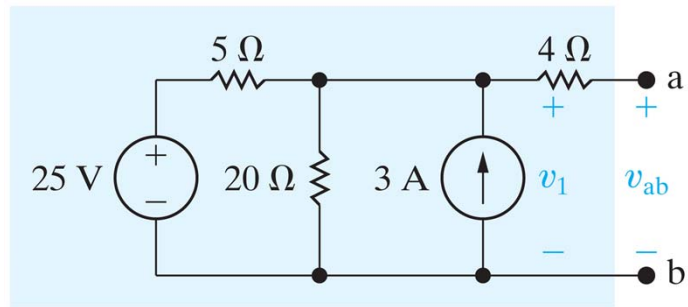

The
Thevenin
equivalent!

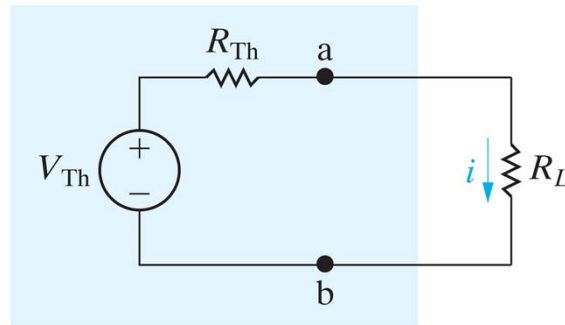


power transfer is maximum when the load resistance, $R_L = R_{Th}$

and we can determine the value of the maximum power by substituting into:


$$p = i^2 R_L = (V_{Th} / [R_{Th} + R_L])^2 R_L$$

$$p_{\max} = V_{Th}^2 / 4R_L$$

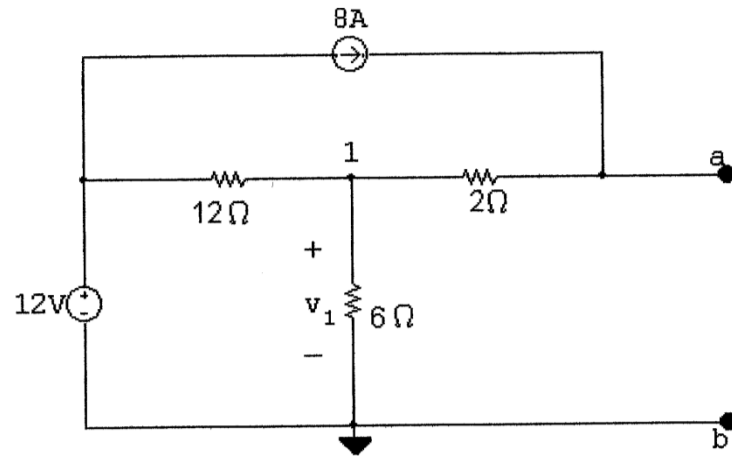Notice: if the problem asks only for the load resistance that will transfer maximum power – you need to calculate R_{Th} only – not V_{Th} also.



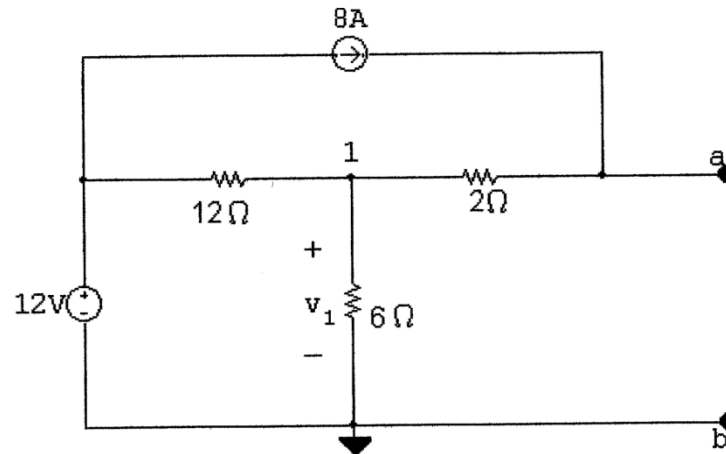What load resistor at terminals a and b will result in maximum power transfer to the load? What will that power be?



We can get R_{th} by method # 2 – deactivating the sources and combining resistances.

$$R_{Th} = 2 + \frac{(12)(6)}{18} = 6 \Omega$$

We can calculate v_1 using node voltage analysis....and V_{th} is v_1 plus the voltage drop across the 2Ω resistor.


$$\frac{v_1 - 12}{12} + \frac{v_1}{6} - 8 = 0$$

$$v_1 = 36 \text{ V}$$

$$\text{So } p_{\max} = (52)^2 / 4 * 6 = 112.67 \text{ W}$$

$$v_{Th} = v_1 + (2)(8) = 52 \text{ V}$$

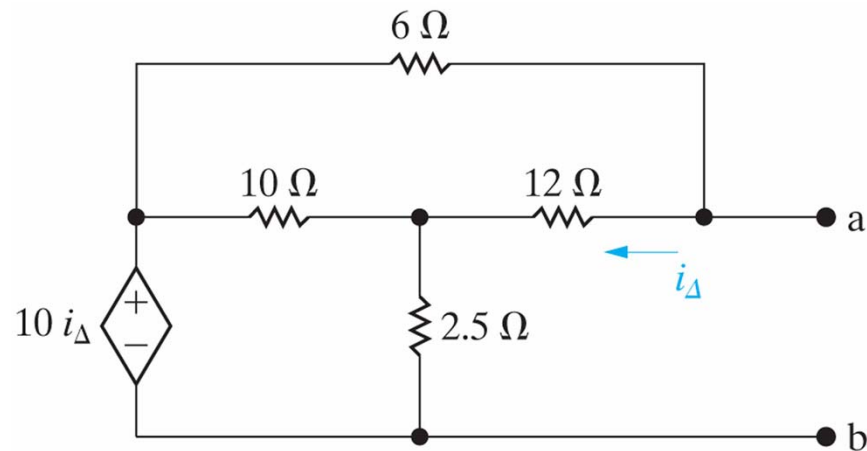Same questionwhat load resistor at terminals a and b will result in maximum power transfer to the load? What will that power be? Notice – this circuit has only a dependent source! What does this tell you about V_{th} ? What does this tell you about methods for calculating R_{th} ?




Well.....if you remembered that circuits with only dependent sources have $V_{th} = 0$..
..and you also remembered that:

$$P_{max} = (V_{th})^2 / 4R_{th}$$


then you'd know that the maximum power transferred to the load resistor would have to be zero!

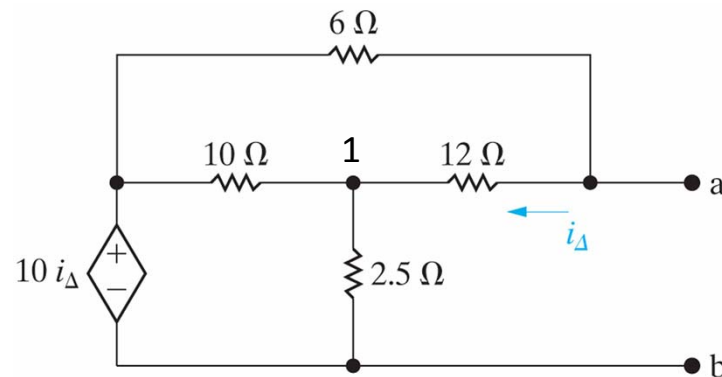But, if you had forgotten this ...you can always solve for V_{th} and R_{th} . To get V_{th} we calculate the open circuit voltage at terminals a and b. We get this by solving the single node voltage equation at node 1.



$$\frac{v_1 - 10i_{\Delta}}{10} + \frac{v_1}{2.5} - i_{\Delta} = 0$$

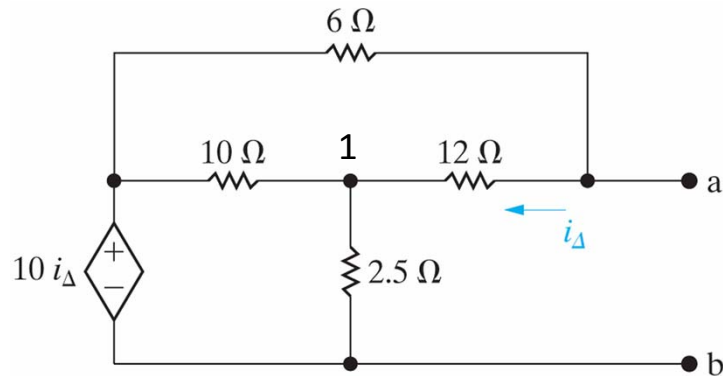We also see there is another relationship between v_1 and i_Δ because of the voltage divider created by the 6Ω , 12Ω and 25Ω resistor across the dependent voltage source.





So:
$$v_1 = 10i_\Delta \frac{25}{6+12+25} = 12.195i_\Delta$$

From the first KCL equation:
$$\frac{v_1 - 10i_\Delta}{10} + \frac{v_1}{2.5} - i_\Delta = 0 \quad \text{so} \quad v_1 = 3.64i_\Delta$$

The value of i_Δ that satisfies both equations is zero...so $10i_\Delta = 0$ and $V_{th} = 0$ and since $P_{max} = (V_{th})^2 / 4R_{th}$ the maximum power transferred is also zero.

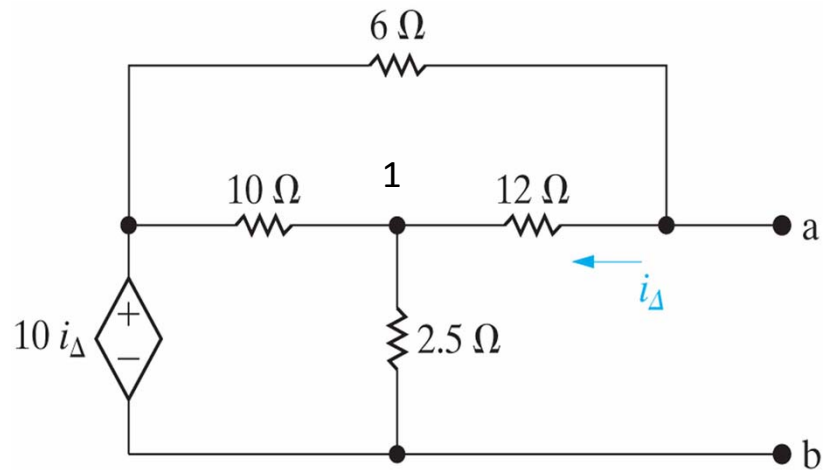What if, instead of maximum power, the problem asked you to determine the Thevenin equivalent circuit for this thing. You already know $V_{th} = 0$...how would you calculate R_{th} for the Thevenin equivalent? Which method would you use?




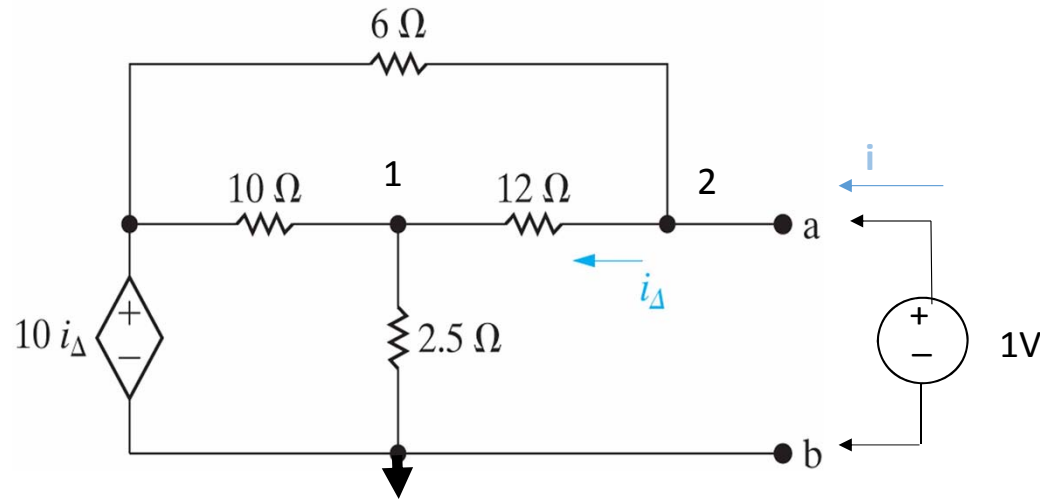


We'll use method #3 ...and attach a test voltage source – here we've chosen it to be 1V. We want to calculate the current, i , flowing out of the test source ...since we know from Ohm's law that the resistance from a to b will be the test voltage, 1V, divided by the current, i . If there were any independent sources in the circuit, we would deactivate them ...but we leave dependent sources alone.

I'll leave the algebra to you. You'll have to solve one KCL equation at node 1 since node 2 will be a quasi-supernode (because of the 1V source) and the other node is also a quasi-supernode.

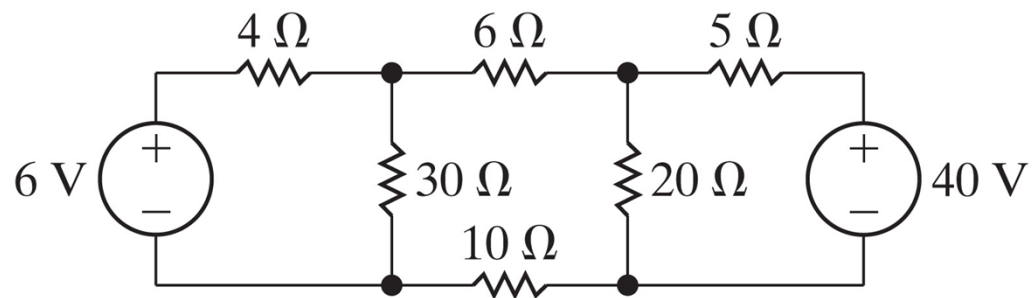We want to find the power (absorbed or supplied) by the 6V source




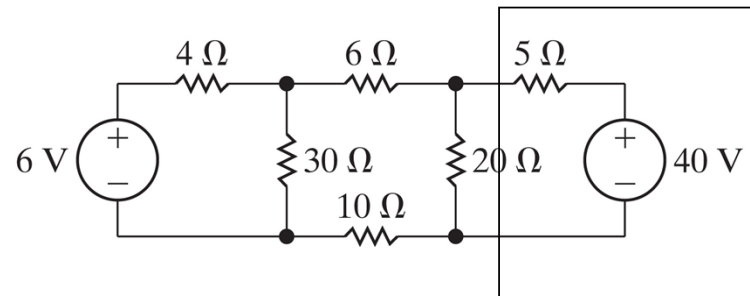Since we only care about the current flowing into or out of the 6V source, probably the easiest way to solve this circuit is through source transforms on the 40V source – leaving the 6V source alone.




Remember


$$i_s = v_s / R$$

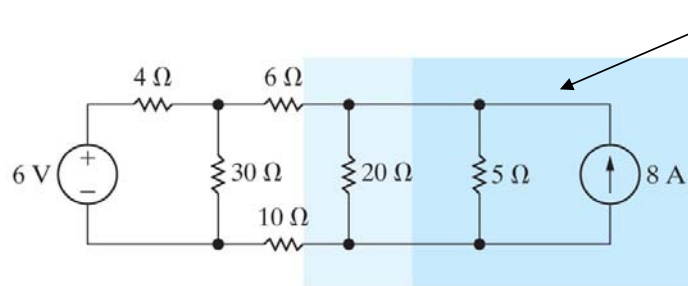


(a) First step

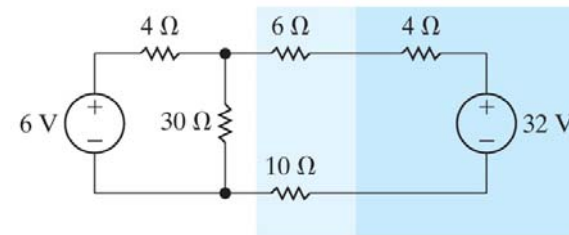

(b) Second step

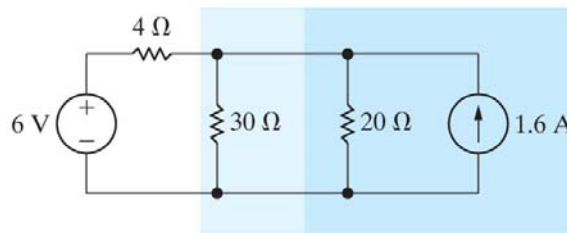

(c) Third step

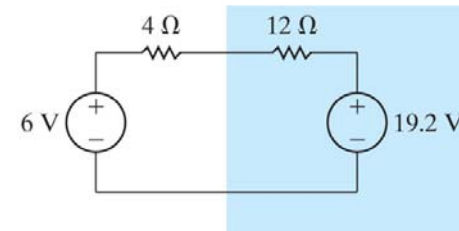


(d) Fourth step


Now it's trivially easy to determine the current through the 6V source – it's $(19.2 - 6)/16 = 0.825\text{A}$

flowing backwards through the voltage source so the source absorbs 4.95 W

Find v_o using Node Voltage Method

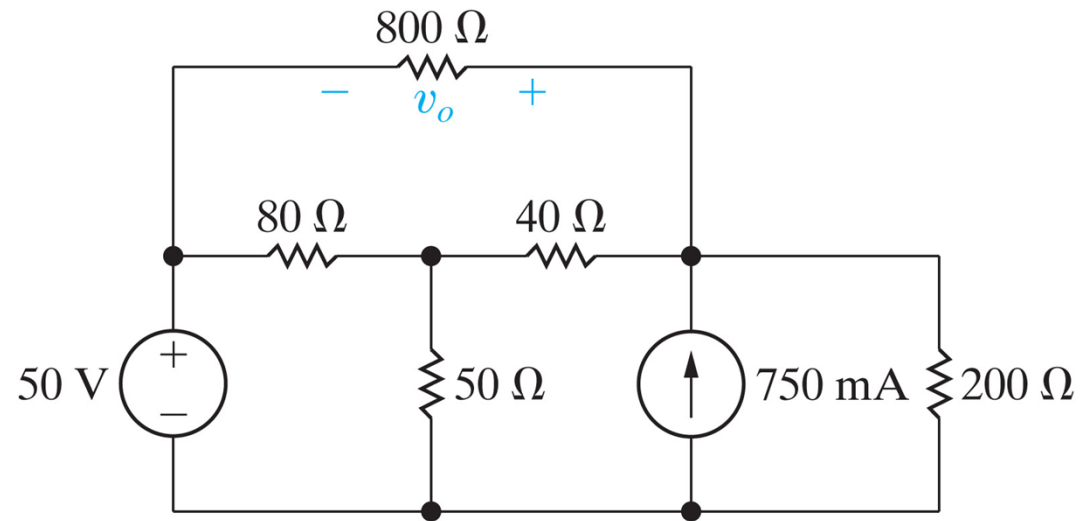

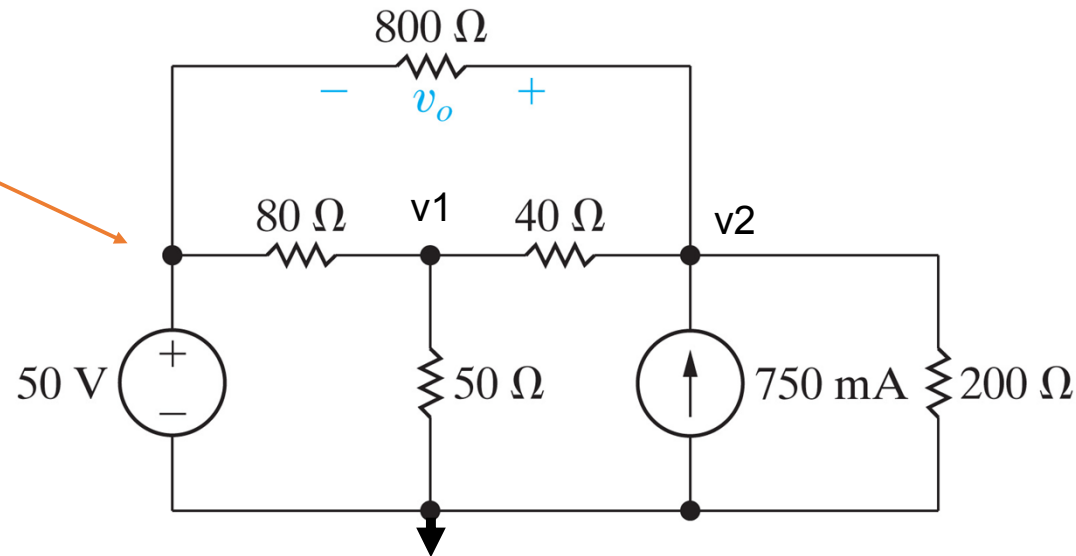Why only two node voltage equations? Why are we ignoring this node?



Number the nodes, pick a reference node, and write the KCL equations at the two remaining essential nodes.

$$(v_1 - 50)/80 + v_1/50 + (v_1 - v_2)/40 = 0 \quad \text{at node } v_1$$

$$v_2/200 - 0.75 + (v_2 - v_1)/40 + (v_2 - 50)/800 = 0 \quad \text{at node } v_2$$

In standard form:


$$\begin{aligned} v_1 \left(\frac{1}{80} + \frac{1}{50} + \frac{1}{40} \right) + v_2 \left(-\frac{1}{40} \right) &= \frac{50}{80} \\ v_1 \left(-\frac{1}{40} \right) + v_2 \left(\frac{1}{40} + \frac{1}{200} + \frac{1}{800} \right) &= 0.75 + \frac{50}{800} \end{aligned}$$


$$v_1 = 34V;$$

$$v_2 = 53.2V$$


$$\text{So } v_0 = v_2 - 50 = 3.2V$$

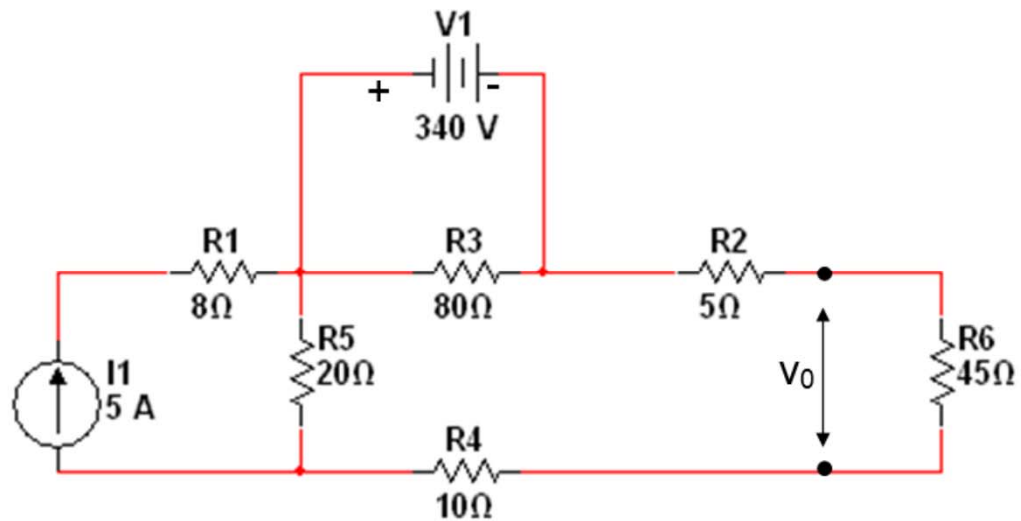Solve for V_0 . Are there any simplifications that can be done before starting the solution?




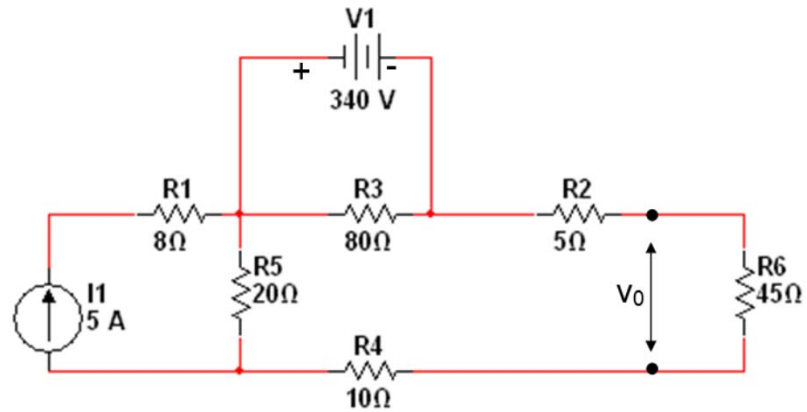

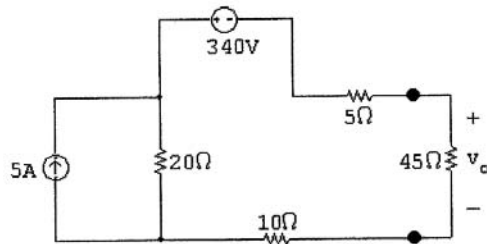
P 4.61 [a] First remove the 8Ω and 80Ω resistors:



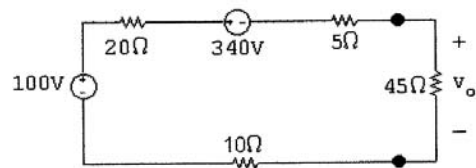Next use a source transformation to convert the 5 A current source and 20Ω resistor:




which simplifies to

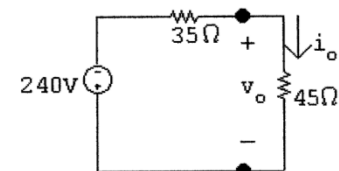


$$\therefore v_o = \frac{45}{80}(-240) = -135\text{ V};$$

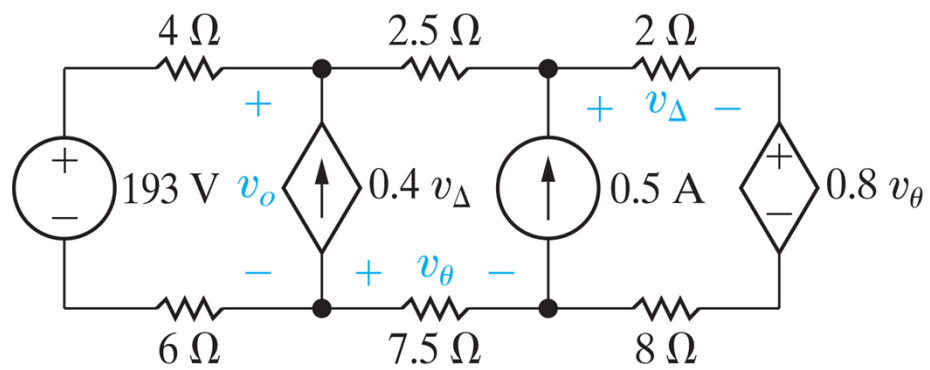Can you do a node voltage analysis of this circuit to determine v_0 ?



node voltage analysis

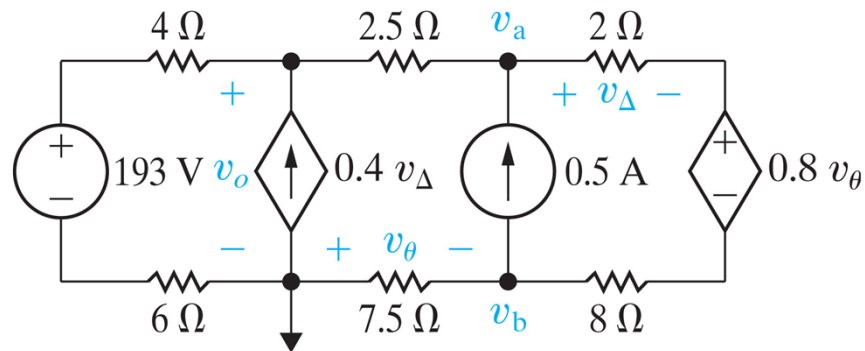

$$(v_0 - 193)/10 - 0.4 v_{\Delta} + (v_0 - v_a)/2.5 = 0$$


$$(v_a - v_0)/2.5 + 0.5 + [v_a - (v_b + 0.8v_{\theta})]/10 = 0$$

$$v_b/7.5 + 0.5 + (v_b + 0.8 v_{\theta} - v_a)/10 = 0$$

And the constraint equations are:

$$v_{\theta} = -v_b$$
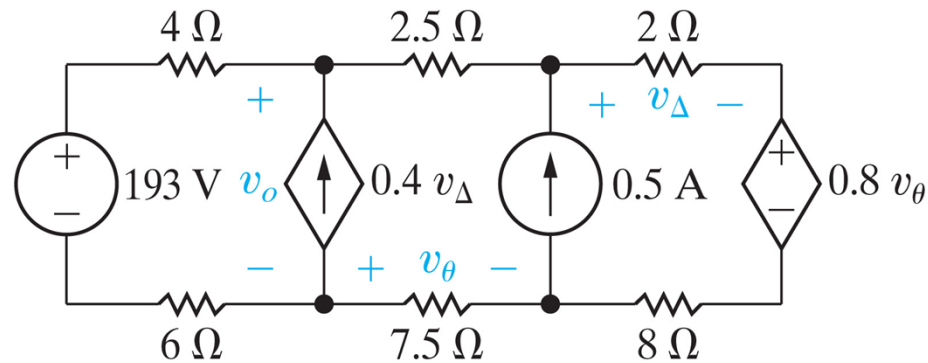
$$v_{\Delta} = [v_a - (v_b + 0.8 v_{\theta})]/10 * 2$$



Could you have done some simplifications ? It's clear that if the two dependent sources had been independent sources, source transforms would have allowed solution of the circuit using only Ohms Law. However, we need to preserve the 7.5 Ohm and 2 Ohm resistor (not combine them) because they define the values of the dependent current and voltage sources. Probably the best strategy would be to do the ordinary node voltage solution and solve the 3 x 3 matrix.

If this all made sense to you and you understand all of the homework problems so far you'll do fine on the mid-term exam.

I'll see you Friday