

Prelab 2

1.

Inputs: manual switch, S
Motion detector, M1
Disable switch, D

Outputs: light, L
Alarm, A

2.

S	M1	D	L	A
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	1
1	1	1	1	0

3.

$$S \cdot M1 \cdot D' = A$$

$$S + M1 \cdot D' = L$$

