
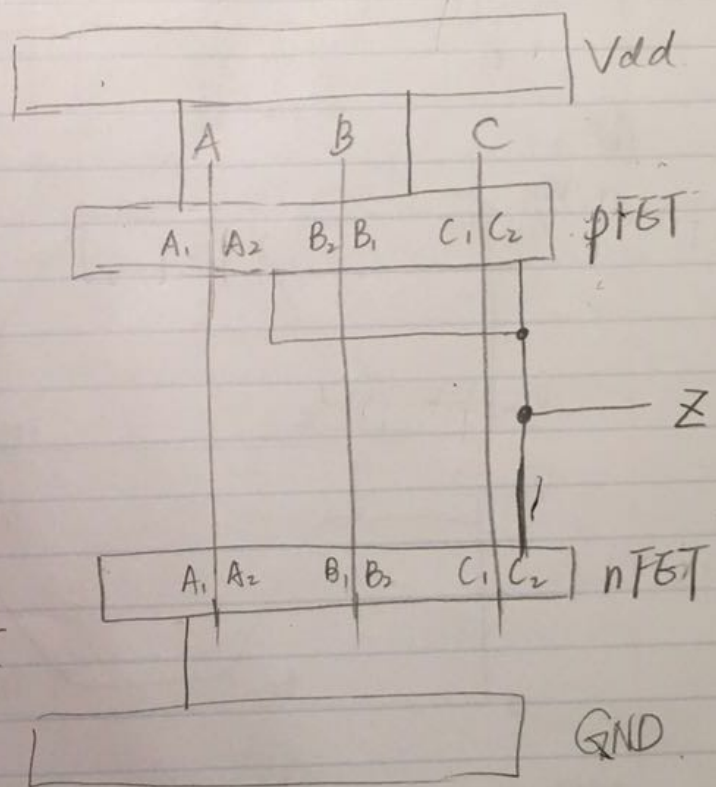


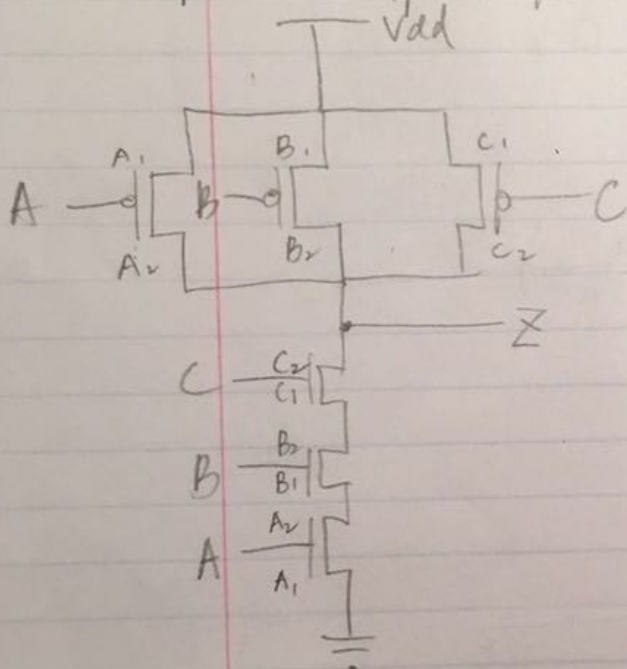
# Prelab 5

NMOS:  $V_{Tn} = 0.39V$ ,  $K_n' = 200 \mu A/V^2$ ,  $\gamma_n = 0$ ,  $\lambda_n = 0$

PMOS:  $V_{Tp} = 0.27V$ ,  $K_p' = 60 \mu A/V^2$ ,  $\gamma_p = 0$ ,  $\lambda_p = 0$



Final design

 

I curve inputs B and C,  
so output Z don't have to be  
outside the rectangle of VDD and GND.