


## Chapter 4 The processor: Datapath & Control

- Two implementations of RISC-V ISA
  - Single cycle implementation
    - Datapath & Control
  - Pipeline implementation
    - Datapath & Control
    - Data dependence/Hazard
- Consider only the core of RISC-V inst. Set
  - memory-reference inst. ld, sd
  - ALU inst. add, sub, and, or -- R-type
  - branch inst. beq, jal

# The Performance Perspective

- Performance of a machine is determined by:

- Instruction count
- cycle time
- CPI

 




- **Processor design (datapath and control) will affect:**

- cycle time
- **CPI**

- Single cycle processor:


- A simple start to understand more complicated pipeline implementation
 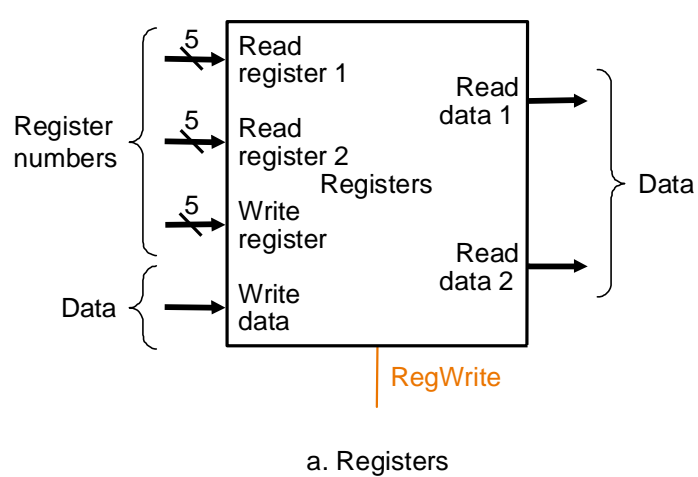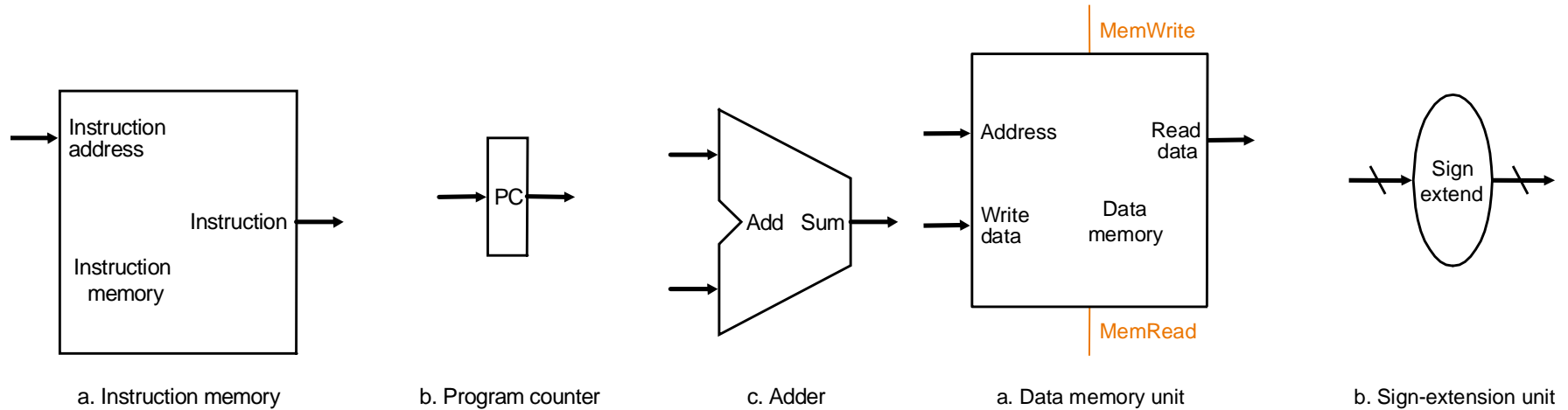
# Functional Units for Implementing instructions



## RISC-V ALU Functions

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract

 

Zero flag:


## Basic Idea of Datapath Design

- Design a datapath for each type of instruction
  - R
  - ld
  - sd
    - Combine ld and sd
  - beq
- Combine all
- Immediate Generation Unit

## Datapath for R-type

- Example: add x3, x4, x5
- Basic steps
  - fetch instruction
  - select registers (rs, rt),
  - ALU operation on two data, need ALU
  - write back registers

## Single-Cycle: Datapath for R-type

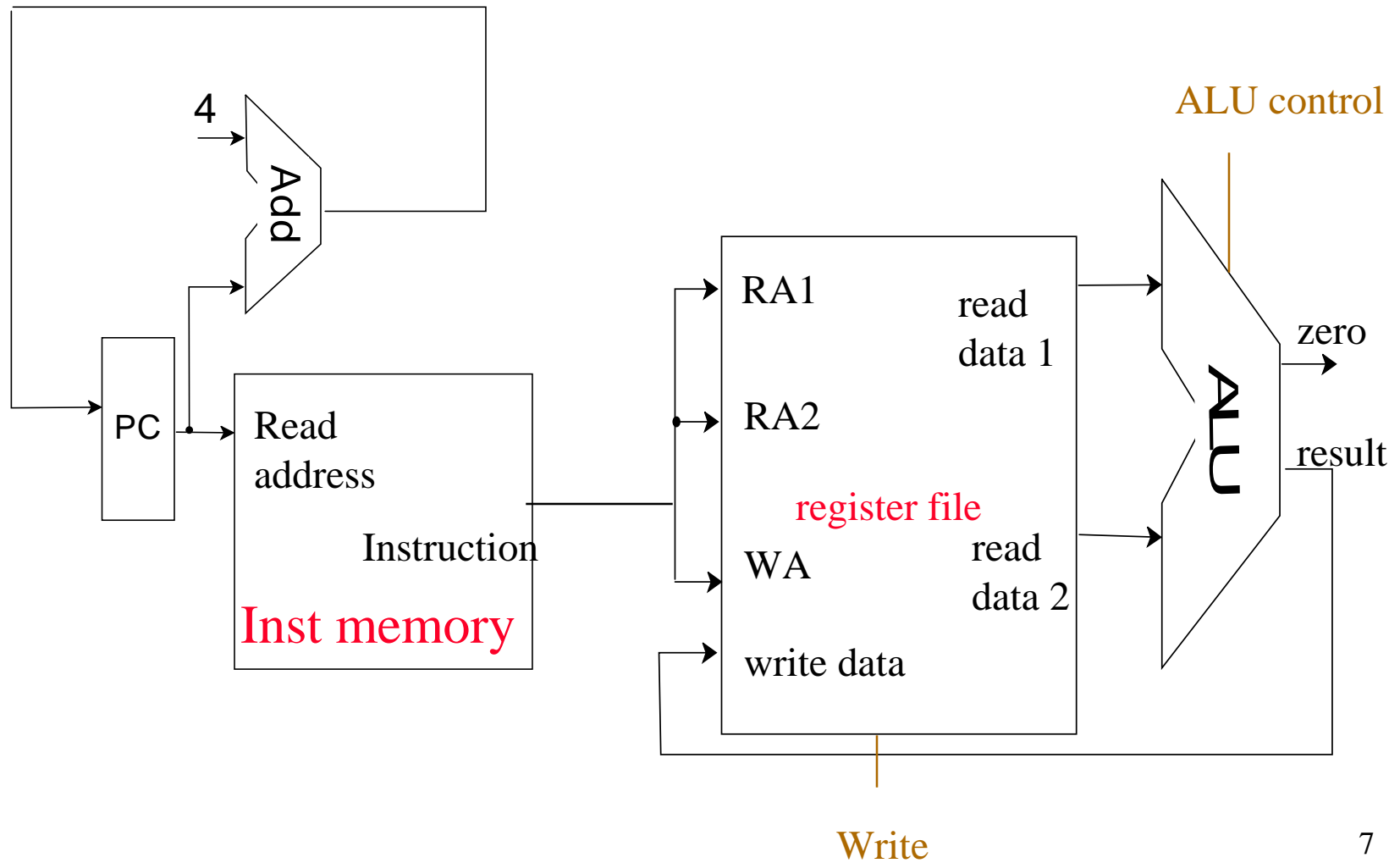

## Datapath for Load Word

- Basic steps: example: `ld x3, 64(x4)`
  - fetch instruction
  - select a register (rs1)
  - calculate address, need ALU
  - access memory (read memory)
  - write register file (rd)



## Datapath for Store Word

- Basic steps: example: `sd x3, 64(x4)`
  - fetch instruction
  - select two registers (rs1, rs2)
  - calculate address, need ALU
  - access memory (write memory)

## Combining datapaths of ld & sd


- Memory address
  - Ld: in fcunct7 and rs2
  - sw: in fcunct7 and rd
- Register write control signal.

## Datapath for beq


- Basic steps: beq x1, x2, offset
  - fetch the instruction
  - select registers
  - test condition, calculate branch address (need additional ALU)
- ALU for branch condition
- Adder for branch address
- Zero: control logic to decide if branch.
 
## Creating a Single Datapath for All Inst.

- Combine datapaths for R-type, memory inst. and branch inst.
  - using multiplexers
  - without duplicating common functional units.
- As an example, combine R-type and memory type datapaths
- Final goal: combine all types of datapaths



R-type data path

 


Memory type datapath

Key Differences:

2nd input to ALU


Value written into register file

# Simple Datapath for Single Cycle

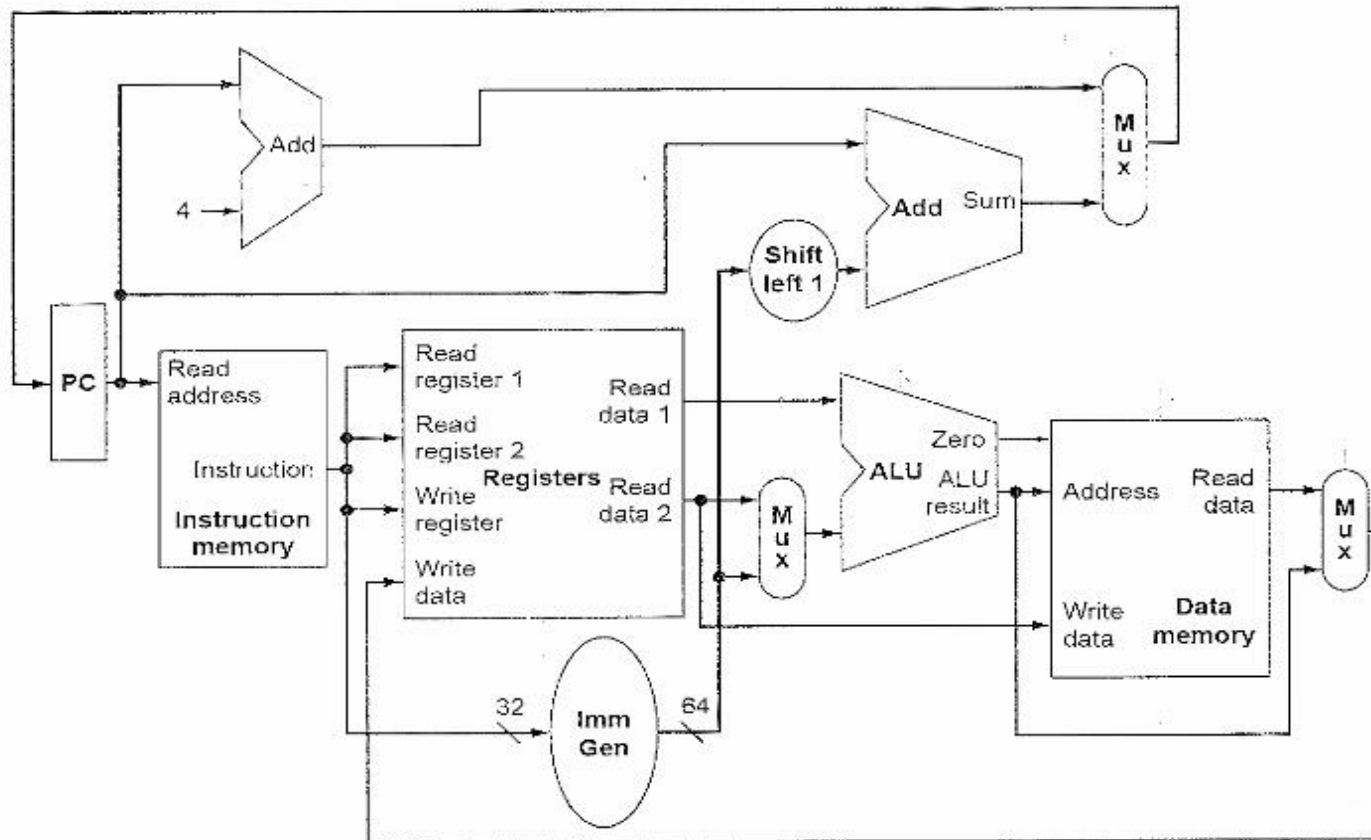


Can execute basic instructions in a single clock cycle

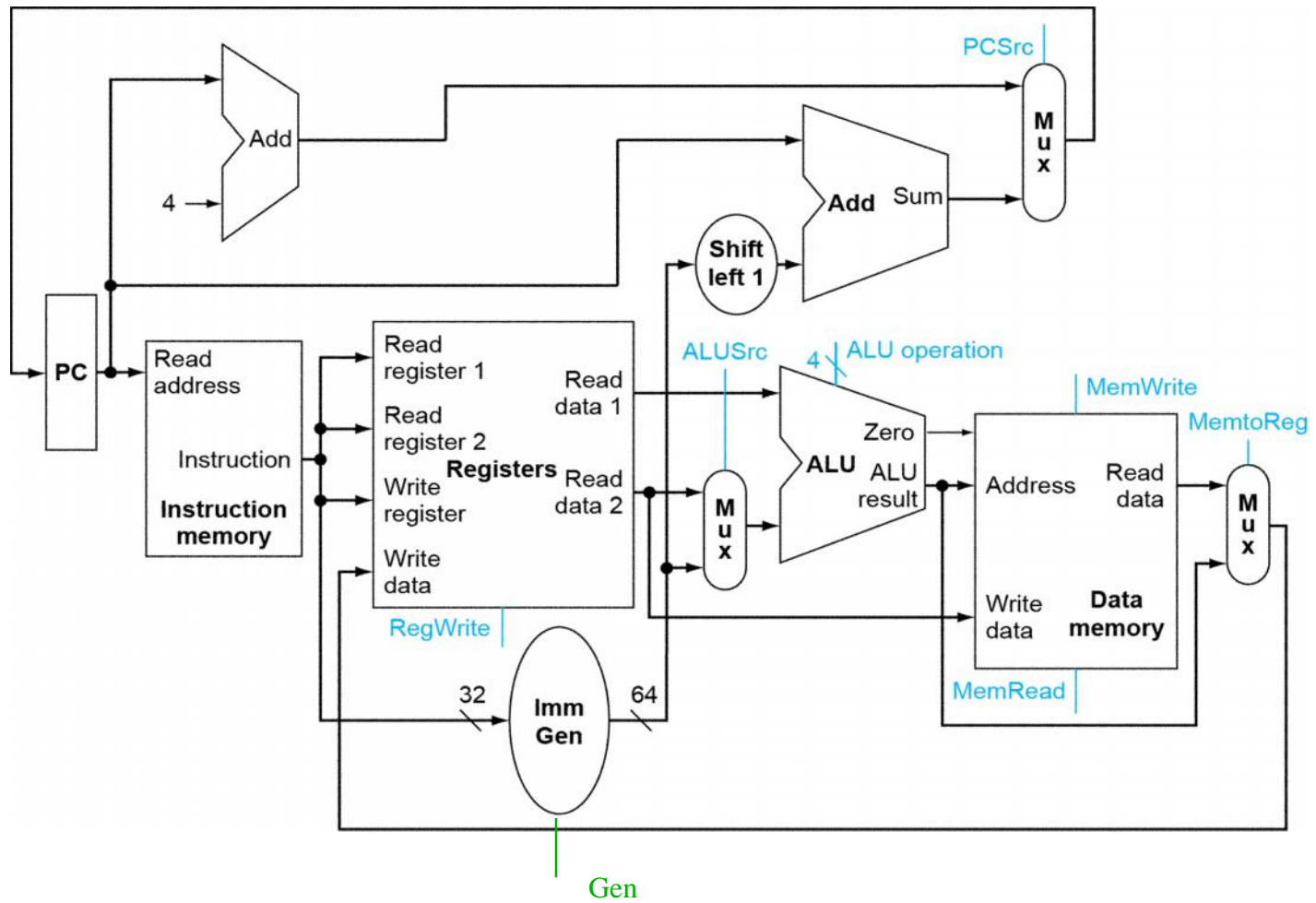No resource can be used more than once during a single cycle



 
# Single-Cycle: Control

- Main control:
  - input: 7-bit from opcode
  - output: 9+ control lines
- ALU control:
  - input: ALUop + 4-bit (funct7 + funct3)
  - output: 4 lines
  - for non R type, ALU control depends on only ALUop
- Control for imm gen ?





# Control

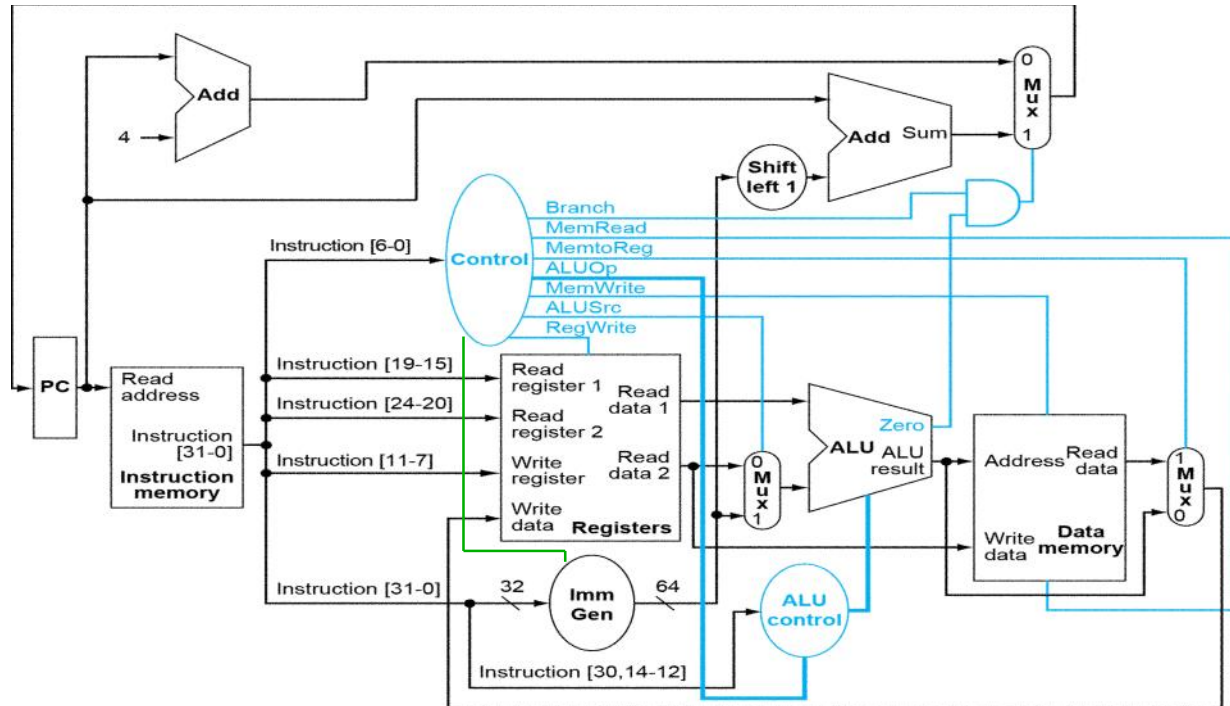


Instruction	RegWrt	Memto-Reg	Brch	Mem Read	Mem Write	ALUSrc	ALUOp1	ALUp0	Gen
R-format									
ld									
sd									
beq									

## Main Control Unit -- Definitions of Control Signals

Signal Name	Effect when deasserted	Effect when asserted
MemRead	None	Data put on read dataoutput
MemWrite	None	Write data into memory
RegWrite	None	Write register
ALUSrc	2nd ALUinput from register file	2nd ALUinput from imm gen
PCSrc	$PC = PC + 4$	$PC = \text{branch address}$
MemtoReg	result of ALU is sent	data in memory is sent

$PCsrc = \text{branch AND zero}$

# Single cycle control

 

## ALU Control

- ALU used for
  - Load/Store: F = add
  - Branch: F = subtract
  - R-type: F depends on opcode

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract

## ALU Control


- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

opcode	ALUOp	Operation	Funct7+funct3	ALU action	ALU control
ld	00	load register	XXXXXXXX XXX	add	0010
sd	00	store register	XXXXXXXX XXX	add	0010
beq	01	branch on equal	XXXXXXXX XXX	subtract	0110
R-type	10	add	0 <u>1</u> 00000 <u>000</u>	add	0010
		subtract	0 <u>1</u> 00010 <u>000</u>	subtract	0110
		AND	0 <u>1</u> 00100 <u>111</u>	AND	0000
		OR	0 <u>1</u> 00101 <u>110</u>	OR	0001


## ALU Control Truth Table

	ALUOp		Inst[30][14:12]		ALU control output
	00		X XXX		0010
	00		X XXX		0010
	01		X XXX		0110
	10		<u>1</u> <u>000</u>		0010
			<u>1</u> <u>000</u>		0110
			<u>1</u> <u>111</u>		0000
			<u>1</u> <u>110</u>		0001

# Datapath With Control

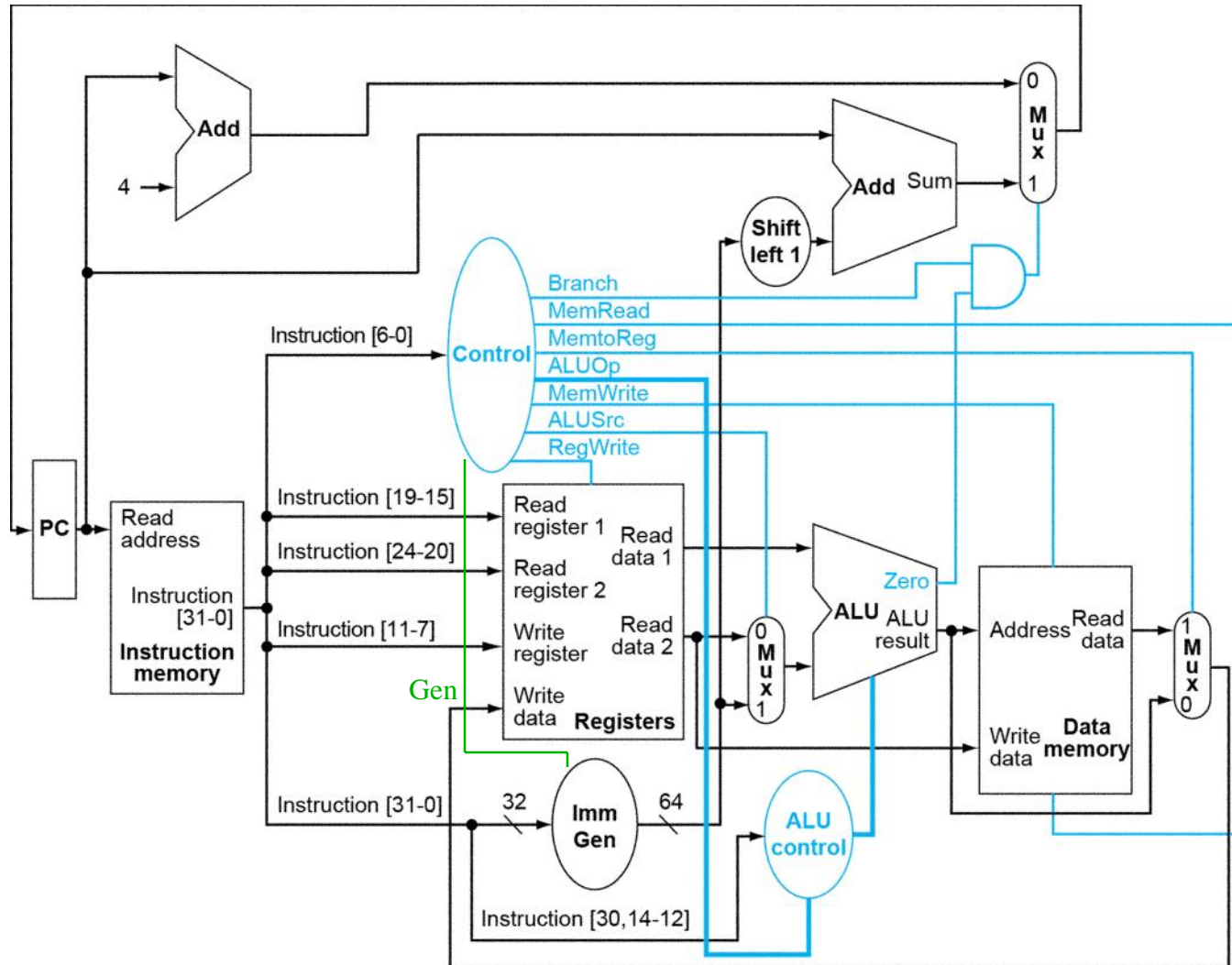


# R-Type Instruction

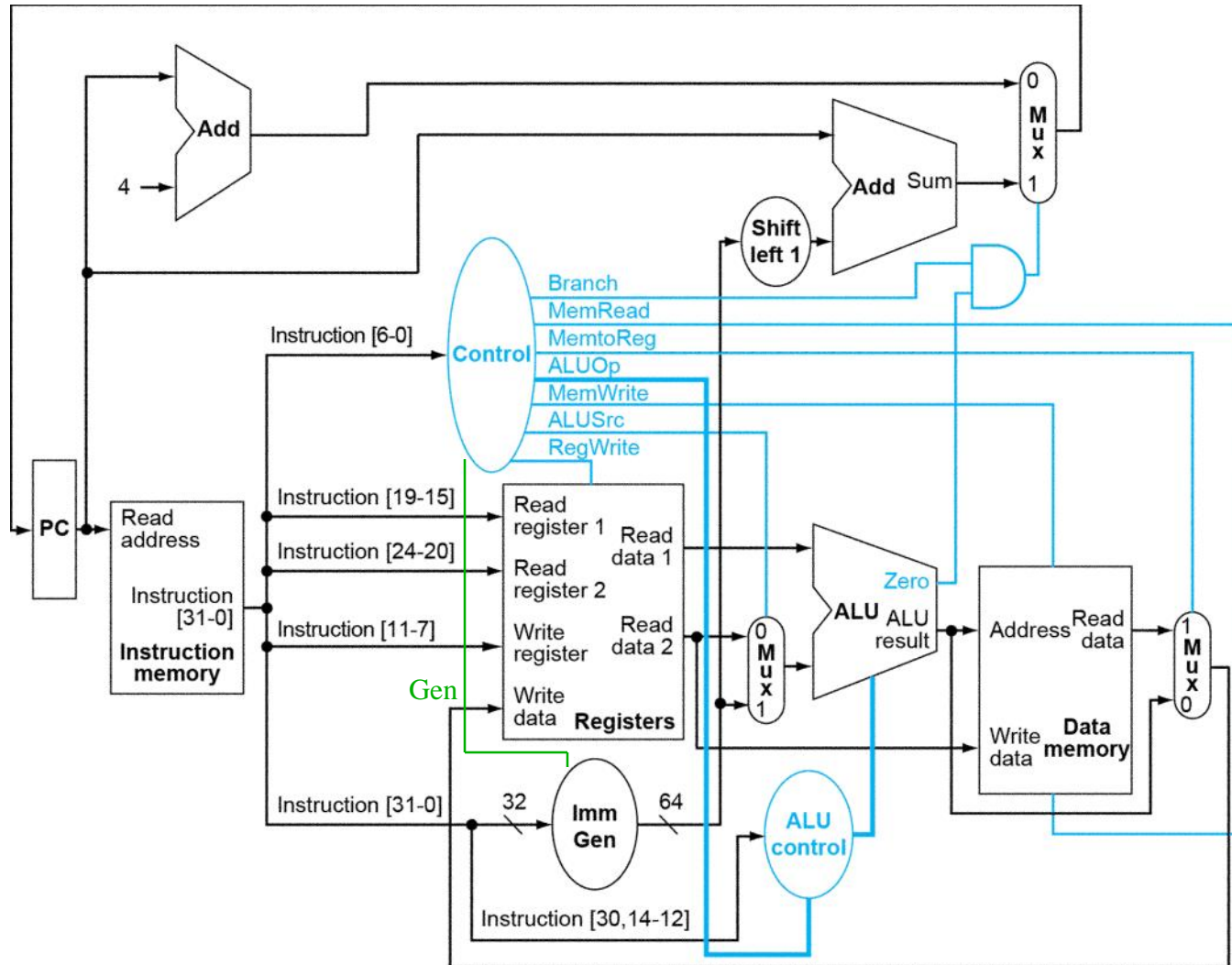





# Load Instruction

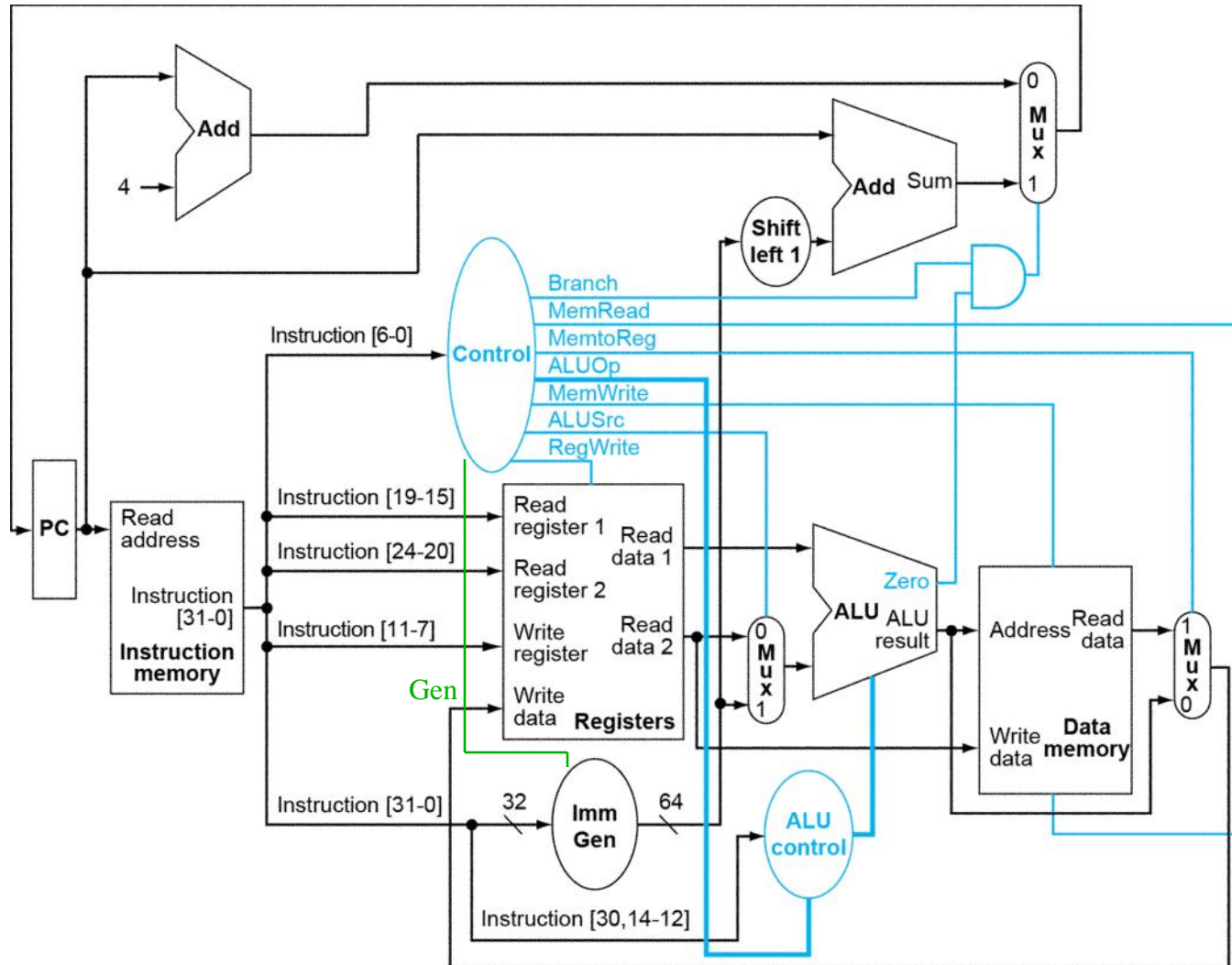

# BEQ Instruction

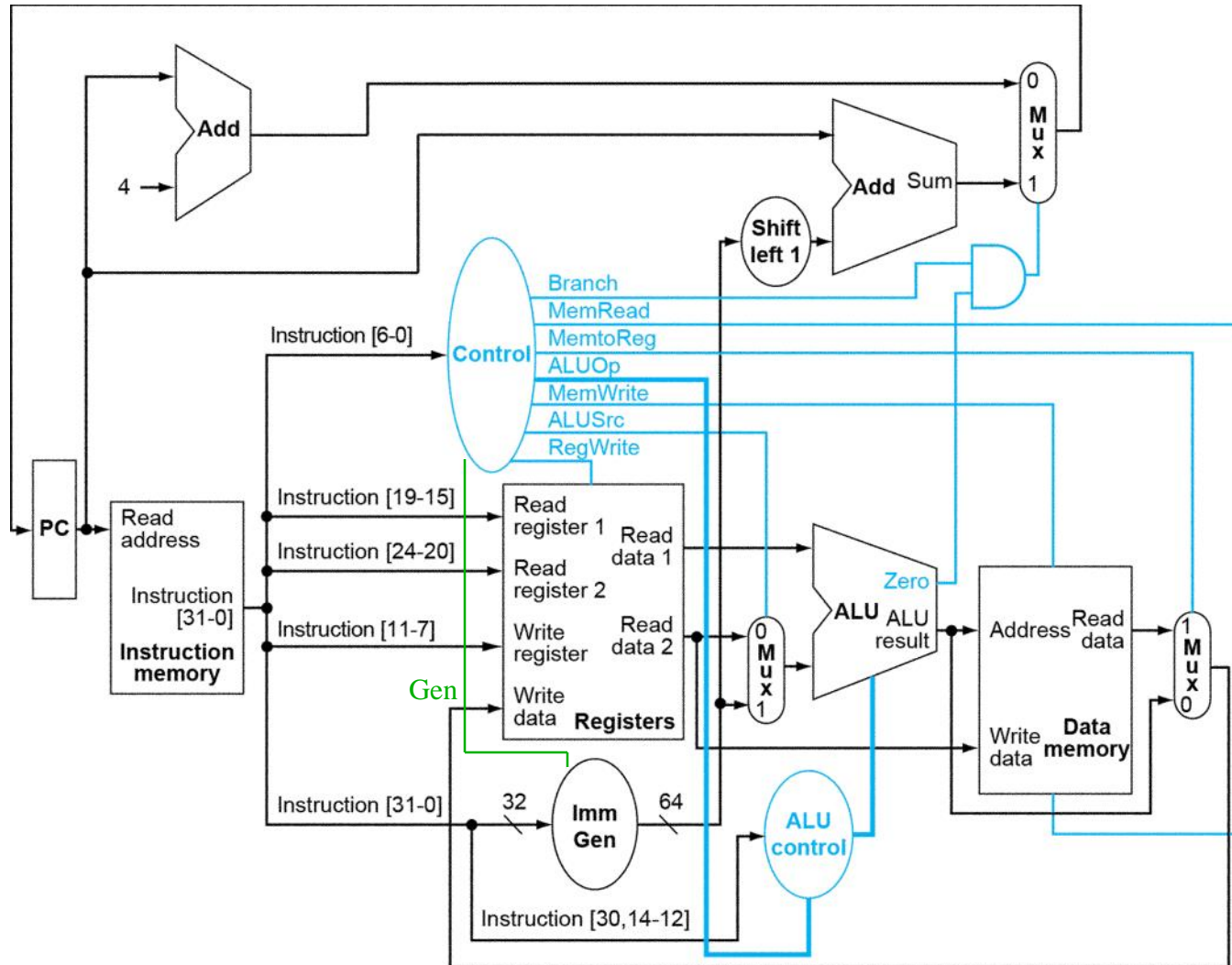

## Add jal to Datapath

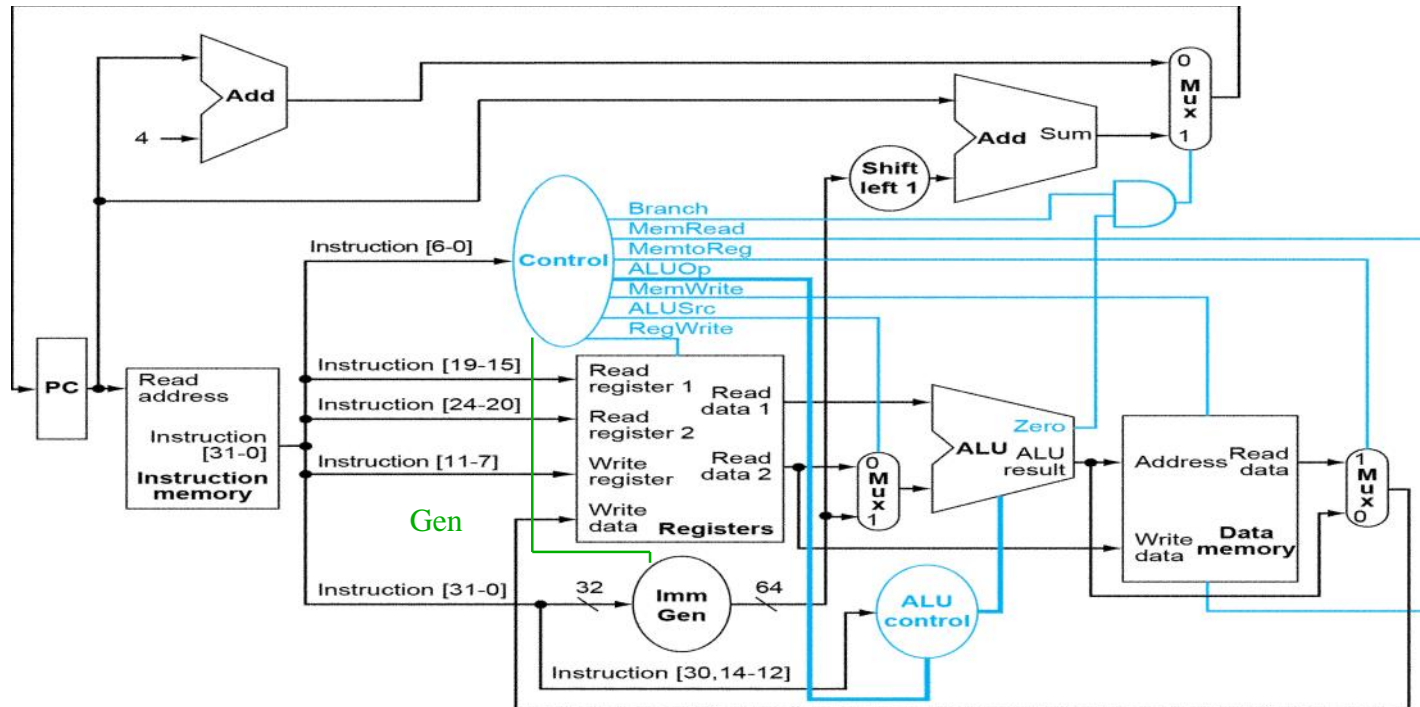

Instruction	RegWrt	Memto-Reg	Brch	Mem Read	Mem Write	ALUSrc	ALUOp1	ALUp0	Gen
R-format									
ld									
sd									
beq									

## Add jal to the datapath

- Operation 1:  $PC = \text{jump address}$ 
  - Assume jump address is formed by imm gen
- Operation 2:  $x_{rd} = PC$

## Discussion on imm gen

- Combinational circuit
- Input: the whole instruction[31:0]
- Four possible outputs
  - Immediate for ld
  - Immediate for sd
  - Immediate for beq
  - Immediate for jal

## Single-Cycle: Summary

- How to construct datapath for R-type, ld/sd, beq, jal
- How to construct the control
  - ALU control
  - main control
  - imm gen
- How the datapath + control to execute instruction

# Execution (cycle) Time Analysis

Arithmetic & Logical




Load



← Critical Path →

Store

 

Branch



- Cycle time  $\geq$  the critical path length
- Long Cycle Time
  - All instructions take as much time as the slowest

Exercise: Can MemtoReg be eliminated and replaced by MemRead?

	Brnch	MemRd	MemtoRg	ALUop	MemWrt	ALUSrc	RegWrt	gen
<i>ld</i>	0	1	1	00	0	1	1	
<i>sd</i>	0	0	x	00	1	1	0	
<i>R</i>	0	0	0	10	0	0	1	
<i>beg</i>	1	0	x	01	0	0	0	
<i>Jal</i>	0	0	x	xx	0	x	0	
	B							



Exercise: What would be the cycle time for the following cases?

- Assume
  - ALU delay=2ns,
  - Adder (PC+4) delay=x ns,
  - Adder (branch address) delay = y ns
- $X=3, y=3$
- $x=5, y=5$
- $x=1, y=8$