

## Part 1


a)

w0	w1	s	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

b)


w0\w1s	00	01	11	10
0	0	0	1	0
1	1	0	1	1

$$Z = w1(s) + w0(s')$$

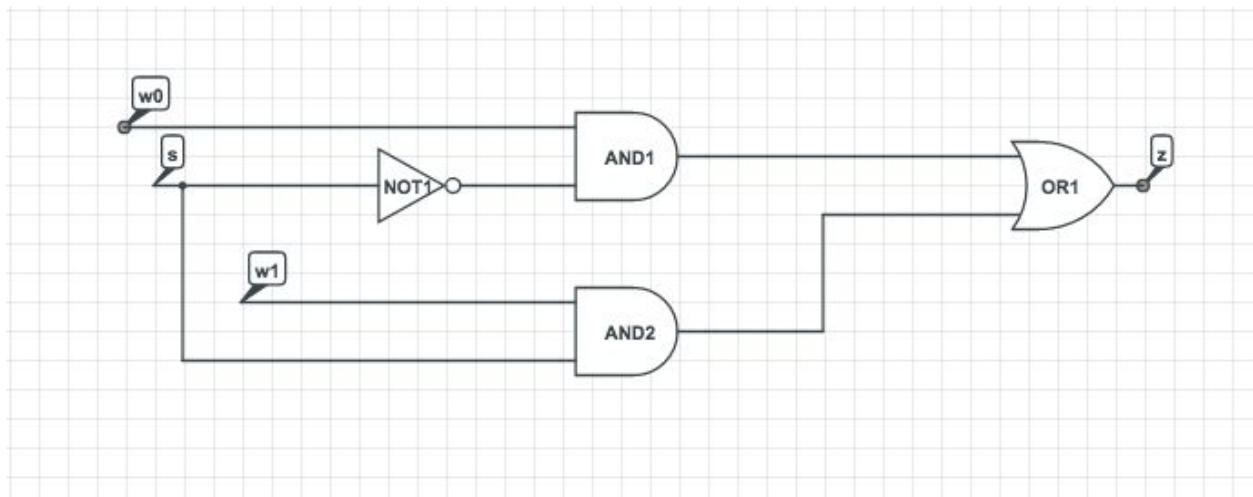

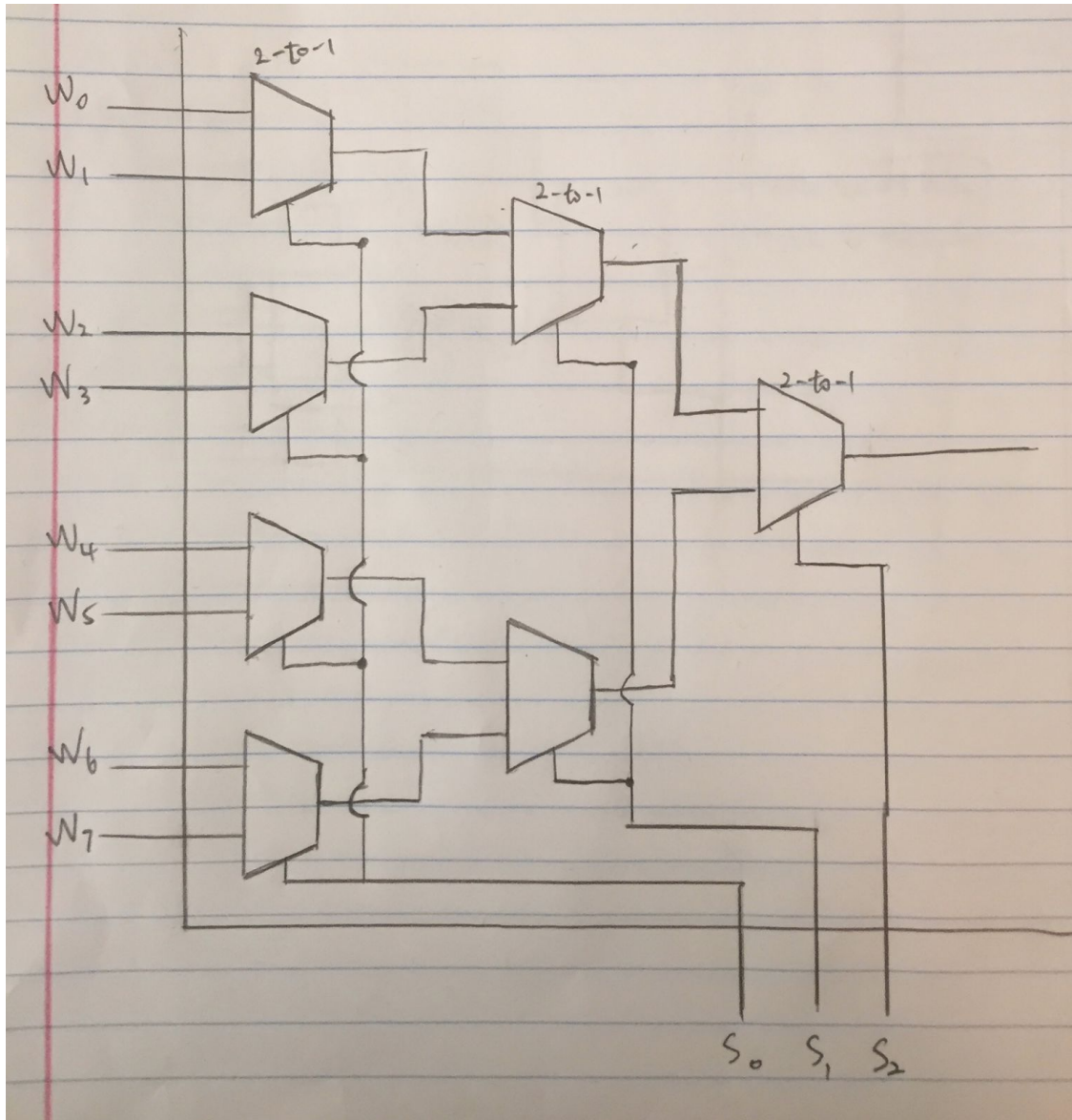
## Part 2

We will need 7 2-1 mux in order to build a 8-1 mux



I have 8 data inputs  $w_0, w_1, w_2, w_3, w_4, w_5, w_6, w_7$  and 3 select inputs  $s_0, s_1, s_2$  ordering from left to right.

As shown in the picture below, when  $s_2s_1s_0 = 1\ 0\ 0$ , the output is  $w_4$ ; when  $s_2s_1s_0 = 0\ 1\ 1$ , the output is  $w_3$ .

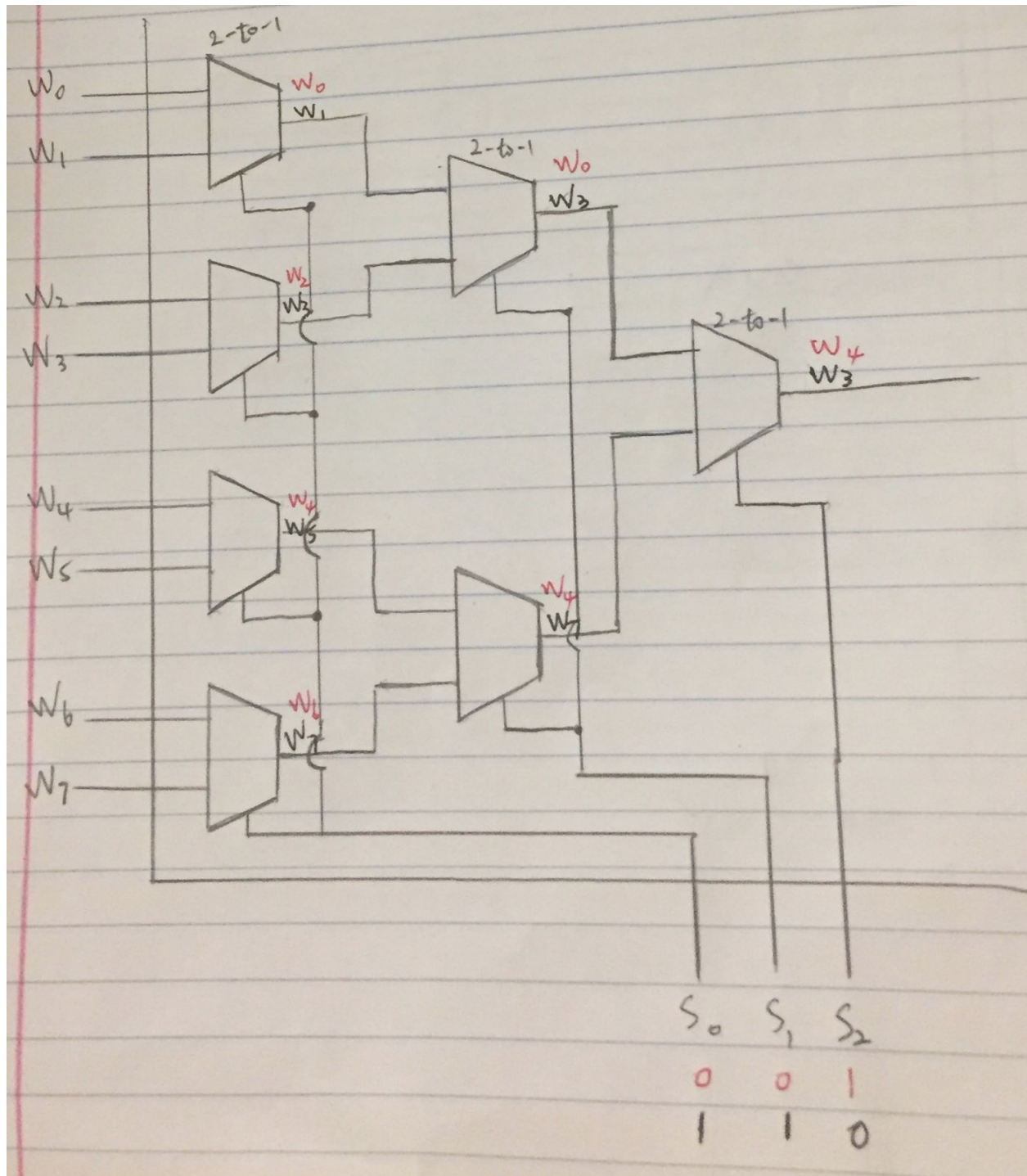

Part 3

Truth Table:

A	B	C	F
---	---	---	---

0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

