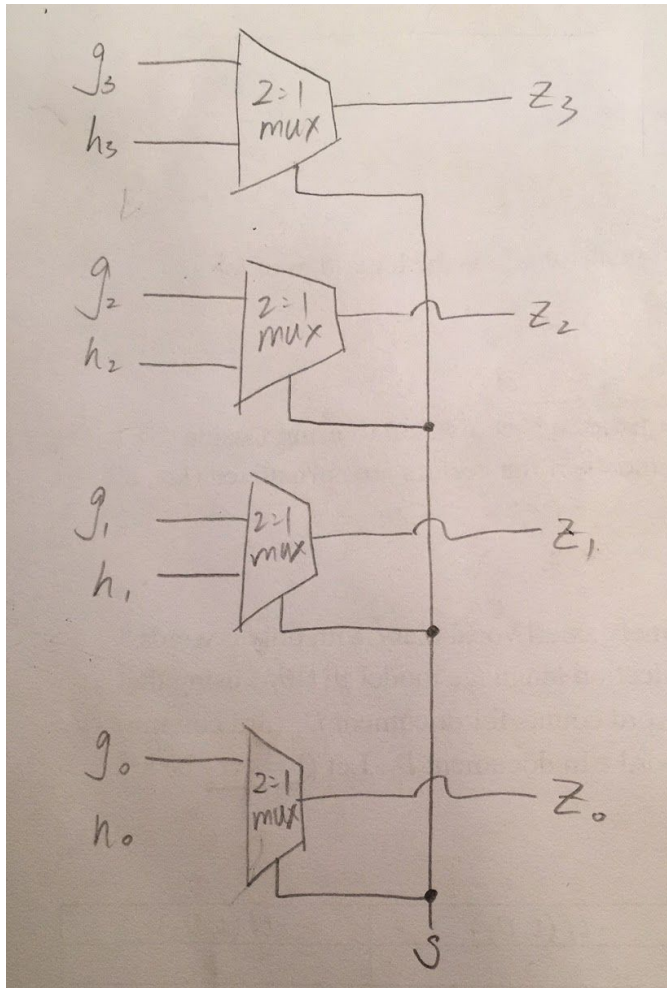


1.




2.


Op-select input	Adder 4-bit A inputs	Adder 4-bit B inputs	Adder Carry-in	Operation	Notes
r1 r0 p1 p0	a3 a2 a1 a0	b3 b2 b1 b0			
0 0 0 0	a3 a2 a1 a0	b3 b2 b1 b0	0	$X = A + B$	Add
0 0 0 1	a3 a2 a1 a0	b3 b2 b1 b0	1	$X = A + B + 1$	Add and increment
0 0 1 0	a3 a2 a1 a0	b3' b2' b1' b0'	0	$X = A - B - 1$	Subtract and decrement
0 0 1 1	a3 a2 a1 a0	b3' b2' b1' b0'	1	$X = A - B$	subtract
0 1 0 0	a3 a2 a1 a0	0 0 0 0	0	$X = A$	Transfer A
0 1 0 1	a3 a2 a1 a0	0 0 0 0	1	$X = A + 1$	Increment A

0 1 1 0	a3 a2 a1 a0	1 1 1 1	0	$X = A - 1$	Decrement A
0 1 1 1	a3 a2 a1 a0	0 0 0 0	0	$X = A$	Transfer A

3.

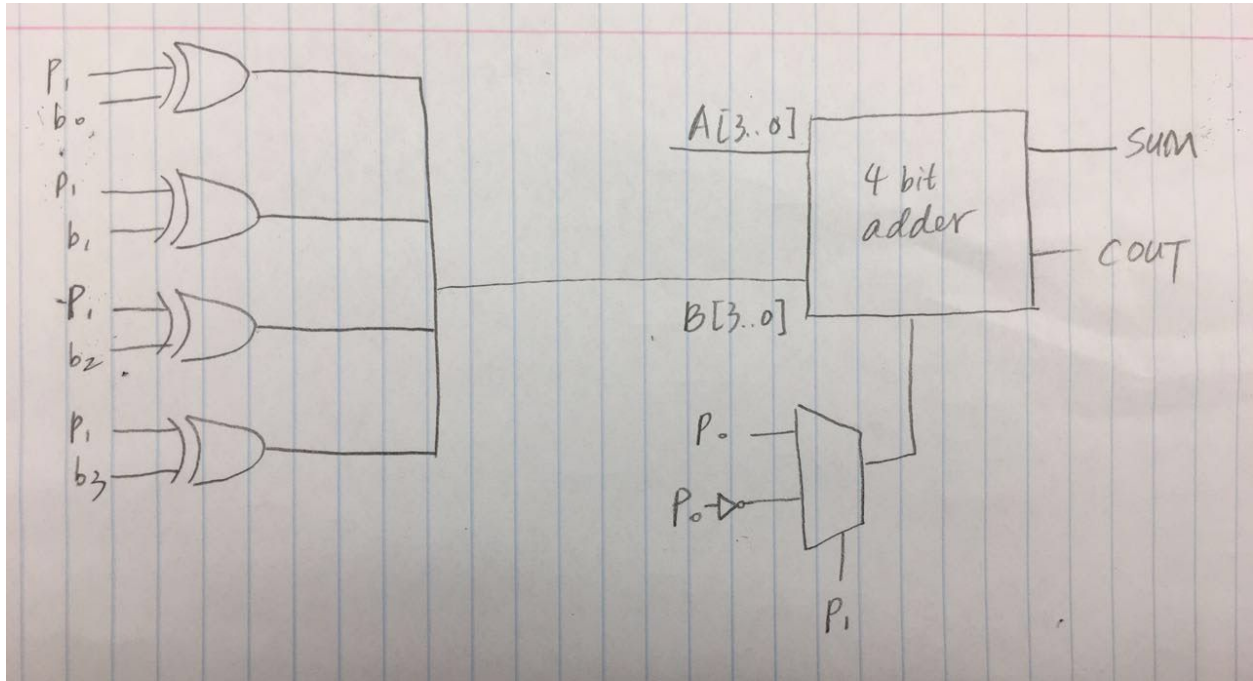

4.

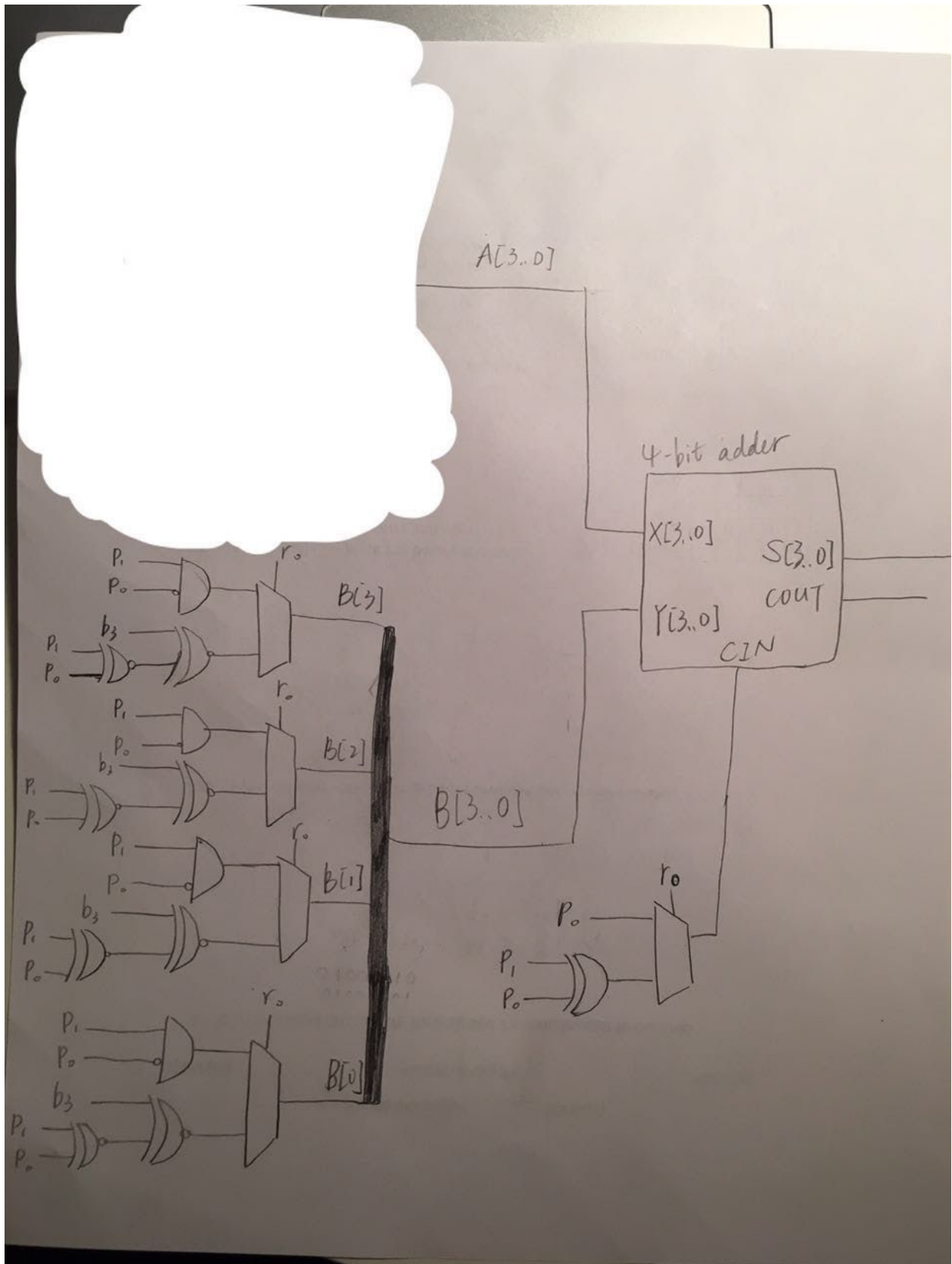

1. Let $r1 = r0 = p1 = p0 = 0$, see if the result is $A + B$.
2. Let $r1 = r0 = p1 = 0$, $p0 = 1$, see if there is an increment compared to the first result, which is $A + B$.
3. Let $r1 = r0 = 0$, $p1 = p0 = 1$, see if the result is $A - B$.
4. Let $r1 = r0 = p0 = 0$, $p1 = 1$, see if there is an decrement compared to the third result, which is $A - B$.
5. Let $r1 = p1 = p0 = 0$, $r0 = 1$, see if A goes through.
6. Let $r1 = 0$, $r0 = p1 = p0 = 0$, see if A goes through.
7. Let $r1 = p1 = 0$, $r0 = p0 = 1$, see if there is an increment compared to the sixth result, which is A.
8. Let $r1 = p0 = 0$, $r0 = p1 = 1$, see if there is an decrement compared to the sixth result, which is A.