


FIVE STAR.
★★★★★

1.


T	Q(t)	Q(t+1)	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

T	Q	0	1
0	0	0	1
1	1	1	0


$D = TQ' + T'Q$

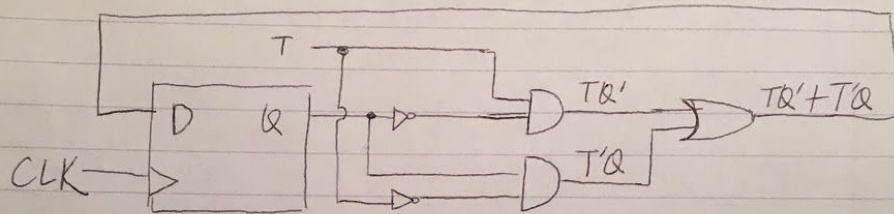


FIVE STAR.
★★★★★

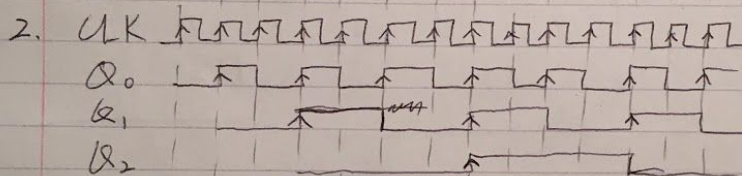

FIVE STAR.
★★★★★

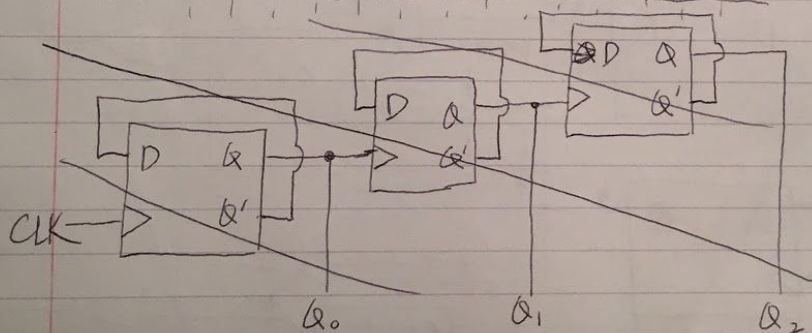

FIVE STAR.
★★★★★

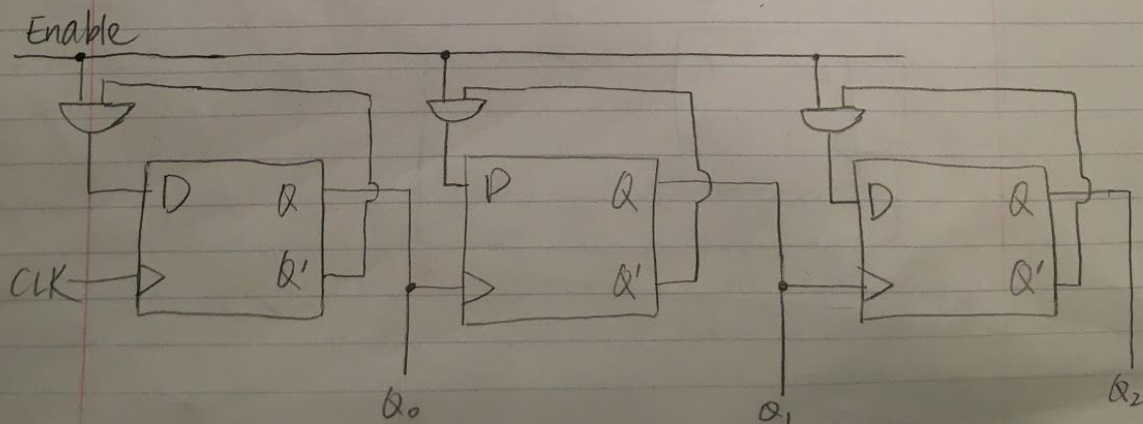

3	Present state			Next state			D_a	D_b	D_c
	a	b	c	A	B	C			
	0	0	0	0	0	1	0	0	1
	0	0	1	0	1	0	0	1	0
	0	1	0	0	1	1	0	1	1
	0	1	1	1	0	0	1	0	0
	1	0	0	1	0	1	1	0	1
	1	0	1	1	1	0	1	1	0
	1	1	0	1	1	1	1	1	1
	1	1	1	0	0	0	0	0	0

$a \backslash bc$ 00 01 11 10

0 0 0 1 0
1 1 1 0 1

$$D_a = ab' + a'bc + abc'$$

$a \backslash bc$ 00 01 11 10

0 0 1 0 1
1 0 1 0 1

$$D_b = b'c + bc'$$

$a \backslash bc$ 00 01 11 10

0 1 0 0 1
1 1 0 0 1

$$D_c = c'$$

