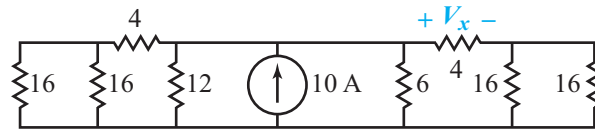


Problem 2.31 Use resistance reduction and source transformation to find V_x in the circuit of Fig. P2.31. All resistance values are in ohms.

Solution:



Problem 2.37 Find R_{eq} for the circuit in Fig. P2.37. All resistances are in ohms.

Solution:



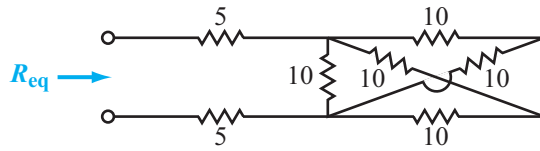


Figure P2.37: Circuit for Problem 2.37.

Problem 3.25 Apply mesh analysis to find I_x in the circuit of Fig. P3.25.

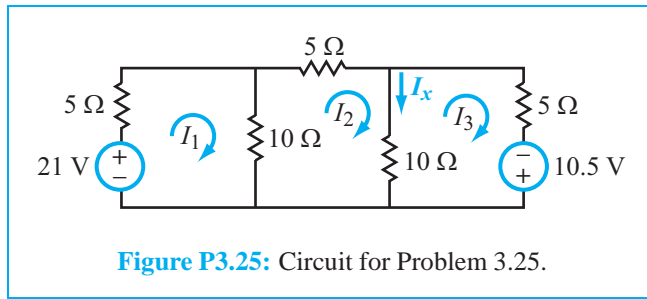


Problem 3.26 Apply mesh analysis to determine the amount of power supplied by the voltage source in Fig. P3.26.

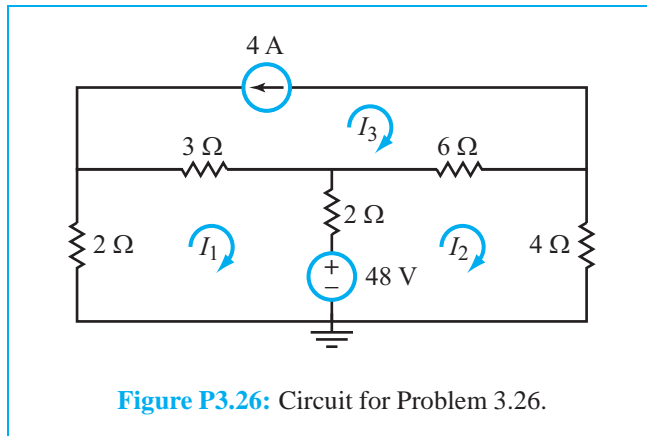


Problem 3.4 For the circuit in Fig. P3.4:


- (a) Apply nodal analysis to find node voltages V_1 and V_2 .
- (b) Determine the voltage V_R and current I .

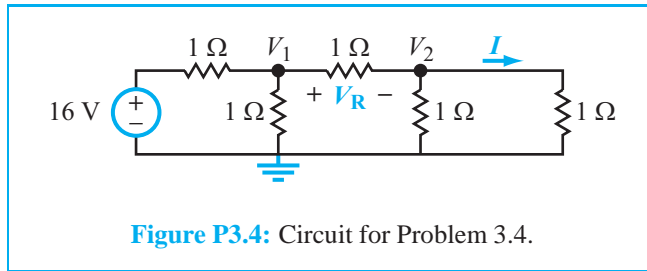

Problem 3.5 Apply nodal analysis to determine the voltage V_R in the circuit of Fig. P3.5.

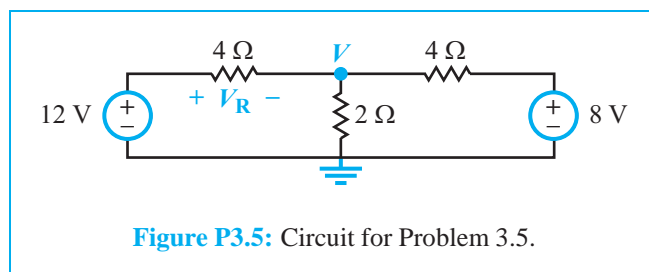

Problem 3.55 Find the Thévenin equivalent circuit at terminals (a, b) for the circuit in Fig. P3.55.

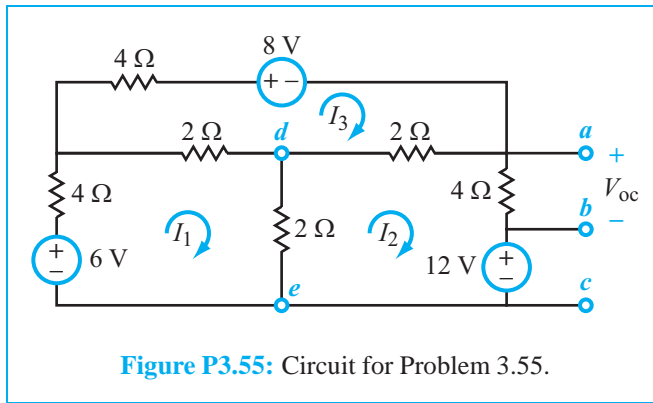

Problem 3.71 Determine the maximum power extractable from the circuit in Fig. P3.71 by the load resistor R_L .



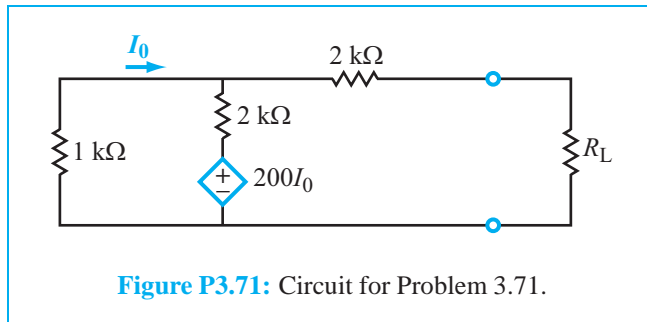


Figure P3.71: Circuit for Problem 3.71.

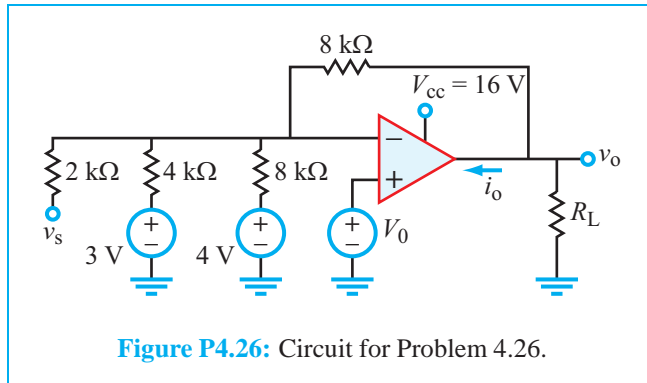
Problem 4.26 Relate v_o in the circuit of Fig. P4.26 to v_s and specify the linear range of v_s . Assume $V_0 = 0$.



Problem 4.34 The circuit in Fig. P4.34 contains two single-pole single-throw switches, S_1 and S_2 . Determine the closed circuit gain $G = v_o/v_s$ for each of the four possible closed/open switch combinations.

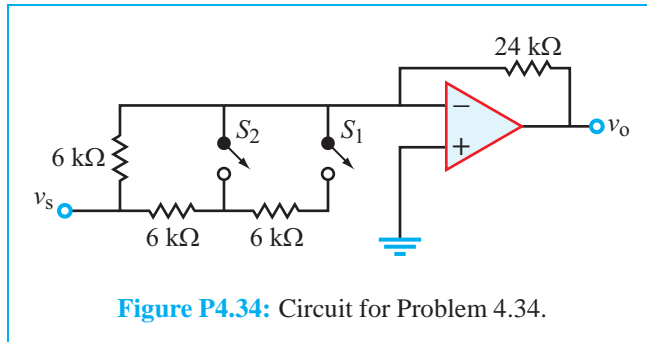


Problem 4.41 Relate v_o in the circuit of Fig. P4.41 to v_s .

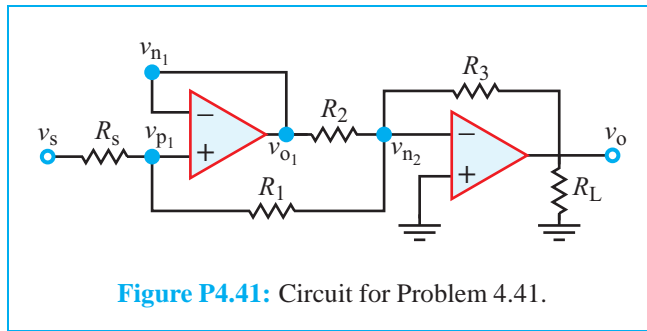


Problem 5.17 Reduce the circuit in Fig. P5.17 into a single equivalent capacitor at terminals (a, b) . Assume that all initial voltages are zero at $t = 0$.

Solution:

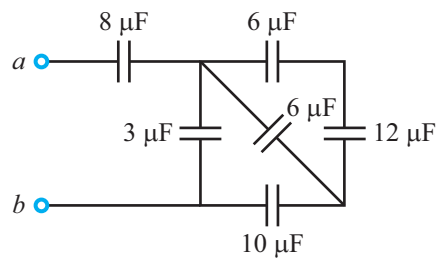

Problem 5.28 For the circuit in Fig. P5.28, determine the voltage across C and the currents through L_1 and L_2 under dc conditions.


Solution:

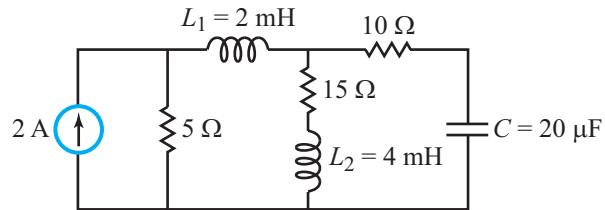

Problem 5.49 After having been in position 1 for a long time, the switch in the circuit of Fig. P5.49 was moved to position 2 at $t = 0$. Determine $i_1(t)$ and $i_2(t)$ for $t \geq 0$ given that $I_0 = 6 \text{ mA}$, $R_0 = 12 \, \Omega$, $R_1 = 10 \, \Omega$, $R_2 = 40 \, \Omega$, $L_1 = 1 \text{ H}$, and $L_2 = 2 \text{ H}$.

Solution:

(a) Circuit

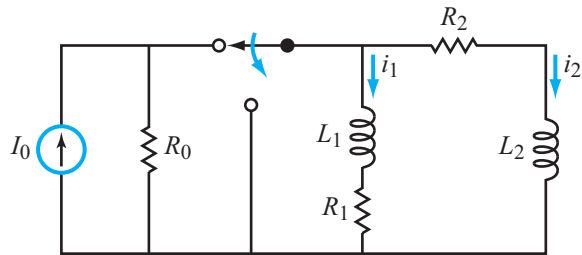

Problem 6.7 For the circuit of Fig. P6.7, determine $i_1(0)$ and $i_2(0)$.

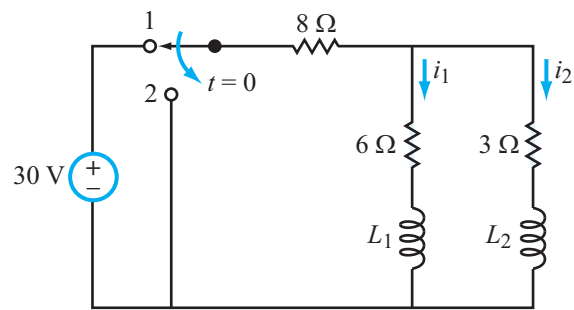


Figure P6.7: Circuit for Problem 6.7.

Problem 7.27 Determine the equivalent impedance:

- (a) Z_1 at 1000 Hz (Fig. P7-27)(a))
- (b) Z_2 at 500 Hz (Fig. P7-27)(b))
- (c) Z_3 at $\omega = 10^6$ rad/s (Fig. P7-27)(c))
- (d) Z_4 at $\omega = 10^5$ rad/s (Fig. P7-27)(d))
- (e) Z_5 at $\omega = 2000$ rad/s (Fig. P7-27)(e))

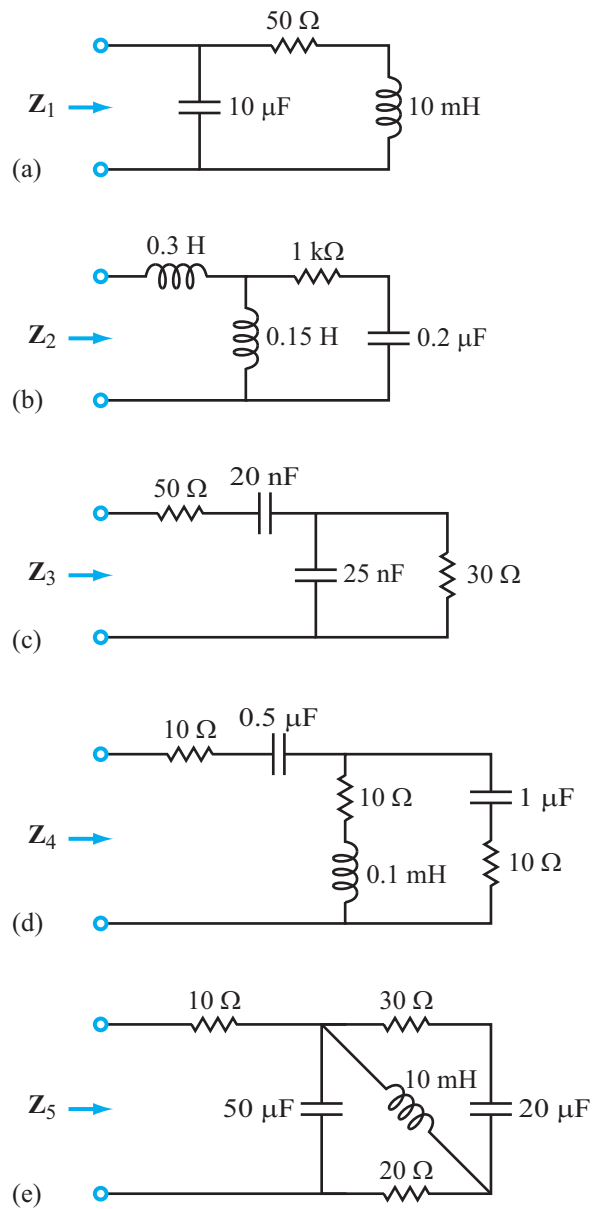


Figure P7.27: Circuit for Problem 7.27.

Problem 7.34 At what angular frequency ω is the current $i(t)$ in the circuit of Fig. P7.34 in-phase with the source voltage $v_s(t)$?

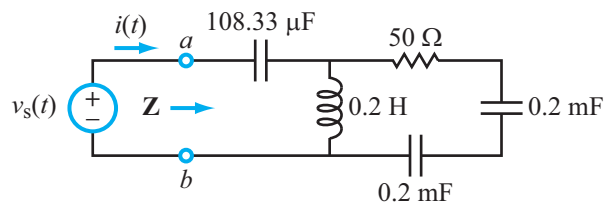


Figure P7.34: Circuit for Problem 7.34.

Problem 8.13 Determine the average power dissipated in the load resistor R_L of the circuit in Fig. P8.13, given that $V_s = 100$ V, $R_1 = 1$ k Ω , $R_2 = 0.5$ k Ω , $R_L = 2$ k Ω , $Z_L = j0.8$ k Ω , and $Z_C = -j4$ k Ω .

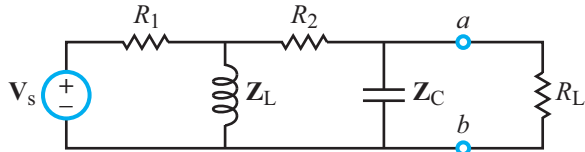


Figure P8.13: Circuit for Problem 8.13.

Section 8-4: Power Factor

Problem 8.22 The RL load in Fig. P8.22 is compensated by adding the shunt capacitance C so that the power factor of the combined (compensated) circuit is exactly unity. How is C related to R , L , and ω in that case?

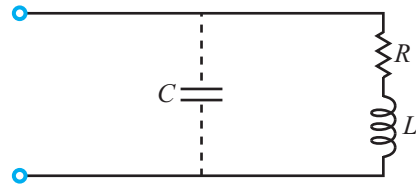


Figure P8.22: Circuit for Problem 8.22.