
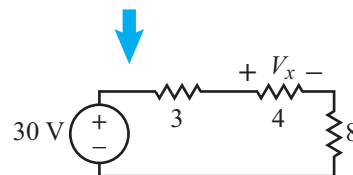
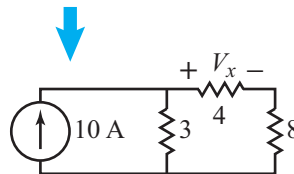
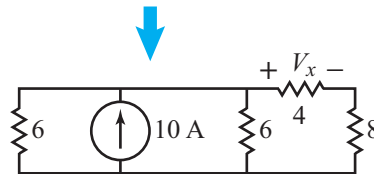
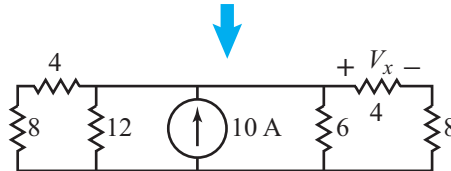


**Problem 2.31** Use resistance reduction and source transformation to find  $V_x$  in the circuit of Fig. P2.31. All resistance values are in ohms.

**Solution:**

Figure P2.31: Circuit for Problem 2.31.

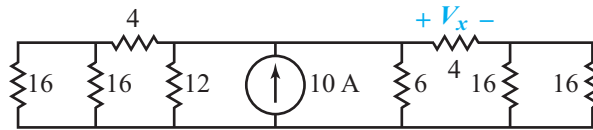

$$V_x = \frac{30 \times 4}{3 + 4 + 8} = 8 \text{ V.}$$

**Problem 2.37** Find  $R_{eq}$  for the circuit in Fig. P2.37. All resistances are in ohms.

**Solution:**



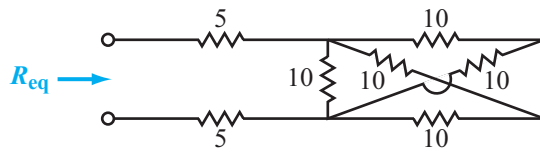
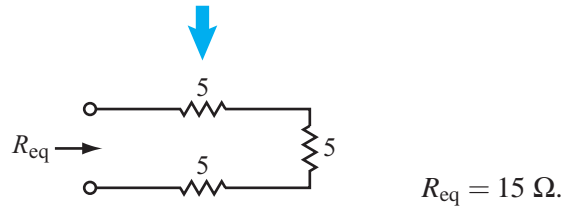


Figure P2.37: Circuit for Problem 2.37.

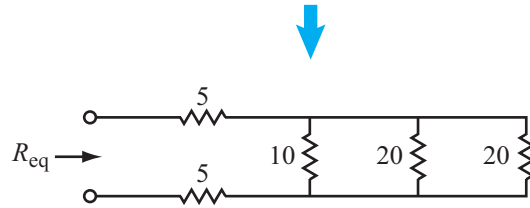

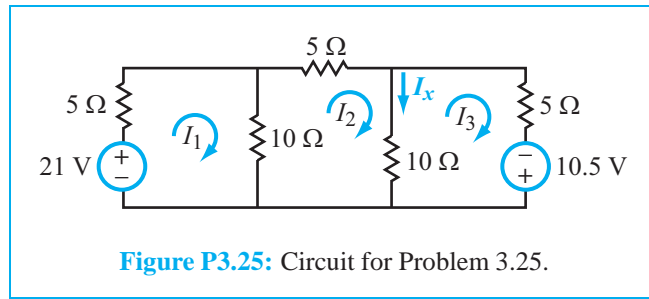**Problem 3.25** Apply mesh analysis to find  $I_x$  in the circuit of Fig. P3.25.



**Solution:**

$$\text{Mesh 1:} \quad -21 + 5I_1 + 10(I_1 - I_2) = 0$$

$$\text{Mesh 2:} \quad 10(I_2 - I_1) + 5I_2 + 10(I_2 - I_3) = 0$$

$$\text{Mesh 3:} \quad 10(I_3 - I_2) + 5I_3 - 10.5 = 0$$


Solution is:

$$I_1 = \frac{13}{5} \text{ A}, \quad I_2 = \frac{9}{5} \text{ A}, \quad I_3 = \frac{19}{10} \text{ A},$$

and

$$I_x = I_2 - I_3 = \frac{9}{5} - \frac{19}{10} = -\frac{1}{10} = -0.1 \text{ A}.$$

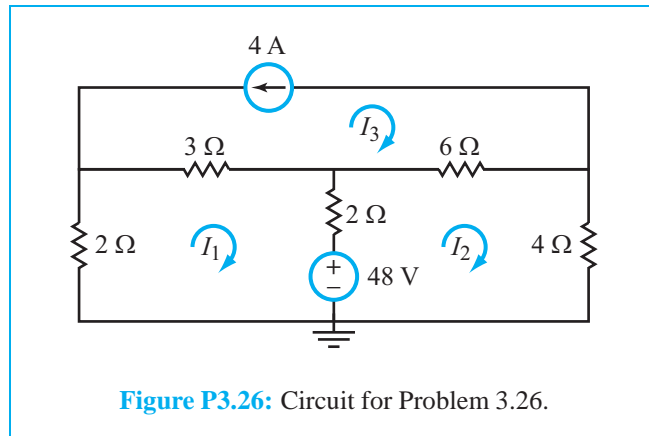**Problem 3.26** Apply mesh analysis to determine the amount of power supplied by the voltage source in Fig. P3.26.



**Solution:**

$$\text{Mesh 1: } 2I_1 + 3(I_1 - I_3) + 2(I_1 - I_2) + 48 = 0$$

$$\text{Mesh 2: } -48 + 2(I_2 - I_1) + 6(I_2 - I_3) + 4I_2 = 0$$

$$\text{Mesh 3: } I_3 = -4 \text{ A.}$$

Solution is:

$$I_1 = -8.4 \text{ A}, \quad I_2 = 0.6 \text{ A}, \quad I_3 = -4 \text{ A.}$$

Current entering “+” terminal of voltage source is:


$$I = I_1 - I_2 = -8.4 - 0.6 = -9 \text{ A.}$$

Hence,

$$P = VI = 48 \times (-9) = -432 \text{ W.}$$

**Problem 3.4** For the circuit in Fig. P3.4:

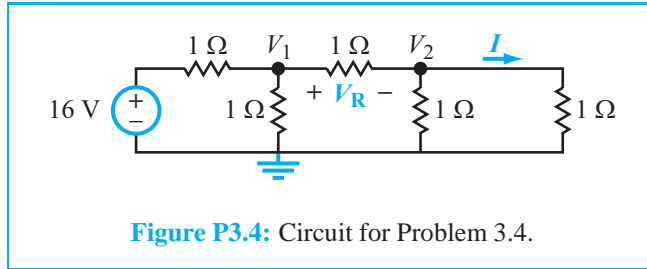- (a) Apply nodal analysis to find node voltages  $V_1$  and  $V_2$ .
- (b) Determine the voltage  $V_R$  and current  $I$ .



**Solution: (a)** At nodes  $V_1$  and  $V_2$ ,

$$\text{Node 1: } \frac{V_1 - 16}{1} + \frac{V_1}{1} + \frac{V_1 - V_2}{1} = 0 \quad (1)$$

$$\text{Node 2: } \frac{V_2 - V_1}{1} + \frac{V_2}{1} + \frac{V_2}{1} = 0 \quad (2)$$

Simplifying Eqs. (1) and (2) gives:

$$3V_1 - V_2 = 16 \quad (3)$$

$$-V_1 + 3V_2 = 0. \quad (4)$$

Simultaneous solution of Eqs. (3) and (4) leads to:


$$V_1 = 6 \text{ V}, \quad V_2 = 2 \text{ V}.$$

**(b)**

$$V_R = V_1 - V_2 = 6 - 2 = 4 \text{ V}$$

$$I = \frac{V_2}{1} = \frac{2}{1} = 2 \text{ A}.$$

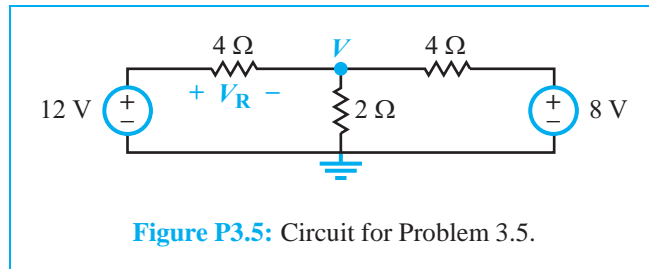**Problem 3.5** Apply nodal analysis to determine the voltage  $V_R$  in the circuit of Fig. P3.5.



**Solution:** At node  $V$ :

$$\frac{V - 12}{4} + \frac{V}{2} + \frac{V - 8}{4} = 0,$$


which leads to

$$V = 5 \text{ V}.$$

Hence,

$$V_R = 12 - V = 12 - 5 = 7 \text{ V}.$$

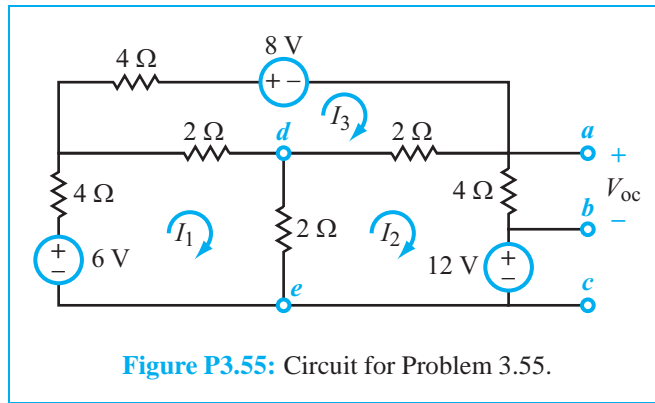**Problem 3.55** Find the Thévenin equivalent circuit at terminals  $(a, b)$  for the circuit in Fig. P3.55.



**Solution:** Since all sources in the circuit are voltage sources, the mesh current by-inspection method can be applied:


$$\begin{bmatrix} 8 & -2 & -2 \\ -2 & 8 & -2 \\ -2 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ -12 \\ -8 \end{bmatrix}$$

Matrix inversion yields:

$$I_1 = -0.1 \text{ A}, \quad I_2 = -1.9 \text{ A}, \quad I_3 = -1.5 \text{ A}.$$

$$V_{\text{Th}} = V_{\text{oc}} = 4I_2 = 4(-1.9) = -7.6 \text{ V}.$$


Suppressing sources:

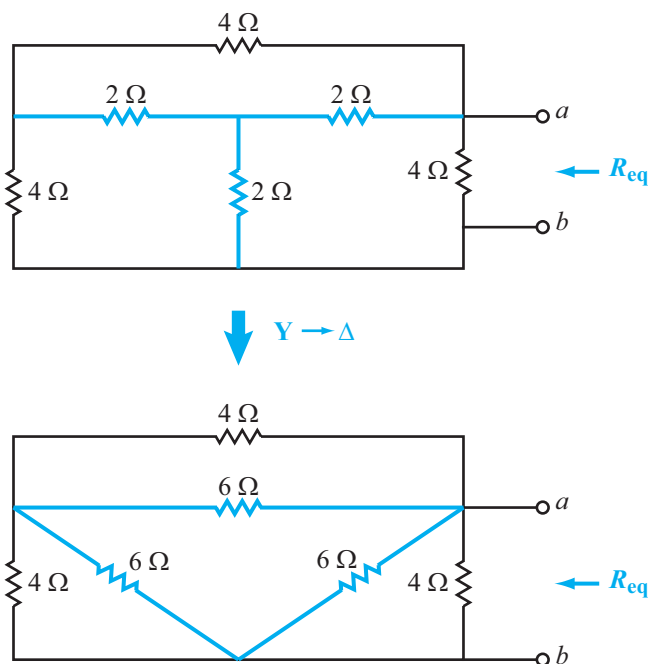

Further simplification leads to


$$R_{\text{Th}} = 1.6 \, \Omega.$$

Hence, the Thévenin circuit is:

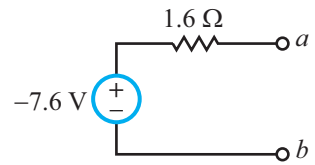



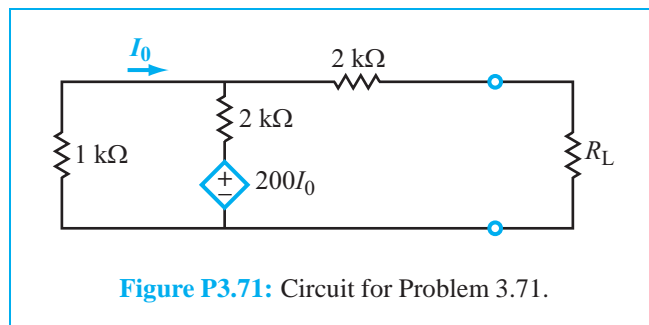**Problem 3.71** Determine the maximum power extractable from the circuit in Fig. P3.71 by the load resistor  $R_L$ .




**Solution:** The circuit has no independent sources. Hence,

$$V_{Th} = 0.$$

Consequently,  $R_L$  cannot extract any power from the circuit.

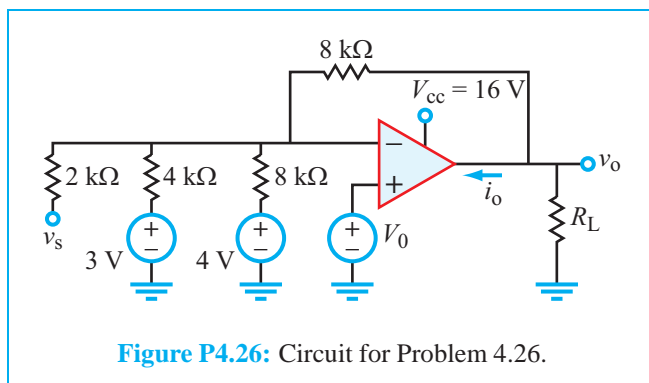**Problem 4.26** Relate  $v_o$  in the circuit of Fig. P4.26 to  $v_s$  and specify the linear range of  $v_s$ . Assume  $V_0 = 0$ .



**Solution:** With  $V_0 = 0$ , this is a summing amplifier circuit. Hence,

$$\begin{aligned} v_o &= - \left[ \left( \frac{8}{2} \right) v_s + \left( \frac{8}{4} \right) \times 3 + \left( \frac{8}{8} \right) \times 4 \right] \\ &= -[4v_s + 6 + 4] \\ &= -[4v_s + 10] \quad (\text{V}). \end{aligned}$$

For  $v_o = V_{cc} = 16 \text{ V}$ ,

$$16 = -4v_s - 10, \quad \text{or } v_s = -6.5 \text{ V}.$$


For  $v_o = -V_{cc} = -16 \text{ V}$ ,

$$-16 = -4v_s - 10, \quad \text{or } v_s = 1.5 \text{ V}$$

Hence,

$$-6.5 \text{ V} \leq v_s \leq 1.5 \text{ V}.$$

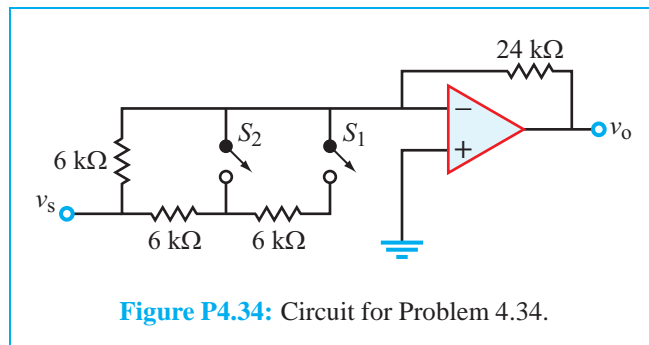
**Problem 4.34** The circuit in Fig. P4.34 contains two single-pole single-throw switches,  $S_1$  and  $S_2$ . Determine the closed circuit gain  $G = v_o/v_s$  for each of the four possible closed/open switch combinations.



**Solution:** This is an inverting amplifier circuit.

$S_1$	$S_2$	$G$
open	open	$-\frac{24}{6} = -4$
open	closed	$-\frac{24}{3} = -8$ ( $6 \parallel 6 = 3$ )
closed	open	$-\frac{24}{4} = -6$ ( $12 \parallel 6 = 4$ )
closed	closed	$-\frac{24}{3} = -8$ ( $6 \parallel 6 = 3$ ; $6 \parallel 0 = 0$ )

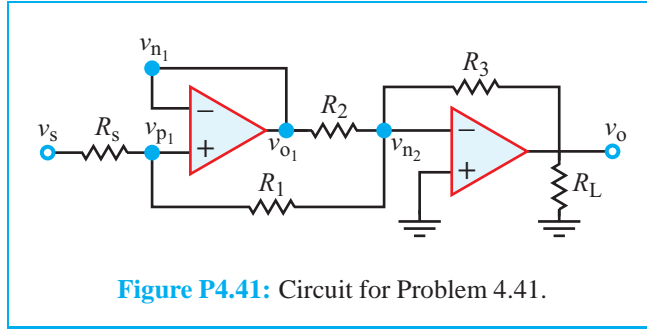**Problem 4.41** Relate  $v_o$  in the circuit of Fig. P4.41 to  $v_s$ .



**Solution:** The second stage is a standard summing amplifier:

$$v_o = \left( -\frac{R_3}{R_2} \right) v_{o1} - \left( \frac{R_3}{R_1} \right) v_{p1}.$$

For the first stage,

$$\begin{aligned} v_{n1} &= v_{o1} \\ v_{n1} &= v_{p1} \\ \frac{v_{p1} - v_s}{R_s} + \frac{v_{p1} - v_{n2}}{R_1} &= 0 \end{aligned}$$

Also,


$$v_{n2} = v_{p2} = 0.$$

Hence,

$$\begin{aligned} v_{p1} &= \frac{v_s R_1}{R_1 + R_s} \\ v_{o1} &= v_{n1} = v_{p1} \\ v_o &= \left( -\frac{R_3}{R_2} - \frac{R_3}{R_1} \right) v_{p1} = - \left( \frac{v_s R_1}{R_1 + R_s} \right) \times \frac{R_3 (R_1 + R_2)}{R_1 R_2} = - \left( \frac{R_3}{R_2} \right) \left( \frac{R_1 + R_2}{R_1 + R_s} \right) v_s. \end{aligned}$$


**Problem 5.17** Reduce the circuit in Fig. P5.17 into a single equivalent capacitor at terminals  $(a, b)$ . Assume that all initial voltages are zero at  $t = 0$ .

**Solution:**

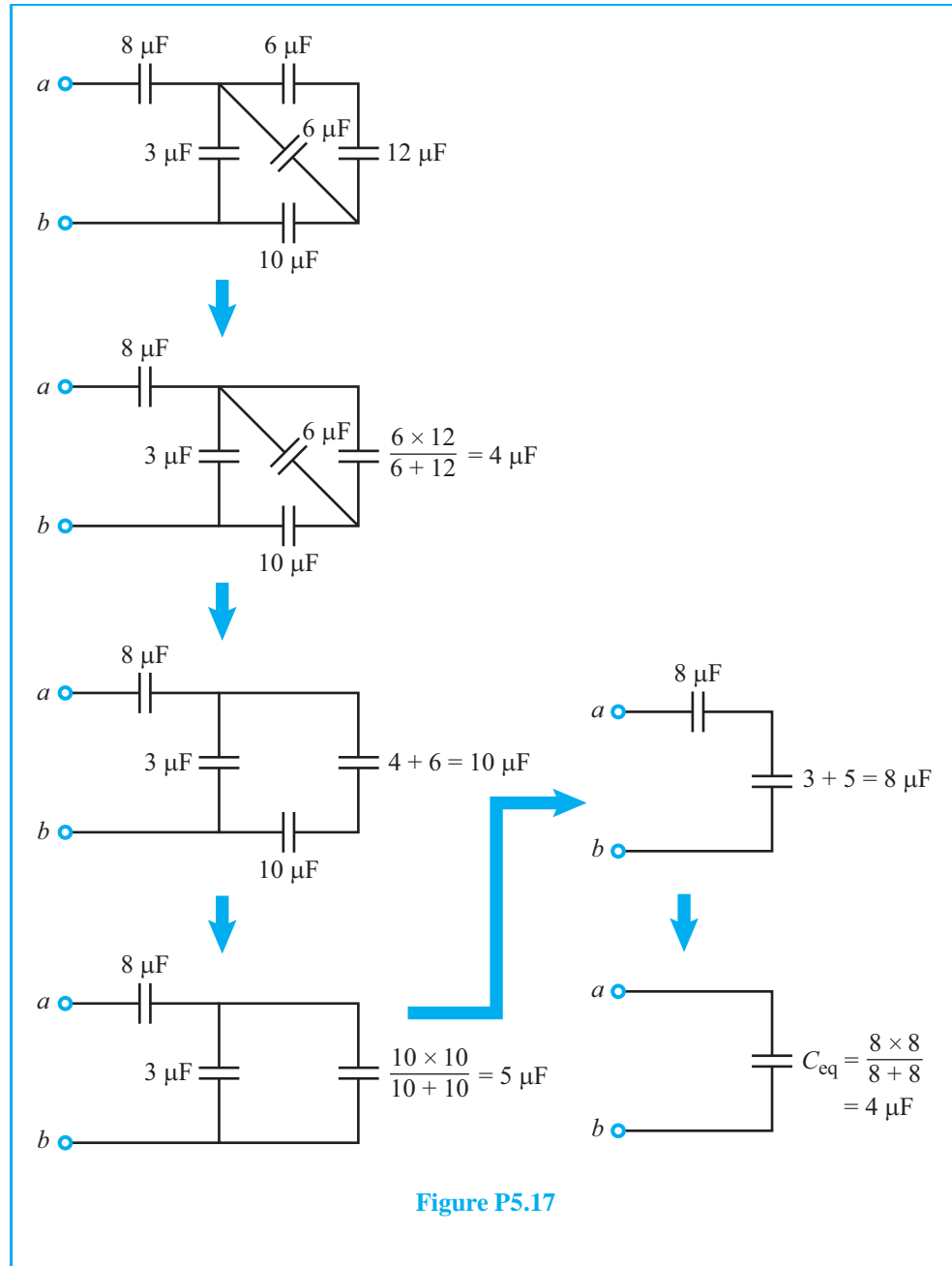

**Problem 5.28** For the circuit in Fig. P5.28, determine the voltage across  $C$  and the currents through  $L_1$  and  $L_2$  under dc conditions.

**Solution:**

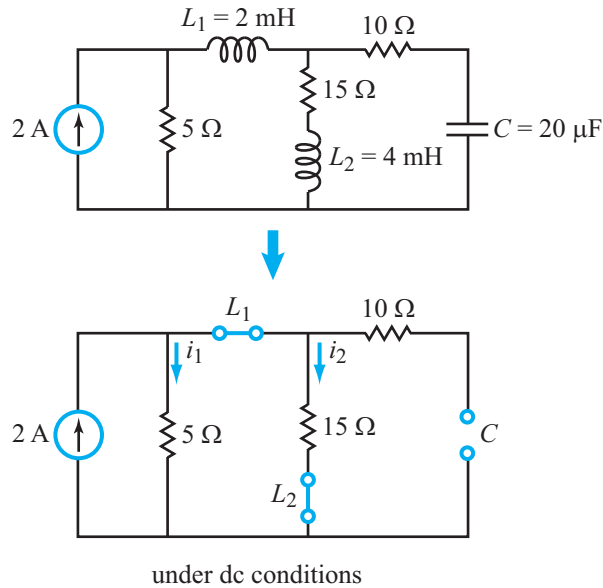

**Figure P5.28**

Current division gives:


$$i_1 = \frac{2 \times 15}{5 + 15} = 1.5 \text{ A}, \quad \Rightarrow \quad i_2 = 0.5 \text{ A}.$$

$$v_C = i_1 \times 5 = 1.5 \times 5 = 7.5 \text{ (V)},$$

Current through both  $L_1$  and  $L_2$  is  $i_2 = 0.5 \text{ A}$ .

**Problem 5.49** After having been in position 1 for a long time, the switch in the circuit of Fig. P5.49 was moved to position 2 at  $t = 0$ . Determine  $i_1(t)$  and  $i_2(t)$  for  $t \geq 0$  given that  $I_0 = 6 \text{ mA}$ ,  $R_0 = 12 \, \Omega$ ,  $R_1 = 10 \, \Omega$ ,  $R_2 = 40 \, \Omega$ ,  $L_1 = 1 \text{ H}$ , and  $L_2 = 2 \text{ H}$ .

**Solution:**

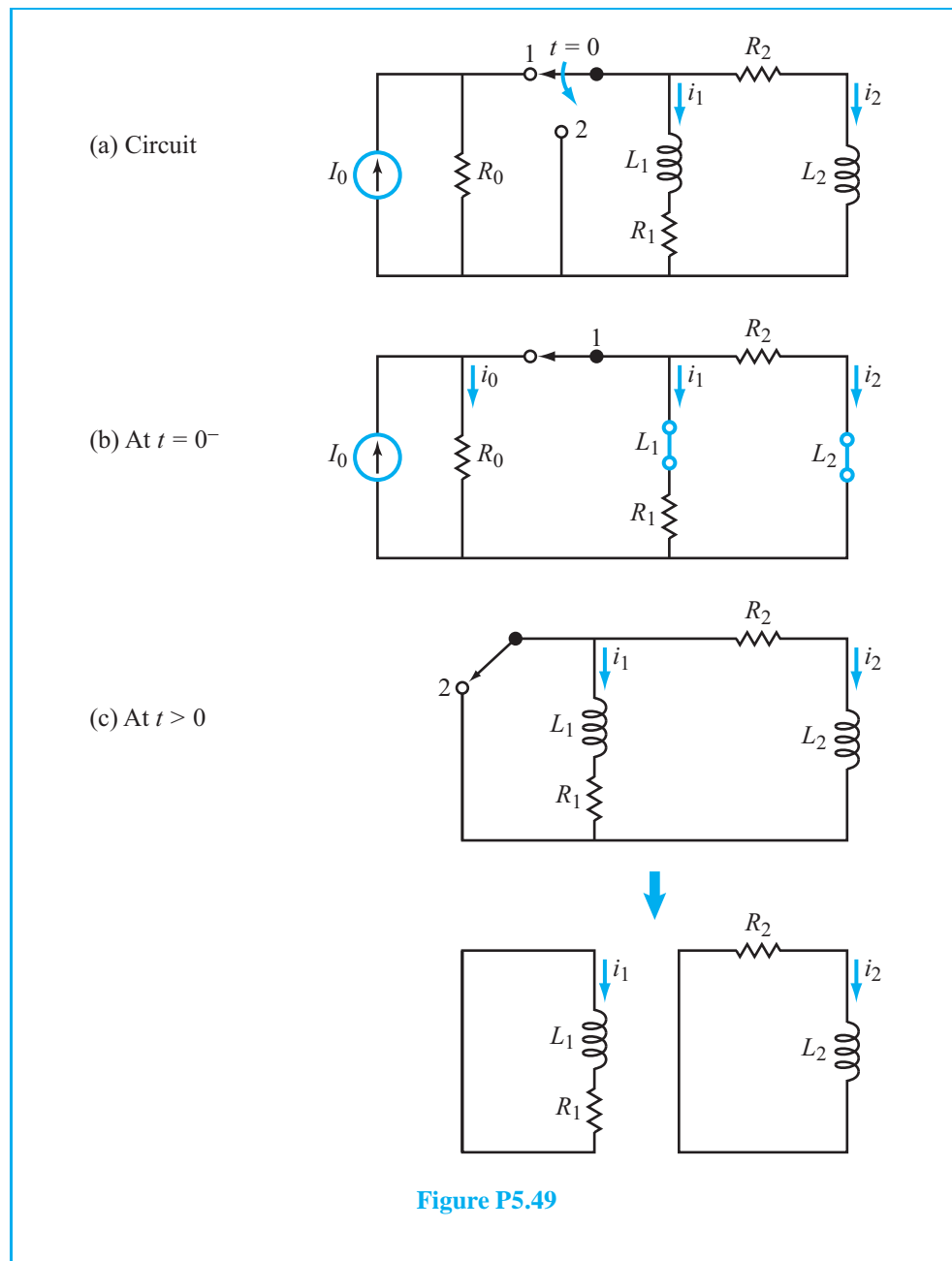

At  $t = 0^-$  (Fig. P5.49(b)),  $I_0$  will flow through the three branches such that

$$i_0 R_0 = i_1 R_1 = i_2 R_2,$$

and  $I_0 = i_0 + i_1 + i_2$ . Hence,

$$i_1(0^-) = \frac{R_0 R_2 I_0}{R_0 R_1 + R_0 R_2 + R_1 R_2} = 2.88 \quad (\text{mA}),$$

$$i_2(0^-) = \frac{R_0 R_1 I_0}{R_0 R_1 + R_0 R_2 + R_1 R_2} = 0.72 \quad (\text{mA}).$$

At  $t > 0$ , we have two independent RL circuits sharing a common short circuit.

### $R_1 L_1$ Circuit

$$i_1(0) = i_1(0^-) = 2.88 \quad (\text{mA})$$

$$i_1(\infty) = 0$$

$$\tau_1 = \frac{L_1}{R_1} = \frac{1}{10} = 0.1 \text{ s}$$

$$i_1(t) = 2.88e^{-10t} \quad (\text{mA}), \quad \text{for } t \geq 0.$$

### $R_2 L_2$ Circuit

$$i_2(0) = i_2(0^-) = 0.72 \quad (\text{mA})$$


$$i_2(\infty) = 0$$

$$\tau_2 = \frac{L_2}{R_2} = \frac{2}{40} = 0.05 \text{ s}$$

$$i_2(t) = 0.72e^{-20t} \quad (\text{mA}), \quad \text{for } t \geq 0.$$




**Problem 6.7** For the circuit of Fig. P6.7, determine  $i_1(0)$  and  $i_2(0)$ .

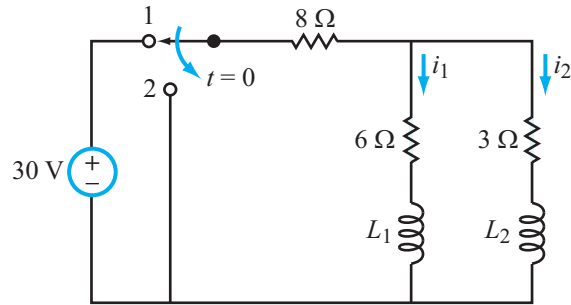

**Figure P6.7:** Circuit for Problem 6.7.

**Solution:**

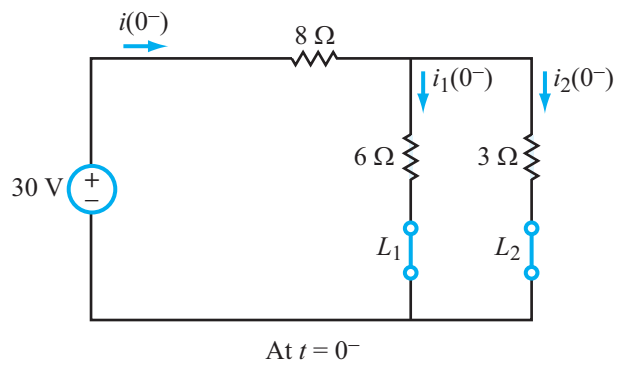

$$3 \parallel 6 = \frac{3 \times 6}{3 + 6} = 2 \, \Omega.$$

Hence,

$$i(0^-) = \frac{30}{8 + 2} = 3 \, \text{A}.$$

Current division gives

$$i_1(0^-) = \frac{i(0^-) \times 3}{6 + 3} = \frac{3 \times 3}{9} = 1 \, \text{A},$$


$$i_2(0^-) = \frac{i(0^-) \times 6}{6 + 3} = 2 \, \text{A}.$$

Since  $i$  in an inductor cannot change instantaneously,

$$i_1(0) = 1 \, \text{A}, \quad i_2(0) = 2 \, \text{A}.$$

**Problem 7.27** Determine the equivalent impedance:


- (a)  $Z_1$  at 1000 Hz (Fig. P7-27)(a))
- (b)  $Z_2$  at 500 Hz (Fig. P7-27)(b))
- (c)  $Z_3$  at  $\omega = 10^6$  rad/s (Fig. P7-27)(c))
- (d)  $Z_4$  at  $\omega = 10^5$  rad/s (Fig. P7-27)(d))
- (e)  $Z_5$  at  $\omega = 2000$  rad/s (Fig. P7-27)(e))

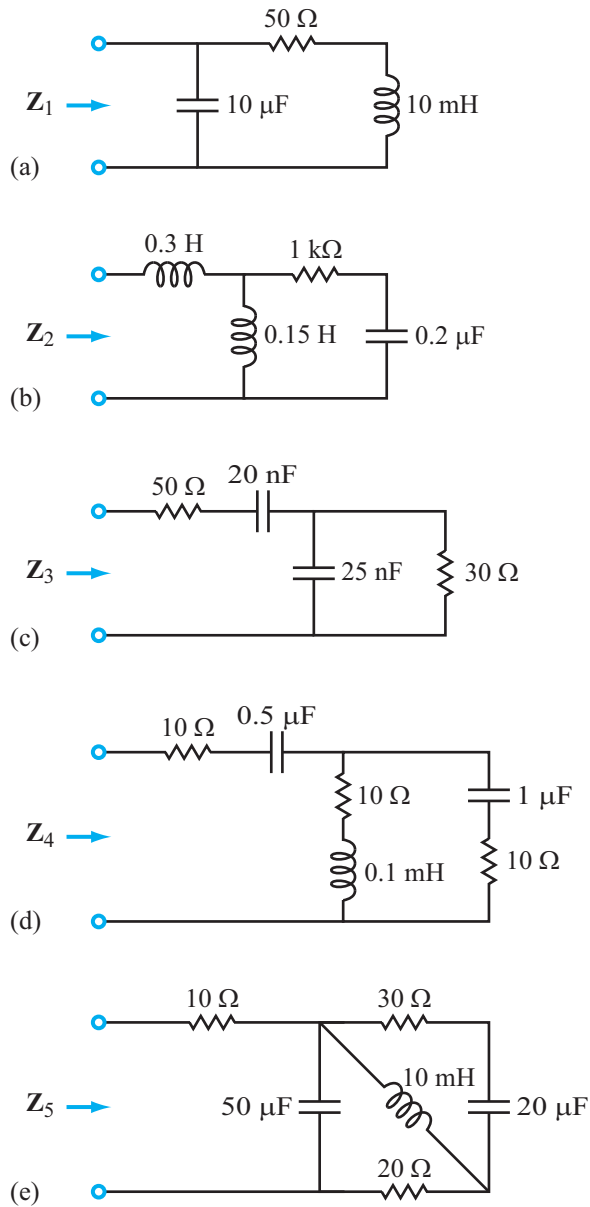

**Figure P7.27:** Circuit for Problem 7.27.

**Solution:**

(a)

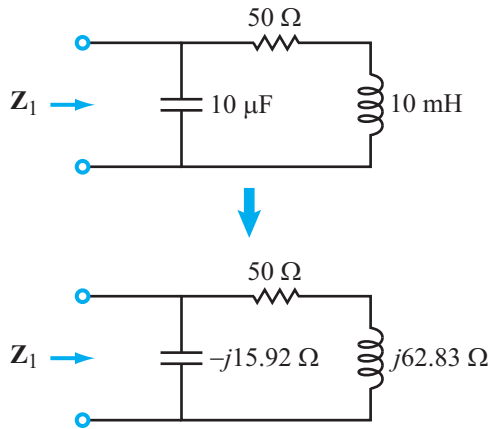


$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{2\pi \times 10^3 \times 10 \times 10^{-6}} = -j15.92\ \Omega$$

$$\mathbf{Z}_L = j\omega L = j2\pi \times 10^3 \times 10^{-2} = j62.83\ \Omega$$

$$\begin{aligned} \mathbf{Z}_1 &= (50 + j62.83) \parallel (-j15.92) \\ &= \frac{(50 + j62.83)(-j15.92)}{50 + j62.83 - j15.92} \\ &= \frac{1000 - j796}{50 + j46.91} \cdot \left( \frac{50 - j46.91}{50 - j46.91} \right) \\ &= \frac{12660 - j86710}{4701} = (2.7 - j18.5)\ \Omega. \end{aligned}$$

(b)

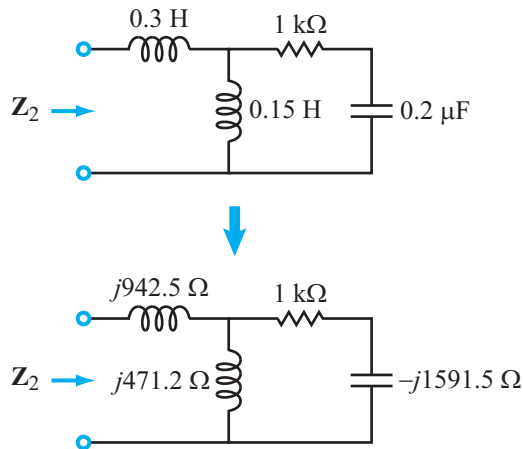



$$\mathbf{Z}_{L_1} = j\omega L_1 = j2\pi \times 500 \times 0.3 = j942.5\ \Omega$$

$$\mathbf{Z}_{L_2} = j\omega L_2 = j471.2\ \Omega$$

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{2\pi \times 500 \times 0.2 \times 10^{-6}} = -j1591.5\ \Omega$$

$$\begin{aligned} \mathbf{Z}_2 &= j942.5 + j471.2 \parallel (1000 - j1591.5) \\ &= j942.5 + \frac{j471.2(1000 - j1591.5)}{1000 - j1591.5 + j471.2} = (98.5 + j1524.0)\ \Omega \end{aligned}$$

(c)

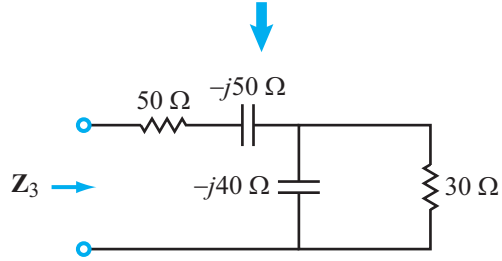
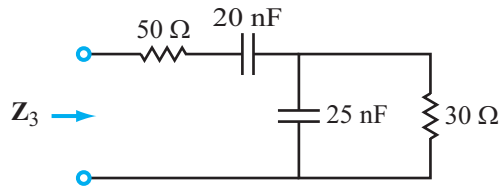


$$Z_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{10^6 \times 20 \times 10^{-9}} = -j50\ \Omega$$

$$Z_{C_2} = \frac{-j}{\omega C_2} = \frac{-j}{10^6 \times 25 \times 10^{-9}} = -j40\ \Omega$$

$$Z_3 = 50 - j50 + \frac{30 \times (-j40)}{30 - j40} = (69.2 - j64.4)\ \Omega.$$

(d)

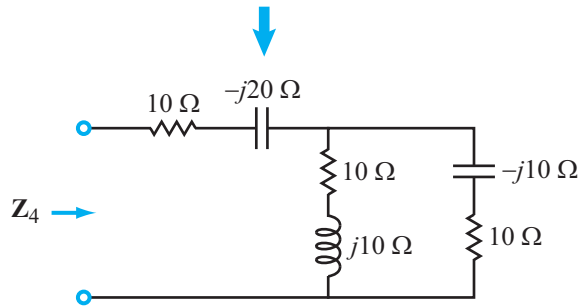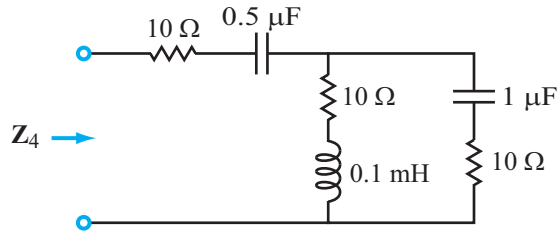






$$Z_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{10^5 \times 0.5 \times 10^{-6}} = -j20\ \Omega$$

$$Z_{C_2} = \frac{-j}{\omega C_2} = -j10\ \Omega$$

$$Z_L = j\omega L = j \times 10^5 \times 10^{-4} = j10\ \Omega$$

$$Z_4 = (10 - j20) + \frac{(10 + j10)(10 - j10)}{10 + j10 + 10 - j10} = (10 - j20) + 10 = (20 - j20)\ \Omega.$$

(e)

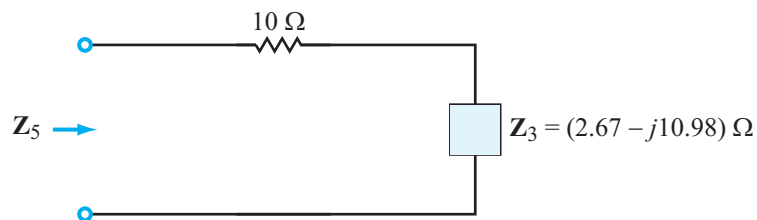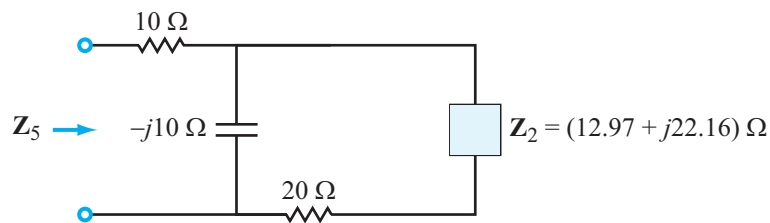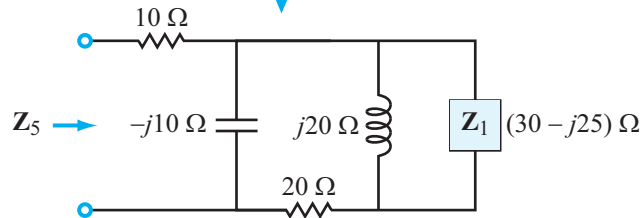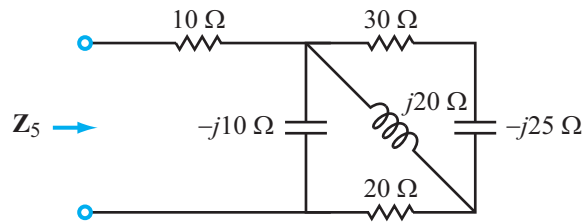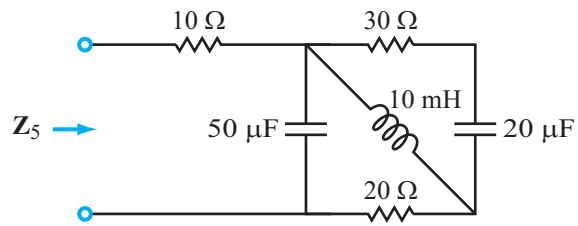

$$\mathbf{Z}_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{2000 \times 50 \times 10^{-6}} = -j10 \, \Omega$$

$$\mathbf{Z}_{C_2} = \frac{-j}{\omega C_2} = \frac{-j}{2000 \times 20 \times 10^{-6}} = -j25 \, \Omega$$

$$\mathbf{Z}_L = j\omega L = j2000 \times 10 \times 10^{-3} = j20 \, \Omega$$

$$\mathbf{Z}_2 = \mathbf{Z}_1 \parallel (j20)$$

$$= \frac{(30 - j25)(j20)}{30 - j25 + j20}$$

$$= \frac{500 + j600}{30 - j5} \cdot \frac{(30 + j5)}{(30 + j5)}$$

$$= \frac{12000 + j20500}{925} = (12.97 + j22.16) \, \Omega$$

$$\mathbf{Z}_3 = (20 + \mathbf{Z}_2) \parallel (-j10)$$


$$= \frac{(32.97 + j22.16)(-j10)}{32.97 + j22.16 - j10}$$

$$= \frac{221.6 - j329.7}{32.97 + j12.16} \cdot \frac{(32.97 - j12.16)}{(32.97 - j12.16)}$$

$$= (2.67 - j10.98) \, \Omega$$

$$\mathbf{Z}_5 = 10 + \mathbf{Z}_3 = (12.67 - j10.98) \, \Omega.$$

**Problem 7.34** At what angular frequency  $\omega$  is the current  $i(t)$  in the circuit of Fig. P7.34 in-phase with the source voltage  $v_s(t)$ ?

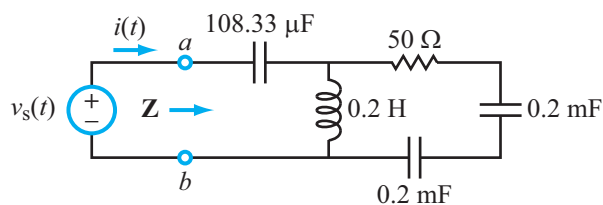

**Figure P7.34:** Circuit for Problem 7.34.

**Solution:** For  $i(t)$  to be in-phase with  $v_s(t)$ , it is necessary that  $\mathbf{Z}$  be purely real. Noting that the two in-series capacities add up to 0.1 mF,

$$\begin{aligned}
 \mathbf{Z} &= \frac{-j}{108.33\omega \times 10^{-6}} + j0.2\omega \parallel \left( 50 - \frac{j}{10^{-4}\omega} \right) \\
 &= -j \frac{9.23 \times 10^3}{\omega} + \frac{j0.2\omega \left( 50 - \frac{j10^4}{\omega} \right)}{50 - j\frac{10^4}{\omega} + j0.2\omega} \\
 &= -j \frac{9.23 \times 10^3}{\omega} + \frac{2000 + j10\omega}{50 + j \left( 0.2\omega - \frac{10^4}{\omega} \right)} \\
 &= -j \frac{9.23 \times 10^3}{\omega} + \frac{(2000 + j10\omega) \left[ 50 - j \left( 0.2\omega - \frac{10^4}{\omega} \right) \right]}{2500 + \left( 0.2\omega - \frac{10^4}{\omega} \right)^2} \\
 &= -j \frac{9.23 \times 10^3}{\omega} + \frac{[1 \times 10^5 + (2\omega^2 - 10^5)] + j \left[ 500\omega - 400\omega + \frac{2 \times 10^7}{\omega} \right]}{2500 + \left( 0.2\omega - \frac{10^4}{\omega} \right)^2}
 \end{aligned}$$


The imaginary part of  $\mathbf{Z}$  has to be zero,

$$-j \frac{9.23 \times 10^3}{\omega} + \frac{j \left( 100\omega + \frac{2 \times 10^7}{\omega} \right)}{2500 + \left( 0.2\omega - \frac{10^4}{\omega} \right)^2} = 0$$

Solution of quadratic equation, obtained after cross multiplication, is


$$\omega = 200 \text{ rad/s} \quad \text{or} \quad 292.8 \text{ rad/s.}$$

**Problem 8.13** Determine the average power dissipated in the load resistor  $R_L$  of the circuit in Fig. P8.13, given that  $V_s = 100$  V,  $R_1 = 1$  k $\Omega$ ,  $R_2 = 0.5$  k $\Omega$ ,  $R_L = 2$  k $\Omega$ ,  $Z_L = j0.8$  k $\Omega$ , and  $Z_C = -j4$  k $\Omega$ .

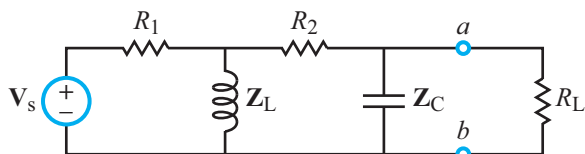

**Figure P8.13:** Circuit for Problem 8.13.

**Solution:**

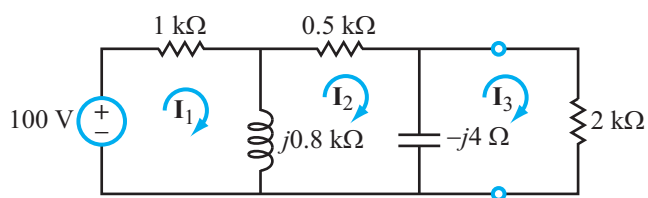

Mesh-current by inspection gives:

$$\begin{bmatrix} (1 + j0.8) & -j0.8 & 0 \\ -j0.8 & (0.5 - j3.2) & j4 \\ 0 & j4 & (2 - j4) \end{bmatrix} \times 10^3 \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix}.$$

MATLAB® software solution gives:

$$\mathbf{I}_1 = 65.36 \angle -31.55^\circ \quad (\text{mA})$$

$$\mathbf{I}_2 = 24.87 \angle 58.48^\circ \quad (\text{mA})$$


$$\mathbf{I}_3 = 22.28 \angle 31.98^\circ \quad (\text{mA})$$

$$P_{\text{av}} = \frac{1}{2} |\mathbf{I}_3|^2 R_L = 496.4 \text{ mW}.$$



## Section 8-4: Power Factor

**Problem 8.22** The RL load in Fig. P8.22 is compensated by adding the shunt capacitance  $C$  so that the power factor of the combined (compensated) circuit is exactly unity. How is  $C$  related to  $R$ ,  $L$ , and  $\omega$  in that case?

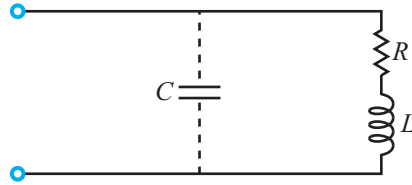

**Figure P8.22:** Circuit for Problem 8.22.

**Solution:** For the combined load, the impedance is

$$\begin{aligned} Z &= (R + j\omega L) \parallel \left( \frac{1}{j\omega C} \right) \\ &= \frac{(R + j\omega L) \left( \frac{-j}{\omega C} \right)}{R + j \left( \omega L - \frac{1}{\omega C} \right)} \\ &= \frac{\omega L - jR}{\omega RC - j(1 - \omega^2 LC)} \\ &= \frac{(\omega L - jR)[\omega RC + j(1 - \omega^2 LC)]}{[\omega RC - j(1 - \omega^2 LC)][\omega RC + j(1 - \omega^2 LC)]} \\ &= \frac{[\omega^2 RLC + R(1 - \omega^2 LC)]}{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2} + \frac{j[\omega L(1 - \omega^2 LC) - \omega R^2 C]}{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2} \end{aligned}$$

For the  $pf$  to be unity, the imaginary component of  $\mathbf{Z}$  has to be zero, which is realized if

$$\omega L(1 - \omega^2 LC) - \omega R^2 C = 0.$$

or

$$C = \frac{L}{R^2 + \omega^2 L^2}.$$