
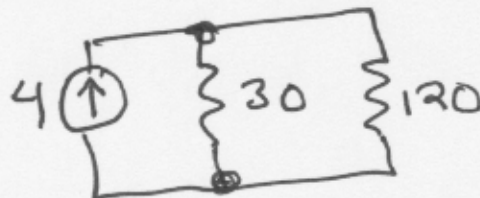
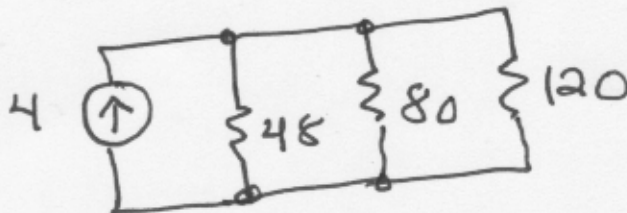
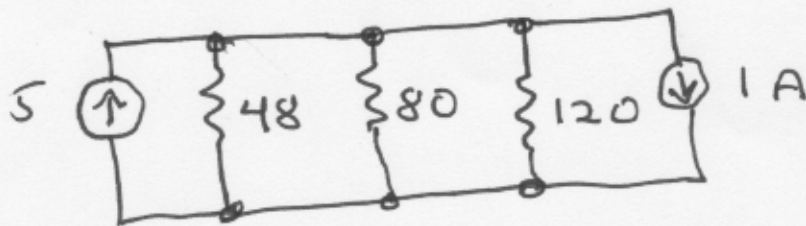
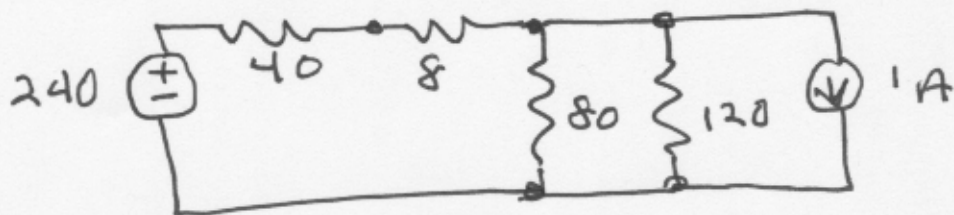


# ELEN 50 W-17 Mid-term II


(2/24/2017)

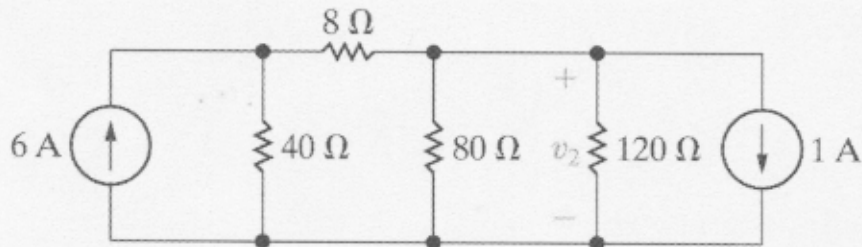1. Use source transforms to calculate  $v_2$  in this circuit:



$$V_2 = 4(24) = 96\text{ V}$$

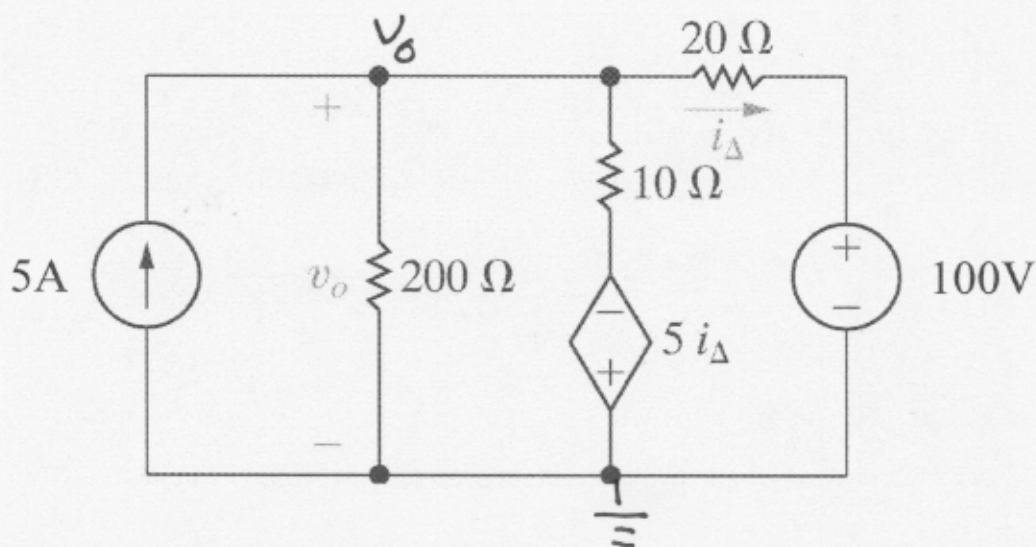2. Use the node voltage method to solve for  $v_0$  in this circuit. How many essential nodes are present? Indicate your choice of reference node in the diagram.



using KCL for the top node:

$$-5 + \frac{v_o}{200} + \frac{v_o + 5i_\Delta}{10} + \frac{v_o - 100}{20} = 0$$

$$i_\Delta = \frac{v_o - 100}{20} \quad \therefore \frac{v_o + 5i_\Delta}{10} = \frac{v_o}{10} + \frac{5v_o}{200} + \frac{500}{200}$$


so

$$-1000 + v_o + 20v_o + 5v_o - 500 + 10v_o - 1000 = 0$$

$$36v_o = 2500$$


$$v_o = 69.444$$

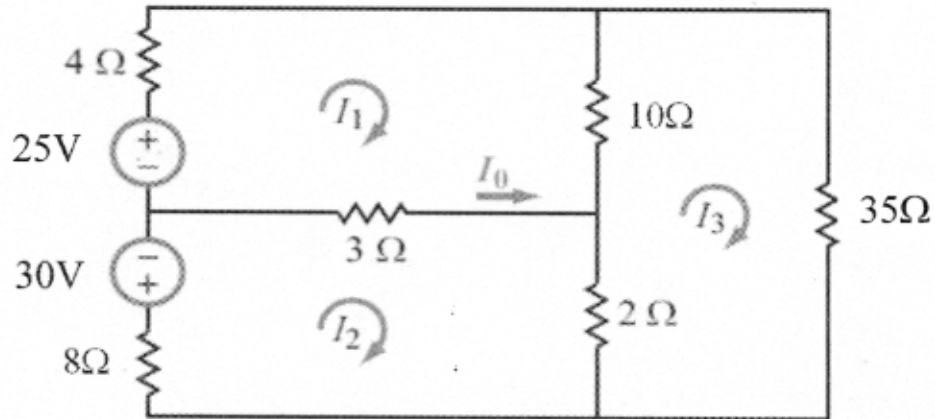3. Write the matrix equation describing the mesh currents,  $I_1$ ,  $I_2$ , and  $I_3$  in terms of the source voltages and resistances using mesh current analysis by inspection. You don't need to solve the matrix equation for the mesh currents.



$$\begin{bmatrix} 17 & -3 & -10 \\ -3 & 13 & -2 \\ -10 & -2 & 47 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 25 \\ -30 \\ 0 \end{pmatrix}$$

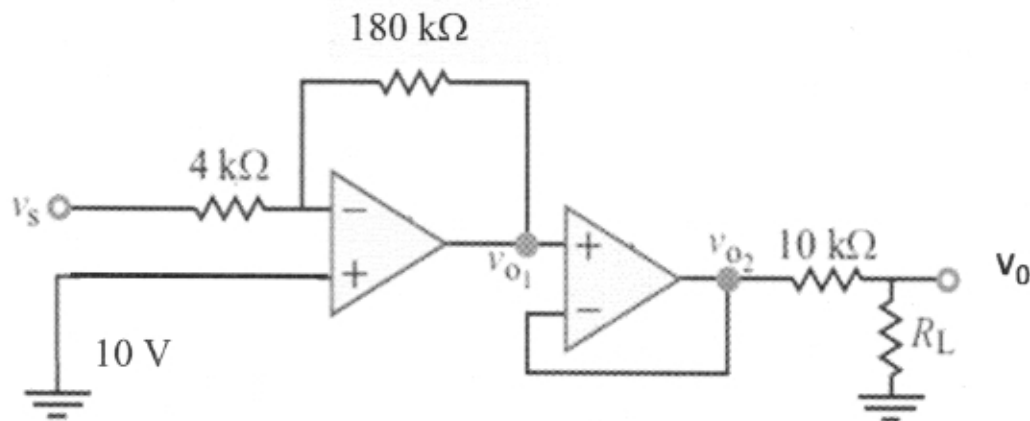4. This circuit contains two ideal op amps. (a.) describe briefly what each amplifier stage does (b.) obtain an expression for the output voltage,  $v_o$  in terms of  $v_s$  and  $R_L$



- The first stage is an inverting amplifier:  
writing KCL at the inverting node:


$$\frac{V_n - V_s}{4K} = \frac{V_{o1} - V_n}{180K} \quad V_n = V_p = 0 \text{ (because } V_p \text{ is ground)}$$

$$\text{SO } -\frac{V_s}{4K} = \frac{V_{o1}}{180K} \quad \text{so } V_{o1} = -45 V_s$$

- the second stage is a follower so  $V_{o2} = V_{o1}$
- finally, the  $10K$  &  $R_L$  form a voltage divider

$$\text{SO } V_o = \frac{R_L}{10K + R_L} V_{o2} = \frac{R_L}{10K + R_L} [-45 V_s]$$

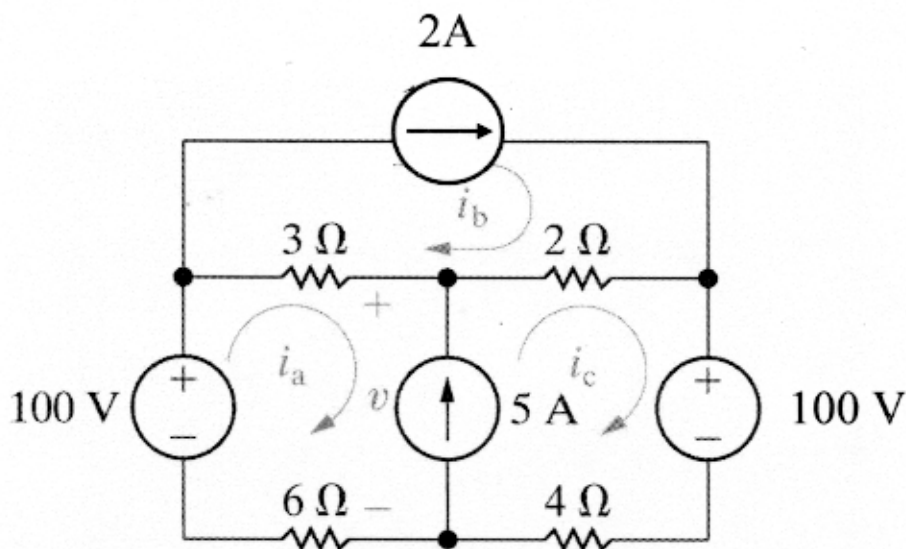5. Solve this circuit by finding mesh currents  $i_a$ ,  $i_b$ , and  $i_c$  using the mesh current method. Is there a supermesh present? How many mesh current equations will have to be solved?



The circuit has a supermesh involving mesh a & mesh b

Also, we already know  $i_b = 2A$  So, writing the

single supermesh equation for the circuit!

$$-100 + 3(i_a - i_b) + 2(i_c - i_b) + 100 + 4i_c + 6i_a = 0$$

$$3i_a - 6 + 2i_c - 4 + 4i_c + 6i_a = 0$$

$$9i_a + 6i_c - 10 = 0$$

for the supermesh  $i_c - i_a = 5$

$$\text{so } 15i_a = -20 \Rightarrow i_a = -\frac{20}{15} = -1.333A$$

$$i_c = 5 + i_a = 3.667A$$