
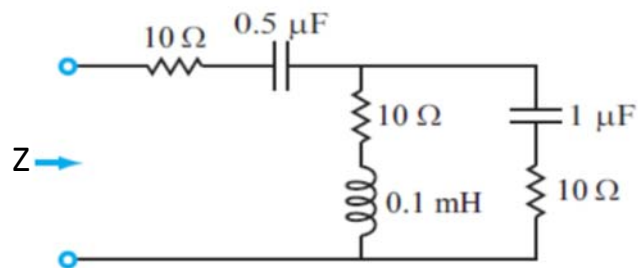


ELEN 50 – W17 HW#4
(due March 10 before class)

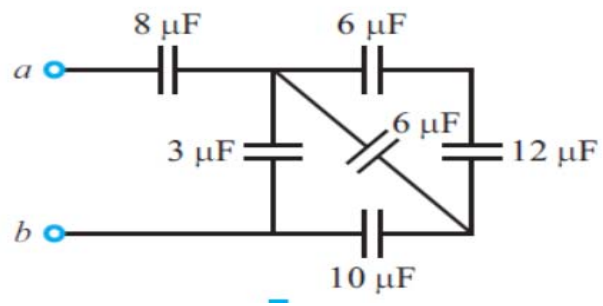
1. What is the complex impedance, Z , of this circuit at $\omega = 10^5$ rad/sec?



2. Reduce this circuit to a single equivalent capacitor:



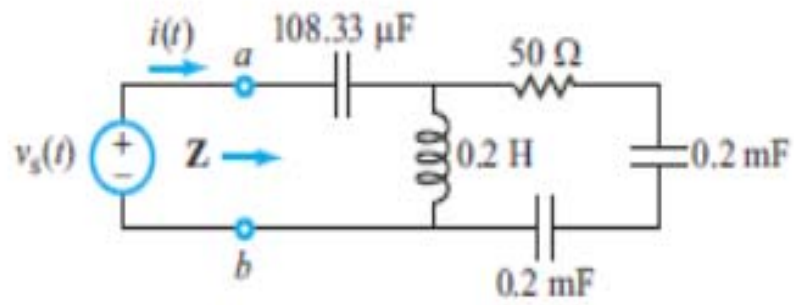3. At what angular frequency, ω , is the current, $i(t)$ in phase with the applied voltage $v_s(t)$?



4. Find the voltage $v(t)$ and current $i(t)$ in this circuit. The switch closes at time $t=0$.

