
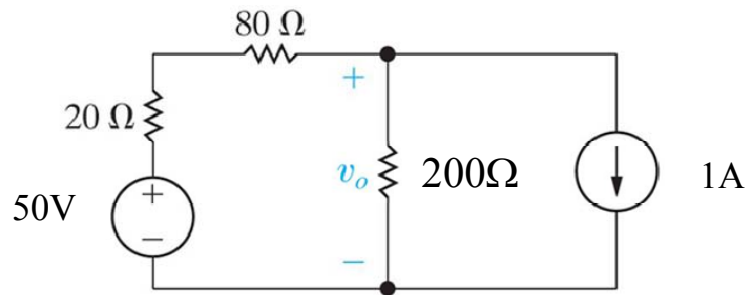


ELEN 50 Winter 2017 Problem Set #2
(due before class 2/3)

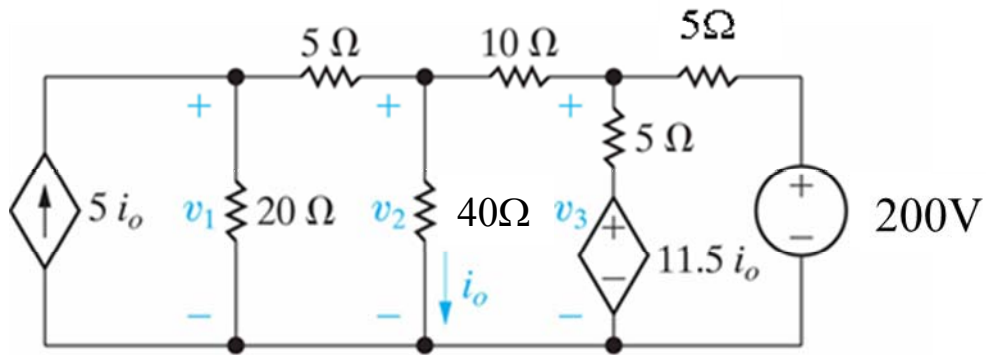
1. Use the node voltage method to find v_o in this circuit. Show your choice of reference node.






2. Find the node voltages v_1 , v_2 , and v_3 in this circuit. Show your choice for a reference node and notice the circuit contains both a dependent current and voltage source. You can show numerical solutions using MATLAB but you must write down the node voltage equations in standard form.



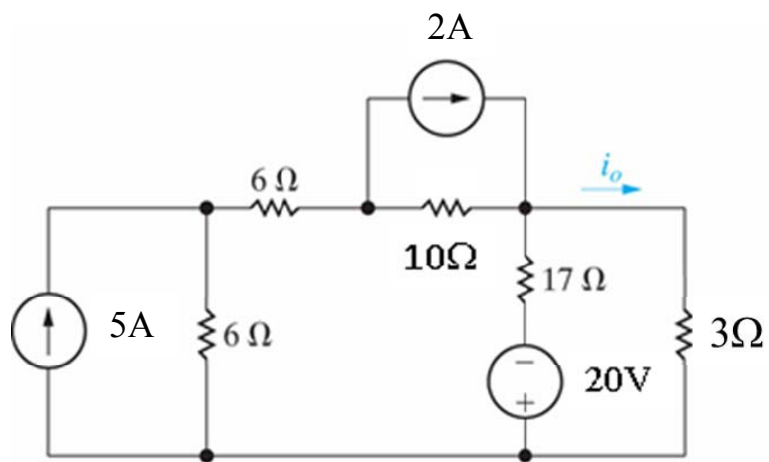3. Use a series of source transformations to find i_o in this circuit:



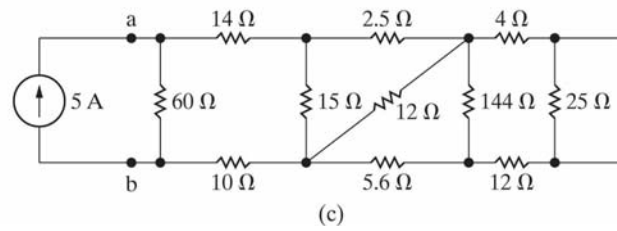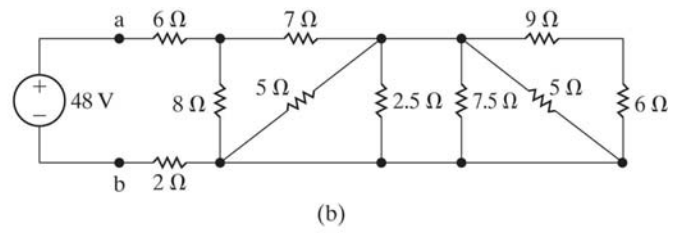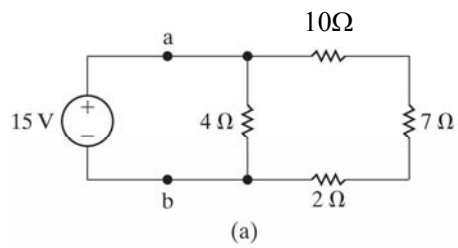4. Find the equivalent resistance R_{ab} for these circuits:



5. Use the node voltage method to find the power developed in the 20V source. Is there a supernode in this circuit? If so, identify it and show your choice of a reference node.

